

DEC-2008**[3462]-145****S.E. (E & TC) (First Semester) EXAMINATION, 2008****SIGNALS AND SYSTEMS****(2003 COURSE)****Time : Three Hours****Maximum Marks : 100**

N.B. :— (i) Answer *three* questions from Section I and *three* questions from Section II.

- (ii) Answers to the two Sections should be written in separate answer-books.
- (iii) Neat diagrams must be drawn wherever necessary.
- (iv) Figures to the right indicate full marks.
- (v) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.
- (vi) Assume suitable data, if necessary.

SECTION I

1. (a) Determine whether the following signals are periodic; if they are periodic, find the fundamental period :

(i) $x(t) = \cos^2(2\pi t)$

(ii) $x[n] = (-1)^n$ [8]


- (b) Sketch the waveforms of the following signals : [10]

(i) $x(t) = u(t + 1) - 2u(t) - 2u(t - 1)$


(ii) $y(t) = r(t + 1) - r(t) + r(t - 2).$

Or

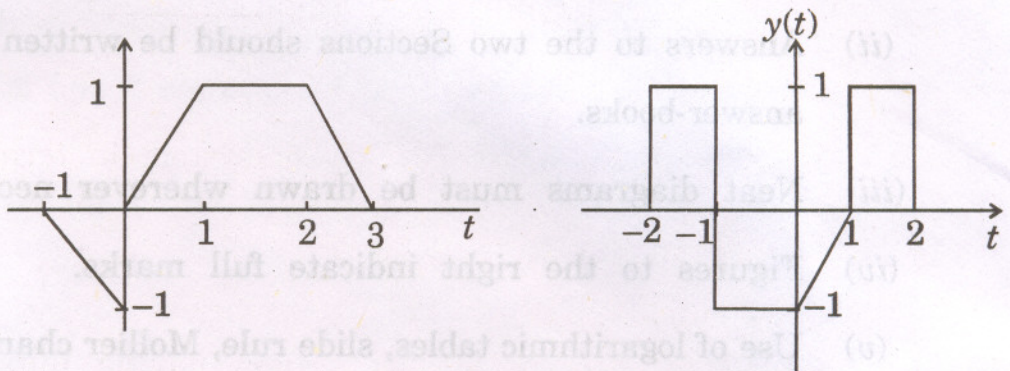
2. (a) The systems that follow have input $x(t)$ or $x[n]$ and output $y(t)$ or $y[n]$. For each system determine whether it is (I) memoryless (II) stable (III) causal (IV) linear (V) time invariant. [10]
- (i) $y[n] = 2x[n] u[n]$
- (ii) $y(t) = x(2 - t)$.
- (b) Let $x(t)$ and $y(t)$ be given in Fig. below. Carefully sketch the following signals : $x(t + 1)$ $y(t - 2)$. [8]



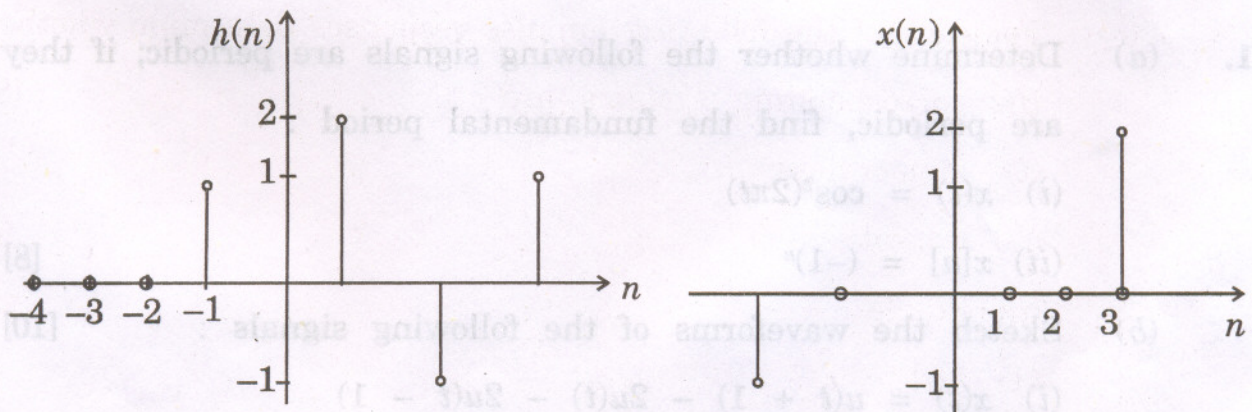3. (a) Evaluate the following discrete time convolution : [8]



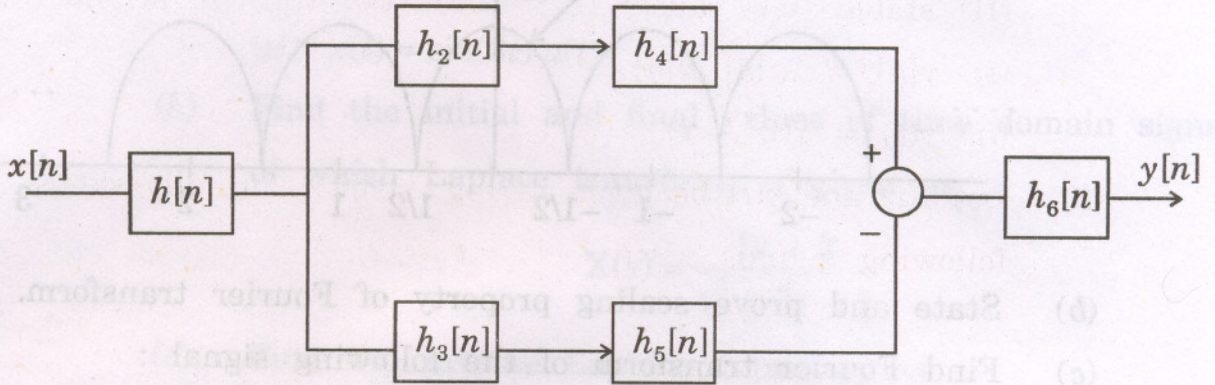- (b) Find the expression for the impulse response relating the input $x[n]$ to output $y[n]$ in terms of the impulse response of each subsystem for LTI system. [4]




- (c) Derive expression for stability of system in terms of impulse response. [4]

Or

4. (a) Find step response of the system having impulse response $h[n] = \delta[n] - \delta[n - 2]$. [5]
- (b) What is the application of convolution and correlation in signals and systems ? [3]
- (c) For each of the following impulse responses determine whether the corresponding systems are : [8]
- (i) Memoryless
 - (ii) Causal
 - (iii) Stable
- (1) $h[t] = e^{-2t} u(t - 1)$
- (2) $h[n] = 2u[n] - 2u[n - 5]$

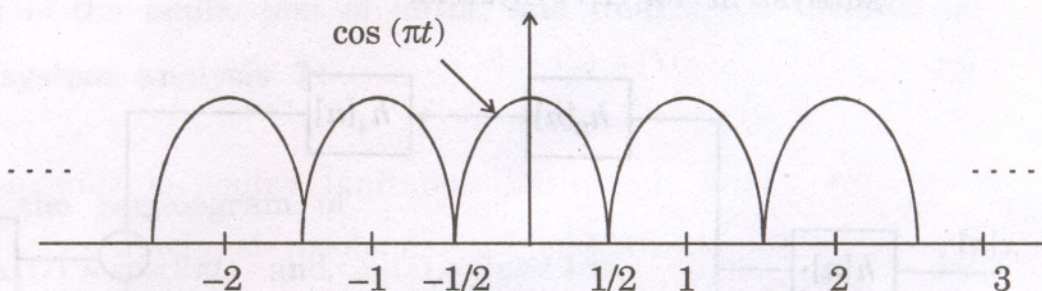5. (a) Find the Fourier series coefficients of full wave rectified cosine waveform shown in the following Fig. [8]



- (b) State and prove scaling property of Fourier transform. [4]
 (c) Find Fourier transform of the following signal :

$$x(t) = \frac{d}{dt} (2t e^{-2t} u(t)). \quad [4]$$

- (d) What are the limitations of Fourier transform over Laplace transform ? [2]

Or

6. (a) Use integration property to find inverse Fourier transform of

$$X(j\omega) = \frac{1}{j\omega(j\omega + 1)} + \pi\delta(\omega). \quad [6]$$

- (b) Find the Fourier representation of the following time domain signal :

$$x(t) = e^{-2t} u(t - 3). \quad [4]$$

- (c) Determine frequency response and impulse response for the system described by the following differential equation. Assume zero initial condition :

$$\frac{d}{dt} (y(t)) + 3y(t) = x(t). \quad [8]$$

SECTION II

7. (a) Determine Laplace transform and ROC of the following signals : [8]

(i) $x(t) = u(t - 5)$

(ii) $x(t) = \sin(3t) u(t)$

- (b) Find the initial and final values of time domain signal $x(t)$ of which Laplace transform is given as : [4]

$$X(s) = \frac{2s + 3}{s^2 + 5s + 6}.$$


- (c) Find the inverse Laplace transform of

$$X(s) = \frac{3s + 2}{s^2 + 4s + 5}. \quad [4]$$

- (d) Explain the significance of region of convergence for Laplace transform. [2]

Or

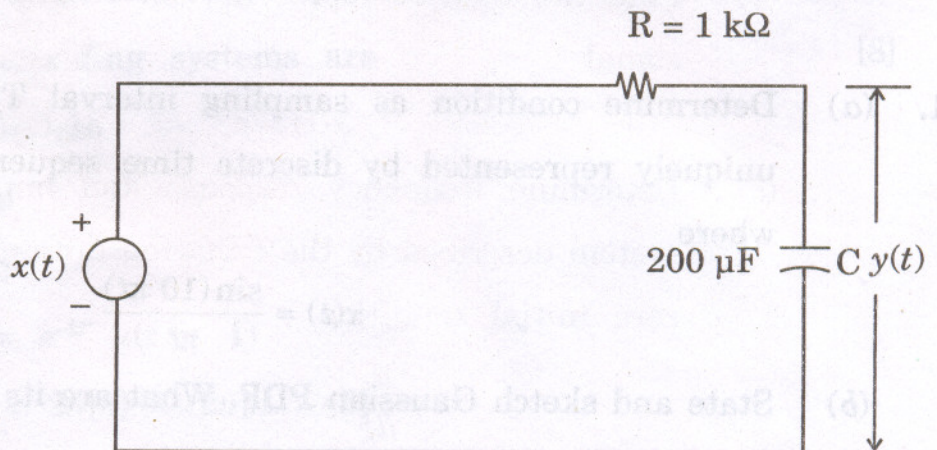8. (a) Use Laplace transform to find the voltage across capacitor $y(t)$ for the RC circuit shown in the figure below. In response to applied voltage $x(t) = \frac{3}{5}e^{-2t}u(t)$ and initial condition $y(0^-) = 2$. [8]



- (b) State and prove convolution and differentiation property of Laplace transform. [8]
- (c) What is the application of initial and final value theorem in LTI system analysis ? [2]

9. (a) Find the correlogram of

$$x_1(t) = \cos(2\pi t) \text{ and } x_2(t) = 2\cos(4\pi t). \quad [4]$$

- (b) State the properties of autocorrelation and sketch the autocorrelation of sine bursts. [8]
- (c) Define energy spectral density and power spectral density functions. What is their application ? [4]

Or

10. (a) State and prove the relation between autocorrelation and ESD. [6]
- (b) Find ESD of the following energy signal :

$$x(t) = e^{-100t}u(t). \quad [4]$$

- (c) Find autocorrelation of the following discrete time signal :

$$x[n] = \{ \underset{\uparrow}{1}, 2, 1 \}. \quad [4]$$

- (d) State Parseval's energy theorem. [2]

11. (a) Determine condition as sampling interval T_s so that $x(t)$ is uniquely represented by discrete time sequence $x[n] = x[nT_s]$ where

$$x(t) = \frac{\sin(10\pi t)}{\pi t}. \quad [4]$$

- (b) State and sketch Gaussian PDF. What are its applications ? [4]

- (c) With example explain the concept of continuous and discrete time random variable. What is PDF and distribution function (CDF) of tossing a dice experiment ? [8]

Or

12. (a) Find the mean and variance of uniform PDF. [6]
(b) What are the properties of mean and variance ? [6]
(c) In a certain city the number of power outages per month is a random variable having Gaussian PDF with $\mu = 10$ (mean) and standard deviation $\sigma = 2.5$. What is the probability that number of outages will be between 5 and 20 ? $\text{erf}(4) = 0.4999$
 $\text{erf}(2) = 0.477$. [4]

S.E. (Elex. & E.&TC) (First Sem.) EXAMINATION, 2008**SEMICONDUCTOR DEVICE AND CIRCUIT****(2003 COURSE)****Time : Three Hours****Maximum Marks : 100**

N.B. :— (i) Answers to the two Sections should be written in separate answer-books.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Use of electronic pocket calculator is allowed.

(v) Assume suitable data, if necessary.

SECTION I

1. (a) State and explain law of mass action. [4]

(b) Define :

(i) Drift current

(ii) Diffusion current

(iii) Mobility. [6]

(c) Determine the conductivity and resistivity of an intrinsic sample of silicon at normal room temperature (i.e. 300 K). Assume electron mobility $\mu_n = 1350 \text{ cm}^2/(\text{V}\cdot\text{sec})$; hole mobility $\mu_p = 480 \text{ cm}^2/(\text{V}\cdot\text{sec})$, intrinsic concentration at 300 K $= 1.52 \times 10^{10}$ and charge of an electron or hole $= 1.6 \times 10^{-19}$ coulomb. [8]

Or

2. (a) An N-type semiconductor has a resistivity of $20 \times 10^{-2} \text{ ohm}\cdot\text{m}$. The mobility of the electrons through a separate experiment

was found to be $100 \times 10^{-4} \text{ m}^2 \text{ V}^{-1}\text{S}^{-1}$. Find the number of electron carriers per m^3 . [6]

(b) Explain features and application of GaAs semiconductor material. [6]

(c) Define a graded semiconductor. Explain why an electric field must exist in a graded semiconductor. Derive required expression. [6]

3. (a) An ideal germanium diode at a temperature of 120°C has a reverse saturation current of $30 \mu\text{A}$ at a temperature of 120°C . Find the dynamic resistance for a 0.2 V bias in (i) The forward direction, (ii) Reverse direction. [6]

(b) A series circuit consist of a forward biased diode and two resistors 330Ω and 470Ω as shown in Fig. 1. Find the value of current through the circuit. Assume diode to be real diode. [4]

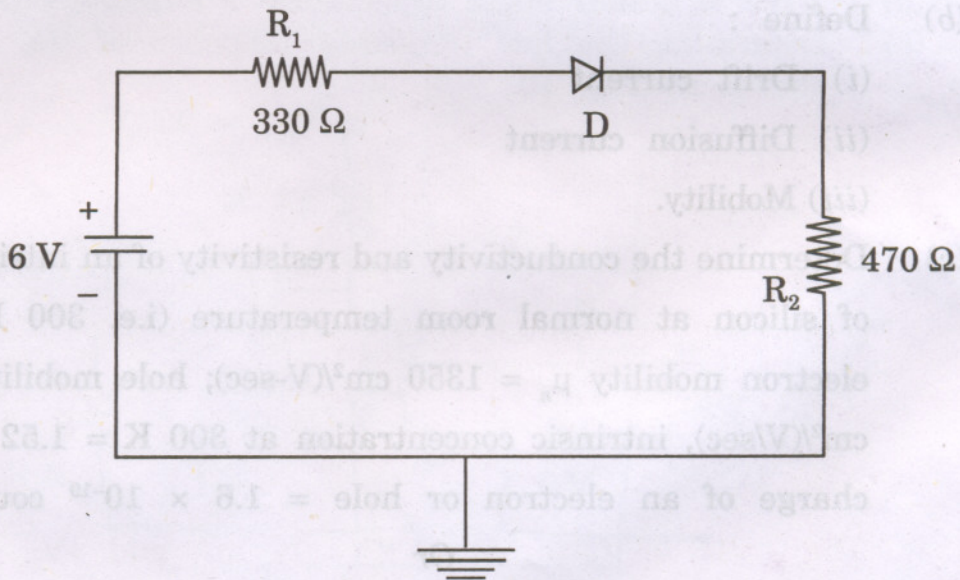


Fig. 1

- (c) Briefly explain the behaviour of junction in forward bias and reverse bias mode for PN diode and draw its volt-ampere characteristics. [6]

Or

4. (a) Explain construction and working of Tunnel diode and V-I characteristics for the same. State its applications. [6]
- (b) What is a Zener diode ? Draw the equivalent circuit of an ideal Zener in the breakdown region. [6]
- (c) A 6.2 V Zener diode has a resistance of $20\ \Omega$. What is the terminal voltage when the current is 25 mA ? [4]

5. (a) Define :
- (i) DC drain resistance (R_D)
 - (ii) AC drain resistance (r_d)
 - (iii) Transconductance (g_m)
 - (iv) Amplification factor (μ)
 - (v) The pinch-off voltage
 - (vi) Channel ohmic region
 - (vii) I_{DSS}
 - (viii) I_{GSS} [8]
- (b) The JFET operating with $I_D = 12\text{ mA}$ and $|V_{DS}| = 6\text{ V}$. If $|V_P| = 3\text{ V}$ and $I_{DSS} = 20\text{ mA}$. [8]

Specify the values of V_{GS} , V_{SS} , R_S and R_G for Fig. 2

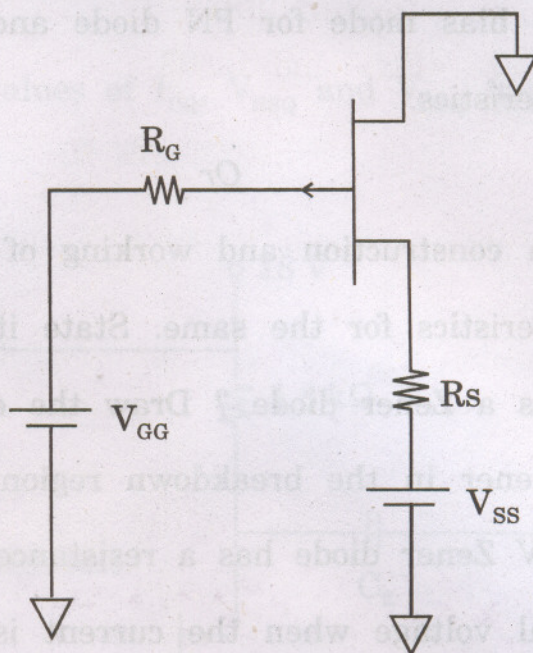


Fig. 2

Or

6. (a) Determine the following for the network shown in Fig. 3
 (i) V_D , (ii) V_S , (iii) V_{DS} , (iv) V_{DG} , (v) I_D and V_{GS} . [8]

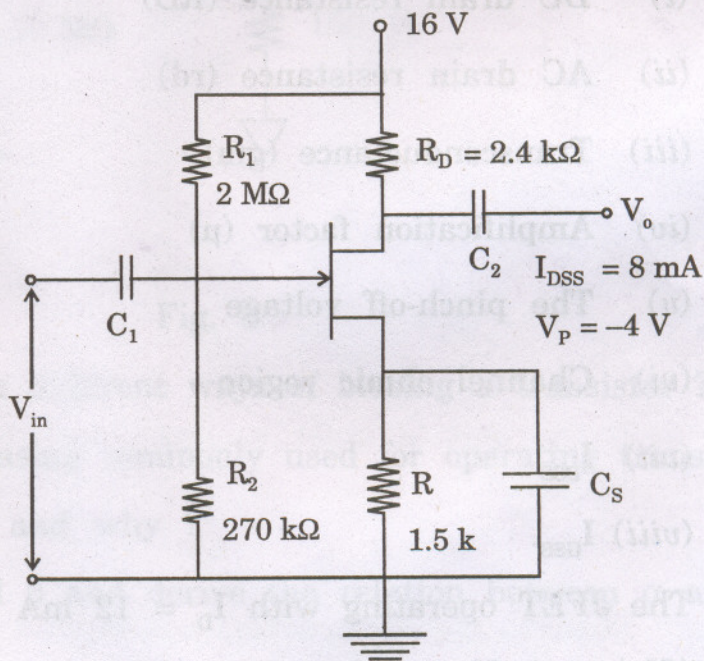


Fig. 3

- (b) What is meant by thermal runaway ? Why thermal runaway will not occur in JFET ? [4]
- (c) Compare JFET and BJT. [4]

SECTION II

7. (a) Draw construction of E-MOSFET and explain drain and transfer curve. [8]
- (b) Determine I_{DQ} and V_{DSQ} for E-MOSFET shown in Fig. 4. [6]

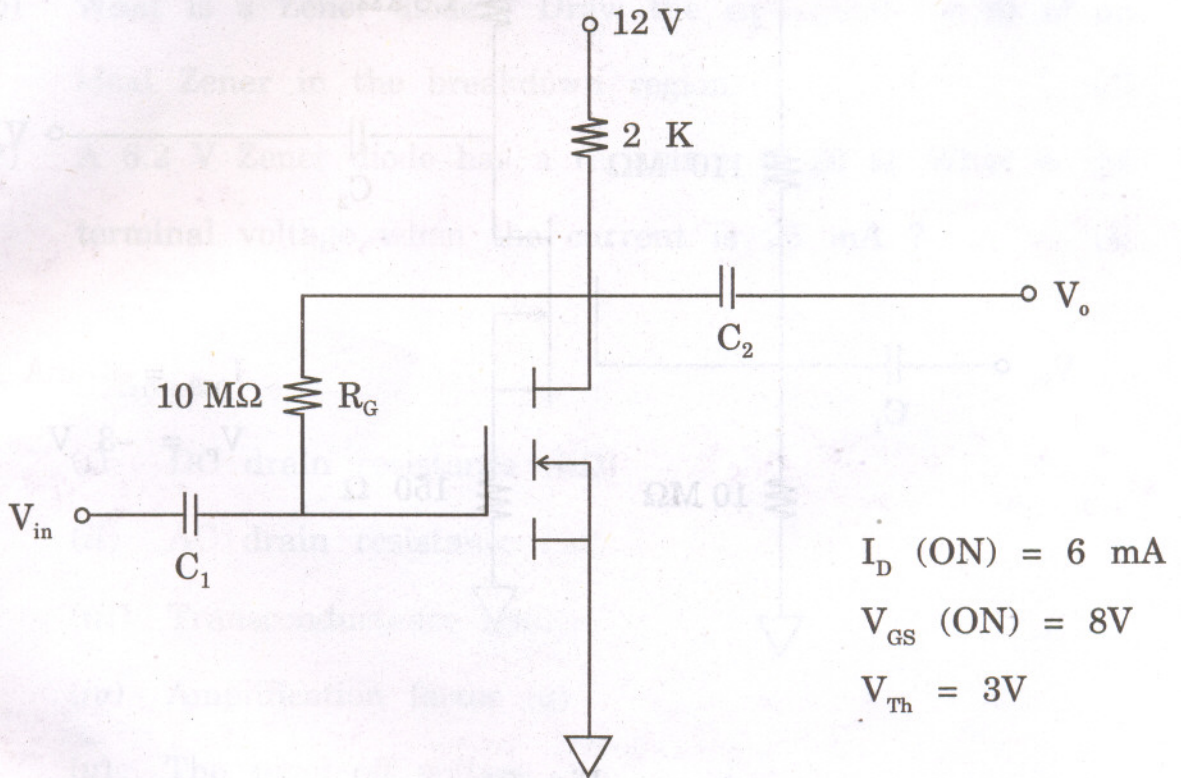


Fig. 4

- (c) Bring out a neat comparison between a JFET and a MOSFET. [4]

Or

8. (a) Describe the construction and explain the operation of depletion type MOSFET, also draw the static characteristics. [8]

- (b) While handling CMOS devices what precautions should be taken ? [4]
- (c) Find out the values of I_{DQ} , V_{GSQ} and V_{DSQ} for the ckt. shown in Fig. 5. [6]

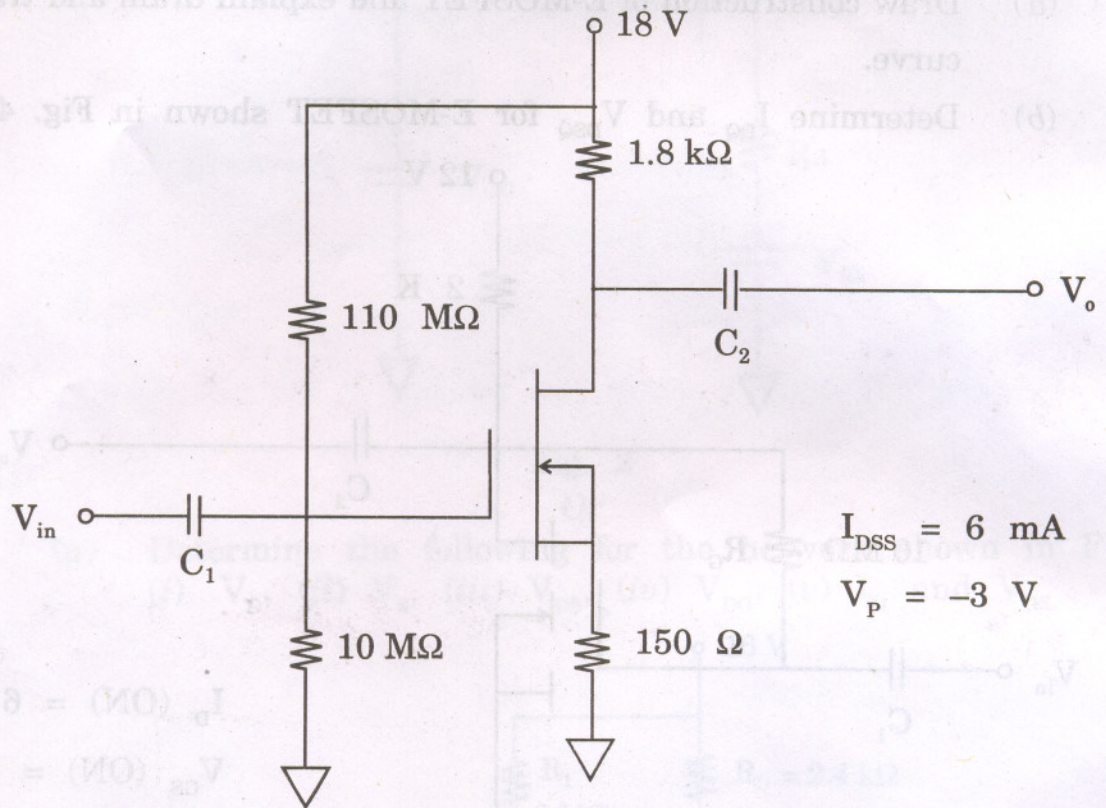


Fig. 5

9. (a) What are the different ways of biasing a transistor ? Which method of biasing commonly used for operating transistor as an amplifier and why ? [6]
- (b) Define α and β and derive the relation between α and β of a transistor. [4]

(c) For a single stage CE amplifier shown in Fig. 6 with

$$R_S = 1 \text{ k}\Omega, R_1 = 50 \text{ k}\Omega, R_2 = 2 \text{ k}\Omega$$

$$R_C = 2 \text{ k}\Omega \text{ and } R_L = 2 \text{ k}\Omega$$

$$h_{ie} = 1.1 \text{ K}$$

$$h_{oe} = 25 \text{ }\mu\text{A/V}$$

$$\text{and } h_{re} = 2.5 \times 10^{-4}$$

find out A_{is} , R_i , A_{VS} and R_o

$$A_{is} = \frac{I_L}{I_S}, \quad A_{VS} = \frac{V_o}{V_s}$$

[6]

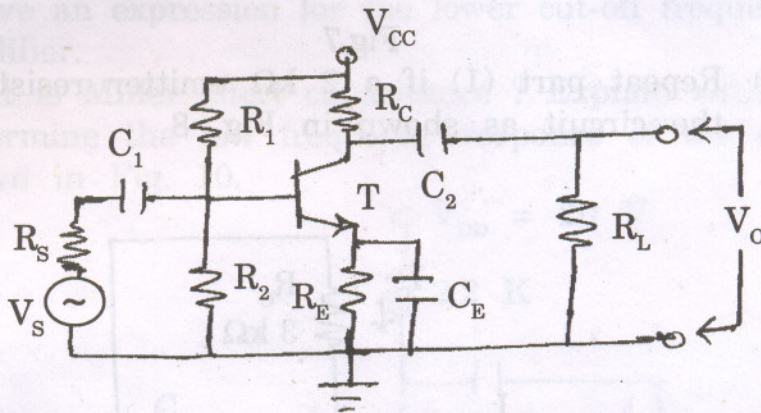


Fig. 6

Or

10. (a) Derive an expression for current gain, voltage gain, input impedance and output impedance of CE amplifier for small signal model.

[8]

- (b) (1) Find out transistor current in ckt. shown in Fig. 7, a silicon transistor with $\beta = 100$ and $I_{CO} = 20 \text{ nA}$ is under consideration and specify in which region transistor operates.

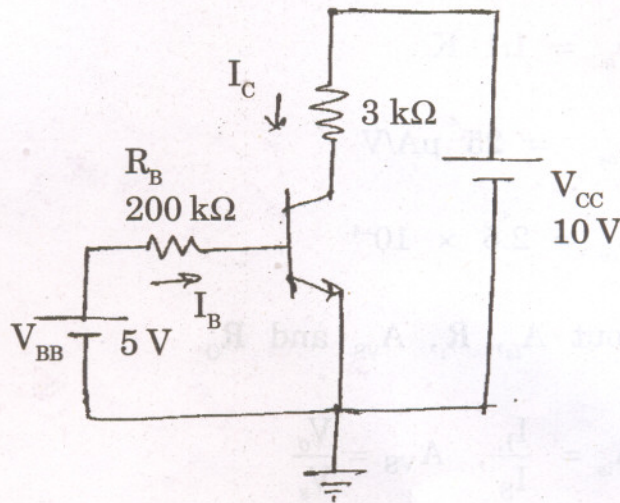


Fig.7

- (2) Repeat part (1) if a $2 \text{ k}\Omega$ emitter resistor is added to the circuit as shown in Fig. 8 [8]

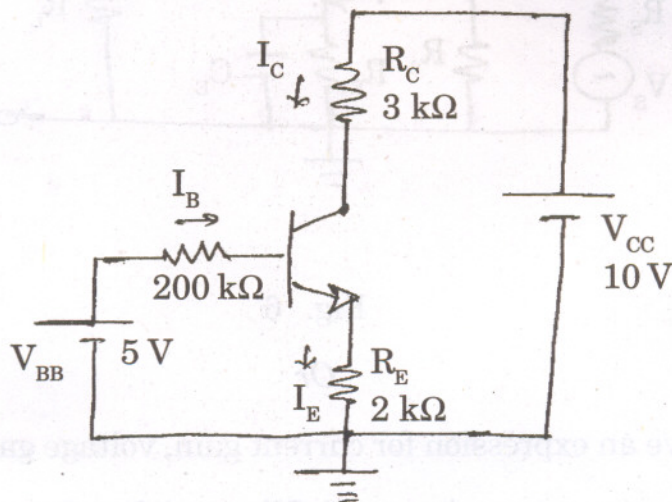


Fig. 8

11. (a) What are the factors that affect the low and high frequency response of BJT amplifier and FET amplifiers ? Justify with reasons. [6]
- (b) Determine the high frequency response of the amplifier ckt. shown in Fig. 9 [8]

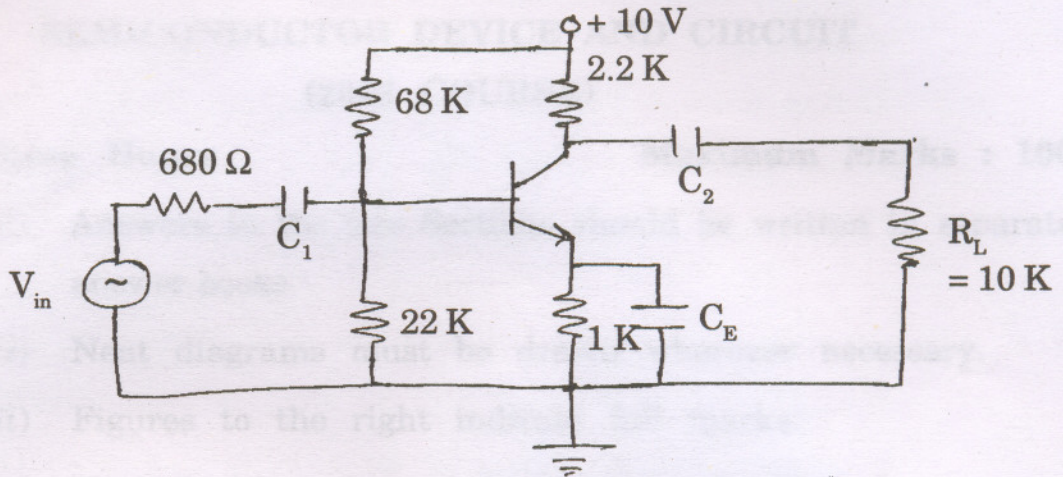


Fig. 9

- (c) What is decibel unit ? Why is it required ? [2]

Or

12. (a) Derive an expression for the lower cut-off frequency of a BJT amplifier. [6]
- (b) What is Miller effect capacitance ? Explain with example. [4]
- (c) Determine the low frequency response of the amplifier ckt. shown in Fig. 10. [6]

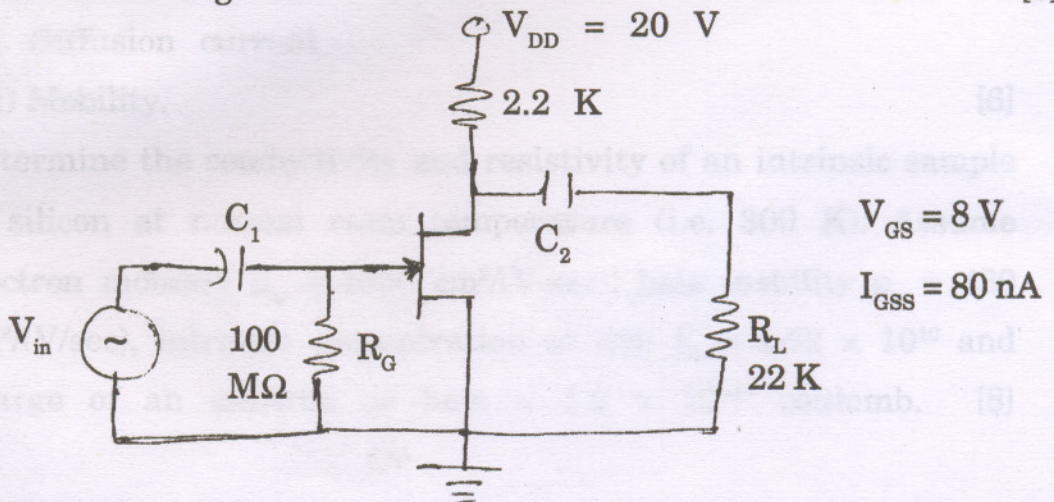


Fig. 10

[3462]-147**S.E. (Elex/ETC) (First Sem.) EXAMINATION, 2008****NETWORK THEORY****(2003 COURSE)****Time : Three Hours****Maximum Marks : 100****N.B. :—** (i) Answer any *three* questions from each Section.

(ii) Answers to the two Sections should be written in separate answer books.

(iii) Neat diagrams must be drawn wherever necessary.


(iv) Figures to the right indicate full marks.

(v) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.

(vi) Assume suitable data, if necessary.

SECTION I

1. (a) For the circuit shown in Fig. 1(a), find the branch currents I_1 , I_2 and I_3 and node voltages V_1 and V_2 . [6]

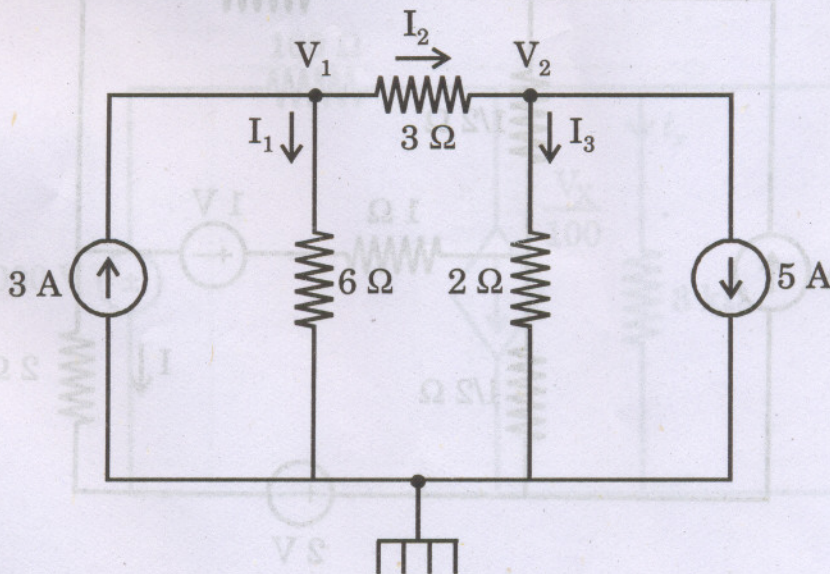**Fig. 1(a)**

- (b) For the network shown in Fig. 1(b), find $V_a(t)$ in the steady state if $V_1 = 2 \sin 2t$. [6]

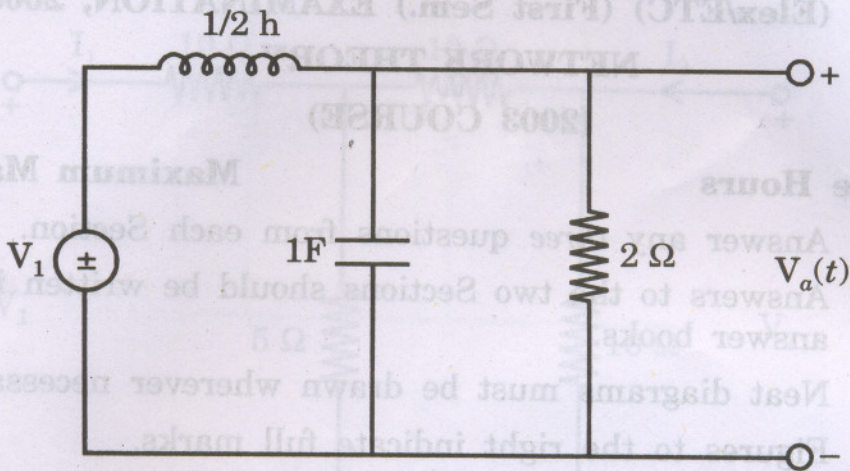


Fig. 1(b)

- (c) Using source shifting and source transformation, find current 'I' in the circuit shown in Fig. 1(c). [6]

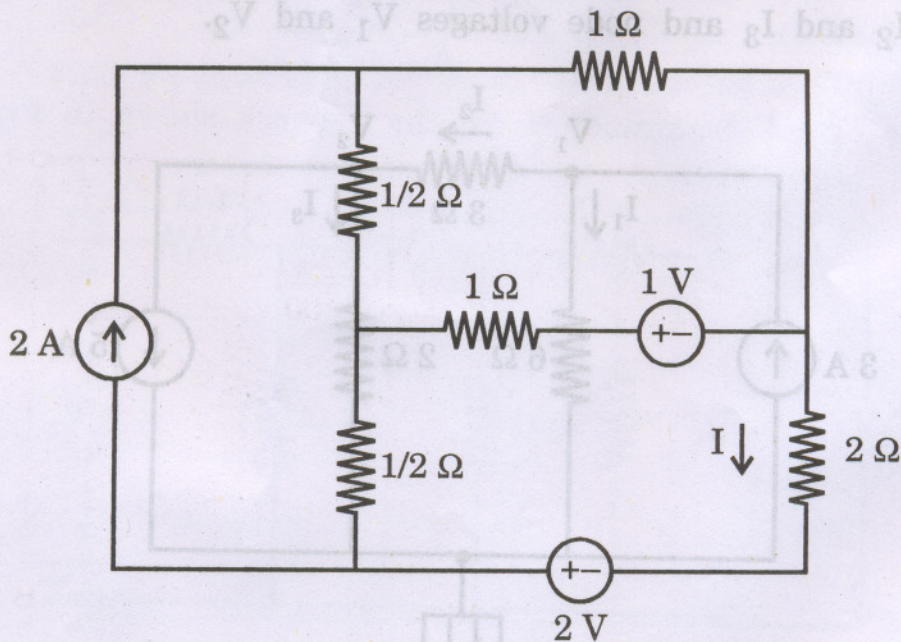


Fig. 1(c)

Or

2. (a) Determine the voltage V_1 in the circuit by using the superposition theorem. Refer Fig. 2(a). [6]

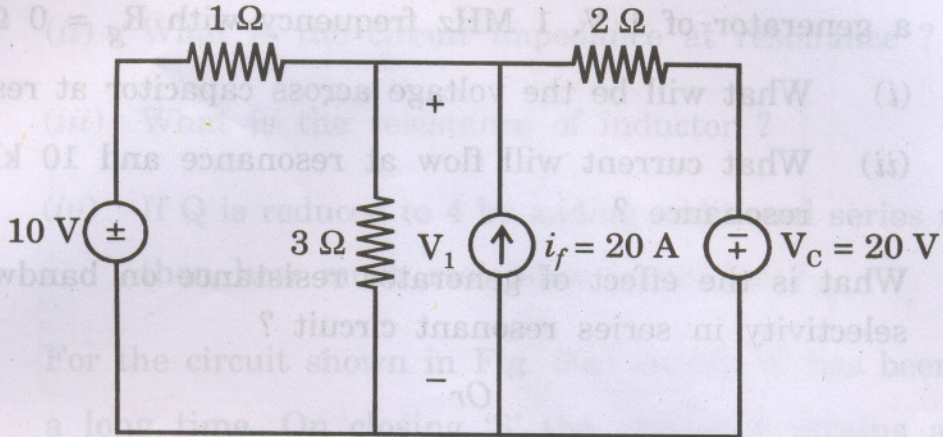


Fig. 2(a)

- (b) State and prove maximum power transfer theorem. [6]
 (c) Find Thevenin and Norton equivalent circuit across A-B in the circuit shown in Fig. 2(c). [6]

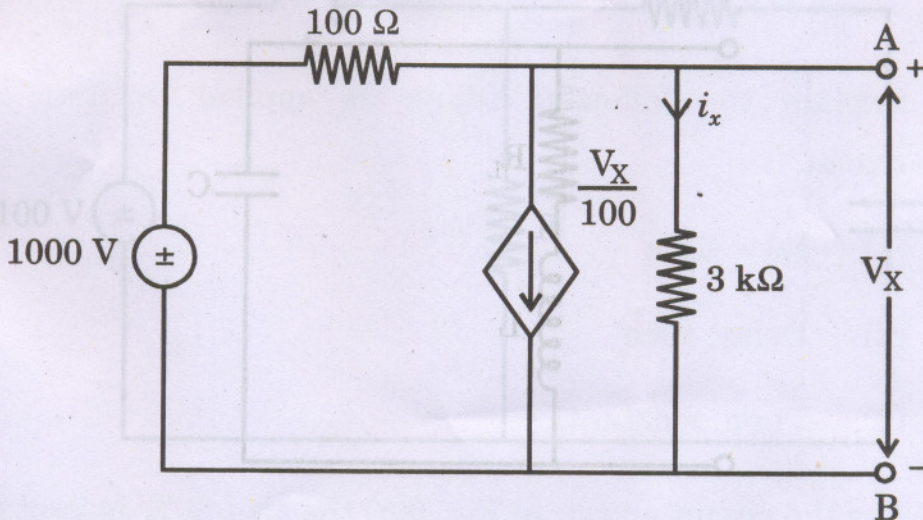


Fig. 2(c)

3. (a) Derive the expression for the impedance of a series resonating circuit in terms of Q_0 and δ . [6]
- (b) A series circuit of negligible resistance and coil of $120 \mu\text{H}$ with 18Ω resistance is resonated at 1 MHz . The circuit is driven by a generator of 1 V , 1 MHz frequency with $R_g = 0 \Omega$.
- (i) What will be the voltage across capacitor at resonance ?
- (ii) What current will flow at resonance and 10 kHz above resonance ? [4]
- (c) What is the effect of generator resistance on bandwidth and selectivity in series resonant circuit ? [6]

Or

4. (a) Give important property of series resonant circuit. Also give application of this circuit. [4]
- (b) In the circuit shown in Fig. 4(b) the inductance of 0.1 H having Q factor of 5 is in parallel with capacitor. Determine the value of capacitance and coil resistance at resonant frequency of 500 rad/sec . [6]

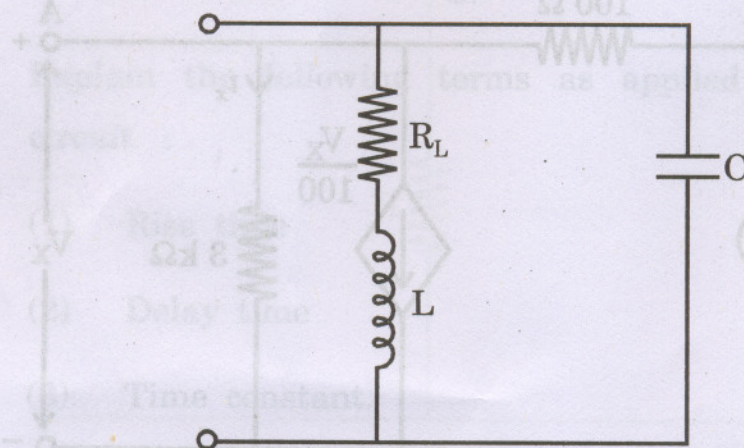


Fig. 4(b)

- (c) A parallel resonant circuit has a coil of $150 \mu\text{H}$ with Q of 60 and resonated at 1 MHz.
- Specify the value of required capacitor.
 - What is the circuit impedance at resonance ?
 - What is the resistance of inductor ?
 - If Q is reduced to 4 by adding additional series resistance, then how much resistance is needed ? [6]

5. (a) For the circuit shown in Fig. 5(a) switch 'S' has been open for a long time. On closing 'S' the capacitor attains a value of 80 V after 10 ms. The S/W has been closed for long time. When 'S' is opened $V_C = 90 \text{ V}$ after half a second. Calculate R and C values. [6]

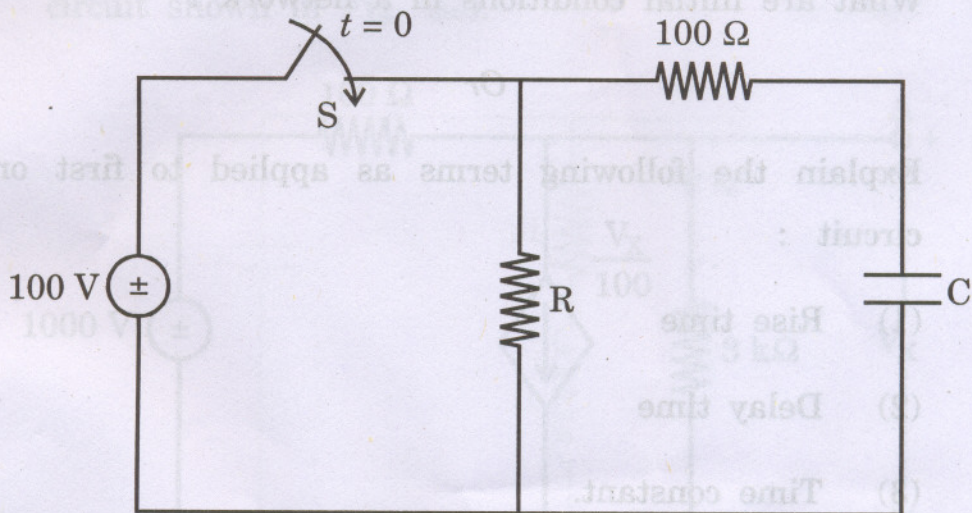


Fig. 5(a)

- (b) The circuit shown in Fig. 5(b) was in steady state with switch on position 1. At $t = 0$ it is moved to position 2. Find $i(t)$ using Laplace transform. [6]

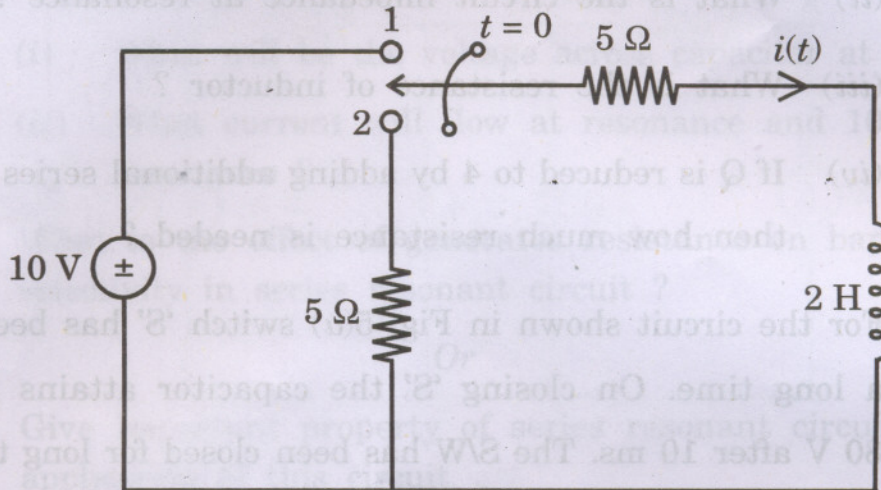


Fig. 5(b)

- (c) What are initial conditions in a network ? [4]

Or

6. (a) Explain the following terms as applied to first order R-C circuit :

- (1) Rise time
- (2) Delay time
- (3) Time constant.

[4]

- (b) For the circuit shown in Fig. 6(b) the switch 'S' is kept in position 1 for long period to establish steady state conditions. The switch

is then shifted to position 2 at $t = 0$. Find out the expression for current after switching the switch to position 2. [6]

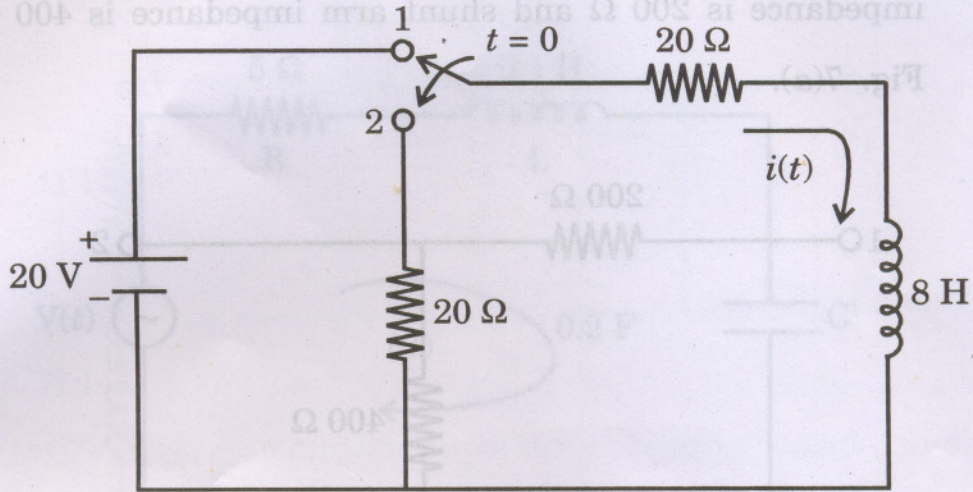


Fig. 6(b)

- (c) In the network shown in Fig. 6(c) the switch K is moved from position 'a' to 'b' at $t = 0$ (a steady state existing in position 'a' before $t = 0$). Solve for the current $i(t)$, using Laplace transform. [6]

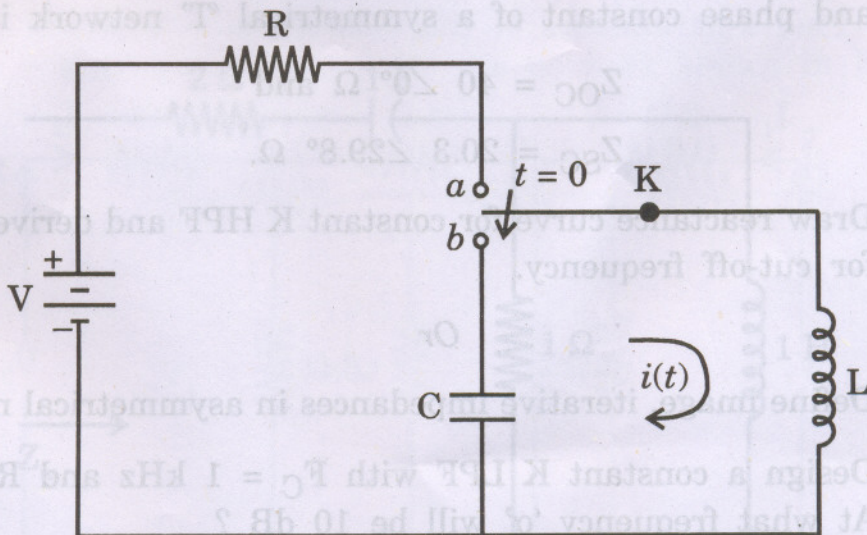


Fig. 6(c)

SECTION II

7. (a) Find an iterative impedance for L section whose series arm impedance is $200\ \Omega$ and shunt arm impedance is $400\ \Omega$. Refer Fig. 7(a). [6]

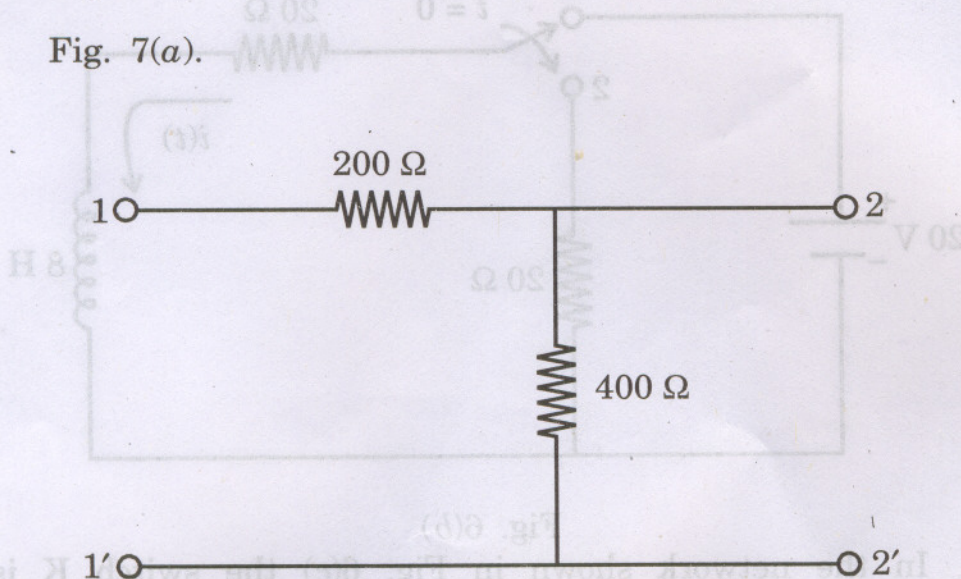


Fig. 7(a)

- (b) Calculate the characteristic impedance, an attenuation constant and phase constant of a symmetrical 'T' network if,

$$Z_{OC} = 40 \angle 0^\circ\ \Omega \text{ and}$$

$$Z_{SC} = 20.3 \angle 29.8^\circ\ \Omega. \quad [6]$$

- (c) Draw reactance curve for constant K HPF and derive expression for cut-off frequency. [4]

Or

8. (a) Define image, iterative impedances in asymmetrical network. [4]
- (b) Design a constant K LPF with $F_C = 1\ \text{kHz}$ and $R_0 = 600\ \Omega$. At what frequency ' α ' will be 10 dB? [6]
- (c) Design π type attenuator to provide attenuation of 10 dB and working into characteristic impedance of $600\ \Omega$. [6]

9. (a) State the necessary condition for driving point functions. [4]
- (b) For the circuit shown in Fig. 9(b), find the driving point impedance and driving point admittance. [6]

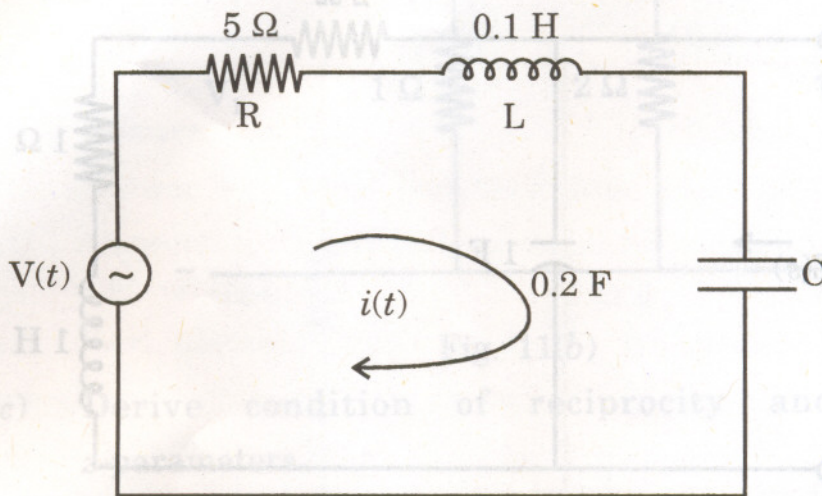


Fig. 9(b)

- (c) Find input impedance $Z_{\text{in}}(s)$ and plot its poles and zeros for the circuit shown in Fig. 9(c). [6]

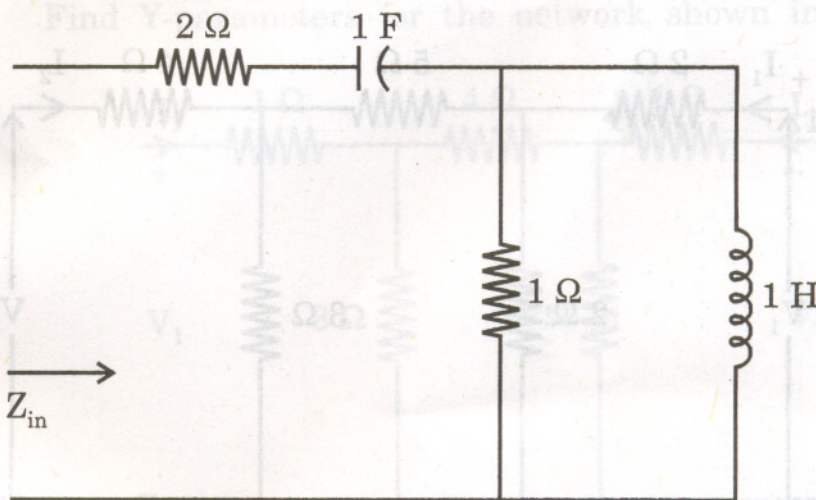


Fig. 9(c)

- Or
10. (a) Explain significance of poles and zeros. [4]
 (b) Find driving point impedance and driving point admittance for the circuit shown in Fig. 10(b). [6]

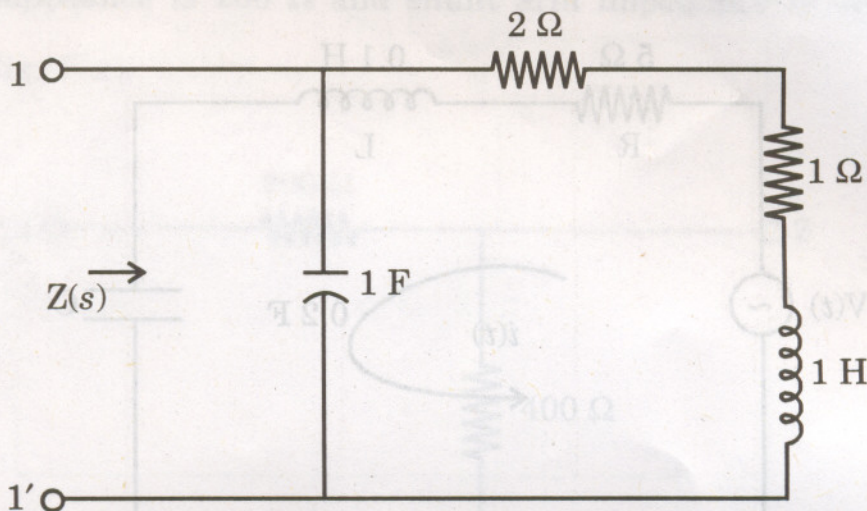


Fig. 10(b)

- (c) Draw pole zero plot for following function :

$$H(s) = \frac{s^2 + 4}{s^2 + 6s + 4}. \quad [6]$$

11. (a) Find z -parameters of the network shown in Fig. 11(a). [6]

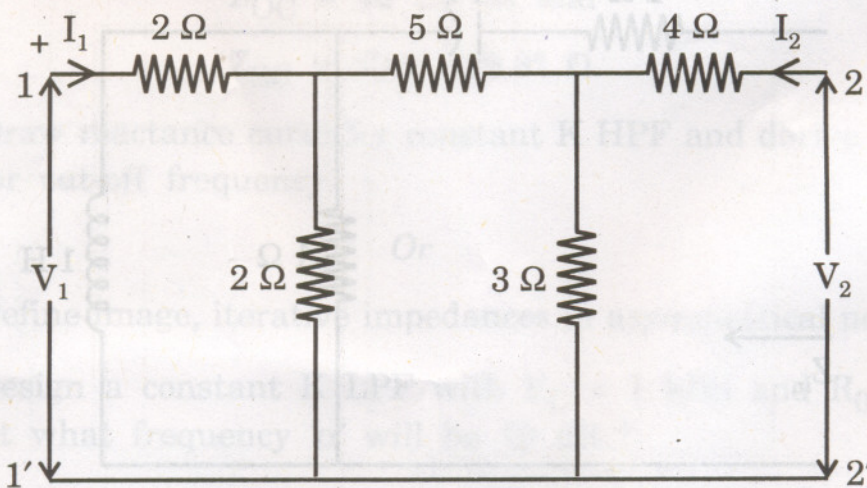


Fig. 11(a)

- (b) Find h -parameters for the network shown in Fig. 11(b). [6]

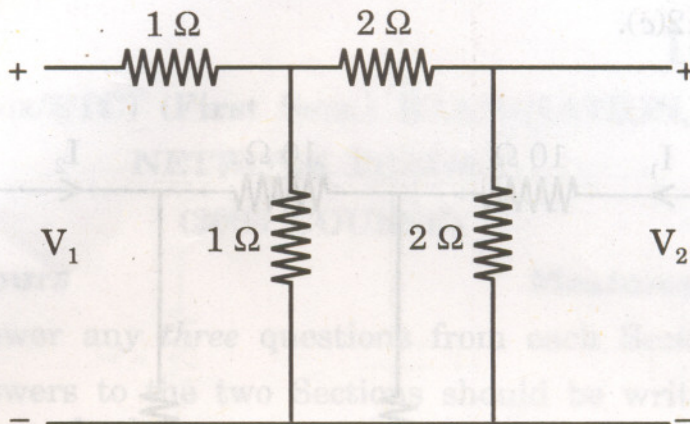


Fig. 11(b)

- (c) Derive condition of reciprocity and symmetry for z -parameters. [6]

Or

12. (a) State whether the following function is suitable for driving point function analysis :

$$Z(s) = \frac{5(4s^3 + 2s^2 + s + 2)}{s^4 + 3s^3 + 4s}. \quad [4]$$

- (b) Find Y -parameters for the network shown in Fig. 12(b). [8]

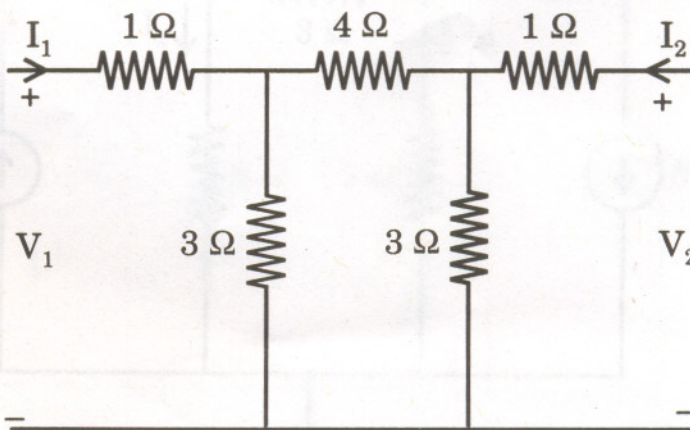


Fig. 12(b)

(c) Determine transmission parameter of the network shown in Fig. 12(c). [6]

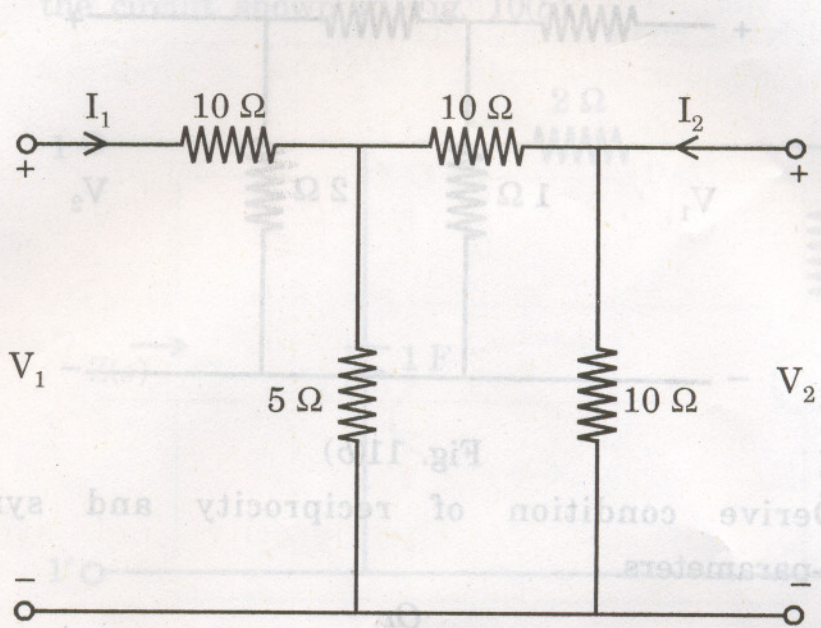


Fig. 12(c)

S.E. (E&TC) (First Semester) EXAMINATION, 2008

CONTROL SYSTEMS

(2003 COURSE)

Time : Three Hours

Maximum Marks : 100

N.B. :— (i) Answers to the two Sections should be written in separate answer-books.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.

(v) Assume suitable data, if necessary.

SECTION I

1. (a) Define the following with an example for each :

(1) Closed loop system;

(2) Non-linear system;

(3) Feed forward system;

(4) Linear system.

[8]

(b) Reduce the following block diagram and obtain the Transfer

function $\frac{C(s)}{R(s)}$ Fig. 1.

[8]

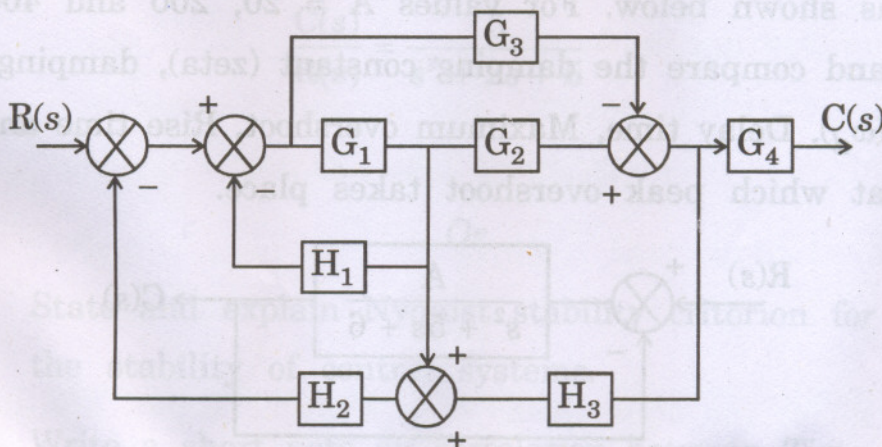


Fig. 1

P.T.O.

Or

2. (a) Compare and contrast with suitable example :
 (1) Open loop system and closed loop system;
 (2) Feedback control system and Feed forward control system. [8]
 (b) Obtain the transfer function for the following SFG using Mason's gain formula Fig. 2. [8]

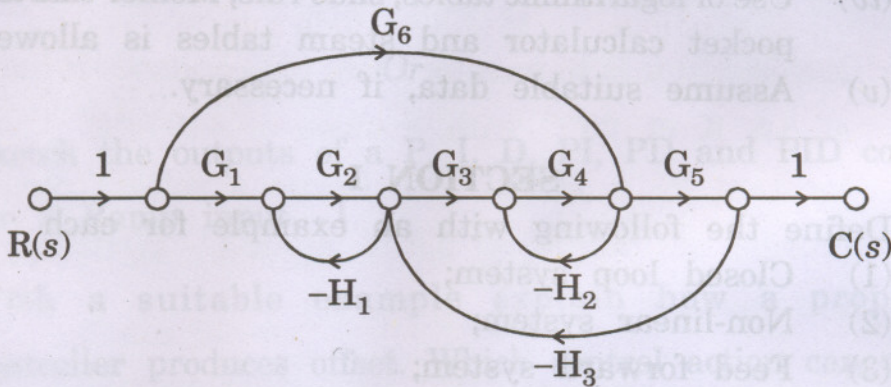


Fig. 2

3. (a) The block diagram (Fig. 3) of a unity feedback control system is shown below. For values $A = 20, 200$ and 400 find out and compare the damping constant (ζ), damping frequency (ω_d). Delay time, Maximum overshoot, Rise time and the time at which peak overshoot takes place. [12]

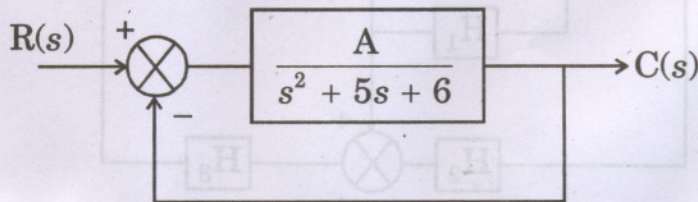


Fig. 3

- (b) Explain Routh-Hurwitz criterion for stability. [4]

Or

4. (a) Determine the range of K so that the system with the following characteristic equation will be stable :

$$s(s^2 + 2s + 3)(s + 2) + K = 0. \quad [4]$$

- (b) Sketch the root locus for the system having :

$$G(s) H(s) = \frac{K}{s(s + 3)(s + 5)} \quad K > 0.$$

Comment on the stability. [12]

5. (a) A feedback control system has :

$$G(s) H(s) = \frac{100(s + 3)}{s(s + 1)(s + 5)}.$$

Draw the Bode plot and comment on stability. [12]

- (b) Determine the Resonant peak (M_r) and Resonant frequency (ω_r) for the system whose transfer function is :

$$\frac{C(s)}{R(s)} = \frac{5}{s^2 + 2s + 5}. \quad [6]$$

Or

6. (a) State and explain Nyquist stability criterion for determining the stability of control systems. [6]
- (b) Write a short note on correlation between Time Domain and Frequency Domain specifications. [4]

- (c) A feedback control system has the open loop transfer function :

$$G(s) H(s) = \frac{100}{s(s+5)}.$$

Draw the Nyquist plot and determine the closed loop stability. [8]

SECTION II

7. (a) Define the following :

(1) State

(2) State variables

(3) State vector

(4) State space. [4]

- (b) What are the advantages of state space techniques over transfer function approach ? [4]

- (c) Obtain the State Space Model for the system given below having overall transfer function :

$$\frac{Y(s)}{U(s)} = \frac{3s + 4}{s^2 + 5s + 6}. \quad [8]$$

Or

8. (a) Explain the state model of a Multiple Input, Multiple output control system with a block diagram. [4]

(b) State the properties of State Transition Matrix. [4]

(c) Obtain the State Transition Matrix for the system :

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -2 & 3 \\ 0 & -3 \end{bmatrix} x(t). \quad [8]$$

9. (a) What is meant by the Gauge Factor of a strain gauge ? Derive an expression for the same. [4]

(b) A thermistor is to monitor room temperature. It has a resistance of 3.5 K at 20°C with a slope of $-10\%/^{\circ}\text{C}$. The dissipation constant $P_D = 30 \text{ mW}/^{\circ}\text{C}$. Devise a voltage divider circuit to provide an output of 5.0 V at 20°C. What is the effect of self heating ? [4]

(c) Sketch a Piezo-electric type accelerometer. Where is it used ? [4]

Or

10. (a) Sensor resistance changes linearly from 100 Ω to 180 Ω as temperature changes from 20°C to 120°C. Find the equation relating resistance and temperature. [4]

(b) With a neat sketch explain the capacitance type level measurement technique. [8]

(c) State the advantages of semiconductor strain gauges over metallic strain gauges. [4]

11. (a) A PI controller has $K_P = 4.5$ and $K_I = 7 \text{ sec}^{-1}$. Find the controller output for an error $E_P = 3 \sin (\pi t)$. [4]
- (b) How do you interpret the NO and NC symbols in Relay ladder logic and PLC ladder logic ? [4]
- (c) Draw the PLC ladder diagram for a Bottle Filling System. Consider all sensors as direct inputs to the PLC. [10]

Or

12. (a) Sketch the outputs of a P, I, D, PI, PD and PID controllers for a Ramp input. [6]
- (b) With a suitable example explain how a proportional controller produces offset. Which control action can eliminate this ? [4]
- (c) With a block diagram explain the working of a PLC. What are its advantages over control relays ? [8]

S.E. (E & TC) (First Sem.) EXAMINATION, 2008**DIGITAL SYSTEMS****(2003 COURSE)****Time : Three Hours****Maximum Marks : 100****N.B. :—** (i) Answer any *three* questions from each Section.

(ii) Answers to the two Sections should be written in separate Answer-books.

(iii) Neat diagrams must be drawn wherever necessary.

(iv) Figures to the right indicate full marks.

(v) Assume suitable data, if necessary.

(vi) Solve question Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6 from Section I and Q. 7 or Q. 8, Q. 9 or Q. 10, Q. 11 or Q. 12 from Section II.

SECTION I

1. (a) With neat circuit diagram explain the working of 2 i/p NAND gate (TTL). [6]
- (b) Describe the characteristics of CMOS family and explain the operation of CMOS inverter. [6]
- (c) Explain with a neat circuit diagram interfacing of TTL and CMOS gates. [6]

Or

2. (a) Define and explain :

- (1) Fan out

(2) Wired ANDing

(3) Figure of merit

(4) Power dissipation

(5) Propagation delay. [10]

(b) Draw and explain the working of 2 i/p CMOS NOR gate. What do you mean by current sinking and current sourcing in TTL gates ? [8]

3. (a) Minimize the function using K map and implement using NOR gates only : [8]

$$f(A, B, C, D) = \Pi M(0, 1, 3, 4, 5, 7, 9)$$

(b) Implement EX-OR gate using NOR gates. [4]

(c) Represent (-15) using :

(1) Sign magnitude form

(2) 1's complement form

(3) 2's complement form. [4]

Or

4. (a) Design and implement a 4-bit binary to gray code converter using discrete gates. [8]

(b) Convert :

(1) $(95)_{10} = ()_8 = ()_{16}$

(2) $(1100)_2 = ()_{\text{gray}}$

(3) $(5)_{10} = ()_7$ segment code (common anode) [4]

- (c) Draw the circuit diagram and explain the working for a multiplexed common cathode display using IC 7447. [4]
5. (a) Implement the following function using 4 : 1 multiplexers :

$$f(A, B, C, D) = \sum m(1, 3, 6, 8, 10, 11, 15)$$
 [8]
- (b) A combinational circuit is defined by the function : [8]

$$F_1(A, B, C) = \sum m(1, 3, 5)$$

$$F_2(A, B, C) = \sum m(2, 4, 5)$$

 Implement a circuit with PLA.

Or

6. (a) Design and implement a full adder circuit using a 3 : 8 decoder. [8]
- (b) Compare PLA and PAL. [4]
- (c) Design 9's complement or circuit using 4-bit adder 7483. [4]

SECTION II

7. (a) Design and implement a 3-bit up/down asynchronous counter. [6]
- (b) Convert a J-K f/f into D f/f and T f/f. [8]
- (c) Design Johnson's counter using 2-bit shift register. Draw the waveforms. [4]

Or

8. (a) Design a mod 25 counter using IC 7490. [6]
- (b) Draw the logical diagram of 4-bit bidirectional shift register. Explain shift left and shift right operation. [8]

(c) Explain race around condition. How can this condition be eliminated ? [4]

9. (a) Design a sequence detector for the following sequence : [8]

— — 110 — —

(b) Design mod 9 counter using IC 74191. [4]

(c) Distinguish between Mealy and Moore machines. [4]

Or

10. (a) Design a sequence generator using shift register to generate the following sequence : [8]

— — 1101011 — —

(b) Explain :

(1) State table

(2) State diagram

(3) Rules for state reduction. [6]

(c) Give the advantages and disadvantages of synchronous counters over asynchronous counters. [2]

11. (a) Explain with block diagram successive approximation A/D converter. [8]

(b) Explain various types of ROMs and their applications. [8]

12. (a) Explain the following terms w.r.t. DAC :

(1) Resolution

(2) Linearity

(3) Accuracy

(4) Setting time.

[8]

(b) Explain the characteristics of the following memories :

(1) NURAM

(2) SDRAM

(3) DRAM

(4) RAM.

[8]

SECTION I

(a) With neat circuit diagram explain the working of 2 V_p NAND gate (TTL).

[6]

(b) Describe the characteristics of CMOS family and explain the operation of CMOS inverter.

[6]

(c) Explain with a neat circuit diagram interfacing of TTL and CMOS gates.

[6]

Or

(a) Define and explain :

(i) Fan out