

S.E. (Computer Engg.) (I Sem.) EXAMINATION, 2009**ELECTRONICS DEVICES AND CIRCUITS****(2003 COURSE)****Time : Three Hours****Maximum Marks : 100**

N.B. :— (i) Answer Question Nos. 1 or 2, 3 or 4 and 5 or 6 from Section I and Question Nos. 7 or 8, 9 or 10 and 11 or 12 from Section II.

(ii) Answers to the two Sections should be written in separate answer-books.

(iii) Neat diagrams must be drawn wherever necessary.

(iv) Figures to the right indicate full marks.

(v) Assume suitable data, if necessary.

SECTION I

1. (a) Explain : [8]

(i) Thermistor bias compensation

(ii) Diode bias compensation.

(b) State *three* stability factors S , S' , S'' for biasing circuits and derive equations of S , S' and S'' for self bias circuit. [10]

Or

2. (a) Compare fixed bias, collector to base bias and self bias circuits with respect to : [8]

(i) Circuit diagram

(ii) Biasing resistances and its location

(iii) Pretence of negative feedback

(iv) Equation for stability factors.

- (b) A silicon transistor operated with self bias gives $V_{CEQ} = 5 \text{ V}$, $I_{CQ} = 2 \text{ mA}$ for $V_{CC} = 10 \text{ V}$ and $R_C = 2 \text{ k}\Omega$. If β for transistor is 50, $V_{BE} = 0.7 \text{ V}$ and stability factor S is 5, calculate the values of biasing resistors R_1 , R_2 and R_E . [10]
3. (a) Draw the hybrid model for typical common emitter amplifier without R_E and derive expression for A_i , R_i , A_v and R_o . [10]
- (b) Write a short note on Bootstrapped emitter follower. [6]

Or

4. (a) A common base amplifier, as shown in Fig. 1 has the following components :
- $R_S = 600 \Omega$, $R_C = 5.6 \text{ k}\Omega$, $R_E = 5.6 \text{ k}\Omega$, $R_L = 39 \text{ k}\Omega$. The transistor parameters are $h_{ie} = 85$ and $h_{oe} = 2 \mu\text{A/V}$. Calculate R'_i , R'_o , A_v and $A_{vS} = V_o/V_S$. [10]

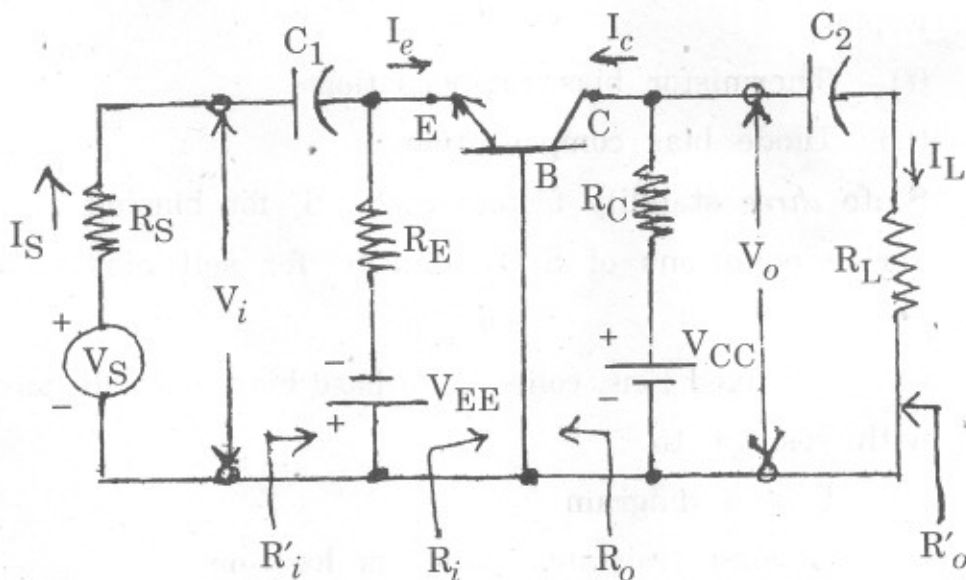


Fig. 1

- (b) Write a short note on Miller's theorem. [6]

5. (a) An ideal class B complementary symmetry push-pull amplifier operates with $V_{CC} = 12\text{ V}$ and $R_L = 5$. If input is sinusoidal, calculate : [10]
- Maximum power output
 - Power dissipation in both transistor
 - Power dissipation in each transistor
 - Conversion efficiency for maximum power output.
- (b) Explain various types of coupling in multistage amplifiers. [6]

Or

6. (a) For the circuit shown in Fig. 2, assume both transistors to be identical with $h_{ie} = 1.1\text{ k}\Omega$, $h_{fe} = 50$ and negligible h_{re} and h_{oe} . Calculate R_i , R_o , A_v and A_{vs} . [10]

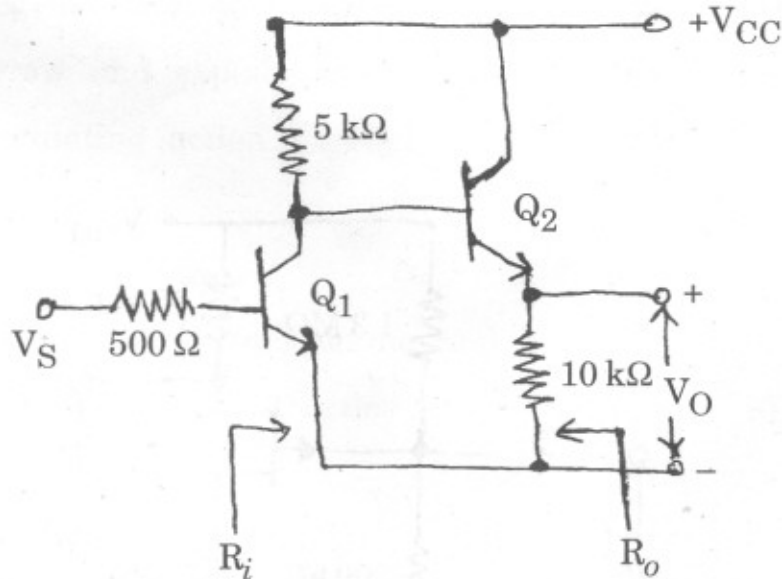


Fig. 2

- (b) Explain harmonic and cross over distortion in large signal amplifiers. [6]

SECTION II

7. (a) A p -channel FET has an $I_{DSS} = -12 \text{ mA}$, $V_P = 5 \text{ V}$, V_{GS} is 5.32 V . Calculate drain current, transconductance. [8]
- (b) With the help of neat diagram, explain the operation of n -channel JFET. Show the internal depletion regions and explain their shape. Also draw static o/p characteristic of JFET. [10]

Or

8. (a) What do you understand by 'pinch off voltages' and 'cut-off voltages' in JFET ? Draw and explain transfer characteristics of JFET. [8]
- (b) For the circuit shown in Fig. 3, p -channel JFET has $V_P = 4 \text{ V}$, $I_{DSS} = 4 \text{ mA}$. Calculate : [10]
- (1) I_{DSQ}
 - (2) V_{GSQ}
 - (3) V_{DSQ}

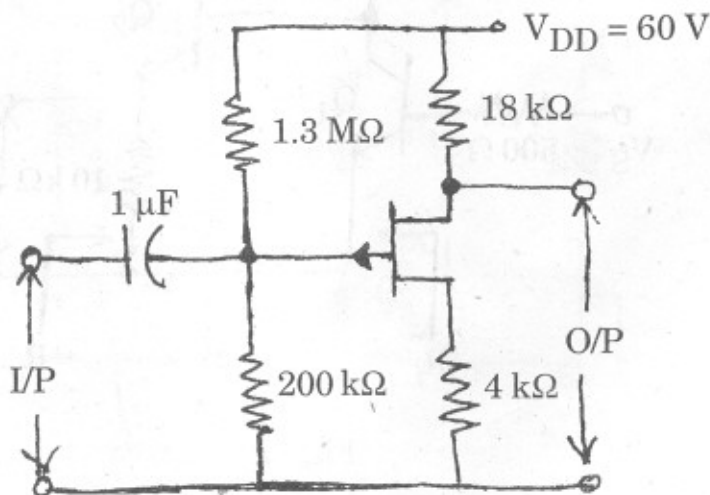


Fig. 3

9. (a) Draw block schematic of an Op-Amp and briefly explain function of each block. [8]
- (b) What is Schmitt trigger ? What are threshold levels and hysteresis ? Explain with neat circuit diagram. [8]

Or

10. (a) How can Op-Amp be used as an inverting amplifier ? Derive an expression for its output and gain. [8]
- (b) Draw and explain triangular waveform generator using Op-Amp 741. [8]
11. (a) Draw and explain *two* transistor model of SCR. Also explain regenerative action in SCR operation. [8]
- (b) Draw and explain stepdown (Buck) switching regulator with regulating action. [8]

Or

12. (a) Draw and explain online and line interactive UPS. [8]
- (b) Explain the construction and working of TRIAC. Sketch its V-I characteristic. [8]