

S.E. (Information Technology) (I Sem.) EXAMINATION, 2009**DIGITAL ELECTRONICS AND MICROPROCESSOR****(2003 COURSE)****Time : Three Hours****Maximum Marks : 100**

- N.B. :—** (i) Answer Question Nos. 1 or 2, 3 or 4, and 5 or 6 from Section I and Question Nos. 7 or 8, 9 or 10 and 11 or 12 from Section II.
- (ii) Answers to the two Sections should be written in separate answer-books.
- (iii) Neat diagrams must be drawn wherever necessary.
- (iv) Figures to the right indicate full marks.
- (v) Assume suitable data, if necessary.

SECTION I

1. (a) Perform the following arithmetic's using 2's complement method. (Show step by step process and comment on result) : [8]
- (i) $(8)_{10} - (6)_{10}$
- (ii) $(6)_{10} - (8)_{10}$
- (iii) $(-8)_{10} - (6)_{10}$
- (iv) $(8)_{10} - (-6)_{10}$
- (b) What is BCD and Excess 3 code ? State specific properties and applications of these codes. [6]
- (c) State representations used for representing negative numbers in binary and represent $(-8)_{10}$ using all these representations (Use 8 bit word length). [4]

Or

2. (a) Perform the following. (Show step by step process) : [8]
- (i) $(11101.101)_2 = ()_{10}$
 - (ii) $(126.77)_8 = ()_{10}$
 - (iii) $(7FE.6A)_{16} = ()_{10}$
 - (iv) $(12AB.CD)_{16} = ()_8$
- (b) Perform the following additions with base 8, 16 and 2 : [6]
- (i) $(2374)_8 + (6276)_8$
 - (ii) $(3FC5)_{16} + (7FAE)_{16}$
 - (iii) $(101101)_2 + (011001)_2$
- (c) What is gray code ? State applications of gray code and explain one of them. [4]

3. (a) Describe the difference between TTL and CMOS with respect to fan-out, power dissipation per gate, propagation delay and noise margin. [4]
- (b) What do you mean by open-collector TTL gate ? What is its advantage ? Explain with suitable circuit. [4]
- (c) A TTL gate is supposed to drive CMOS gates. What arrangement has to be made to work this interface satisfactorily ? Justify your answer with suitable circuit diagram. [8]

Or

4. (a) What is the difference between low power TTL and Schottky TTL ? [4]
- (b) Define the terms sourcing and sinking current with respect to CMOS family and give typical values for CMOS family. [4]
- (c) Explain wired logic using two CMOS inverters. [8]

5. (a) Simplify the following Boolean function using K map and realize the same : [6]

$$F(A, B, C, D) = \prod M(0, 4, 9, 15) \cdot d(2, 7, 13)$$

- (b) Design and draw the basic circuit of single digit BCD adder using IC 7483. Explain the logic to convert it into two digit BCD adder. [10]

Or

6. (a) Design a full subtractor circuit using 4 : 1 multiplexers and some logic gates. Explain your logic and optimization using truth table. [6]

- (b) Design BCD to 7-segment code decoder using logic gates. Assume common anode 7-segment LED's. [10]

SECTION II

7. (a) Define the following terms as applied to Flip-Flop : [4]

(i) Set-up time

(ii) Hold time

(iii) Propagation delay

(iv) Power dissipation.

- (b) How will you convert the basic SR Flip-Flop into J-K Flip-Flop? [6]

- (c) Draw and explain the internal architecture of IC 7490. Design and draw BCD MOD 12 counter with IC 7490 and draw the waveform for the same. [8]

Or

8. (a) What do you mean by synchronous and asynchronous sequential circuits ? State merits and demerits of both the circuits. [4]
- (b) With neat diagrams, explain the working of the Bidirectional shift register with shift right and shift left facility. [6]
- (c) Design a Mod-6 counter using J-K Flip-Flops. (Use excitation table) and draw timing diagrams and determine the duty cycle of the output of the most significant stage. [8]
9. (a) What are the advantages of the R-2R ladder DAC over the Weighted resistor type DAC ? [4]
- (b) What do you mean by sample and hold circuit ? How is it necessary in ADC ? [4]
- (c) With the help of suitable diagram, explain the basic operation of Dual slope ADC. [8]

Or

10. (a) State and explain Sampling theorem. [4]
- (b) Define the following parameters of DAC's : [4]
- (i) Settling time
 - (ii) Resolution
 - (iii) Monotonicity
 - (iv) Conversion time
- (c) Explain successive approximation technique of conversion of simple 8-bit ADC. [8]

11. (a) Explain the block diagram of 8255 PPI. Explain all of its operation modes with control word format in detail. [10]

(b) What is the difference between : [6]

(i) Memory mapped I/O and I/O mapped I/O

(ii) Polled I/O data transfer and interrupt driven I/O data transfer.

Or

12. (a) What are various addressing modes of 8085 microprocessor ? Explain all 8085 addressing modes with suitable instructions as an example. [10]

(b) State the syntax and mention operations carried out by 8085 microprocessor to execute the following instructions : [6]

(i) LHLD

(ii) DAA

(iii) CMP