

Total No. of Questions : 12]

[Total No. of Printed Pages : 4

[3561]-19

F. E. Examination - 2009

BASIC ELECTRONIC ENGINEERING

(2003 Course)

Time : 3 Hours]

[Max. Marks : 100

Instructions :

- (1) Answer **any three** question from each section.
- (2) Answer to the **two sections** should be written in **separate answer-books**.
- (3) Black figures to the right indicate full marks.
- (4) Neat diagrams must be drawn wherever necessary.
- (5) Use of electronic pocket calculator is allowed.
- (6) Assume suitable data, if necessary.

SECTION - I

- Q.1) (A) A Fullwave Bridge Rectifier is supplied from 230V, 50 Hz and uses a transformer of turns ratio 15:1. It uses load resistance of 50Ω . Calculate Load Voltage and Ripple Voltage. Assume Standard Value of Ripple Factor and Ideal Diodes; Transformer. [08]
- (B) Differentiate between zener Breakdown and Avalanche Breakdown. [04]
- (C) Explain different types of Biasing Circuits in a transistor with relevant circuit diagram. [06]

OR

- Q.2) (A) Write short notes : [06]
- (1) Photodiode
 - (2) Varactor Diode

(B) Give comparison of CE, CB, CC on the basis of : [04]
 A_i ; Phase difference between input and output
 R_i ; Configurationwise Applications

(C) Explain the effect of temperature on p-n junction. Determine the forward current for a Germanium Diode at room temperature (27°C) when the voltage across it is (1) 0.1V (2) 0.3V. Assume reverse saturation current of 1 nA. [08]

Q.3) (A) Calculate the Component Values in a zener Regulator to meet following specifications. [08]

$$V_o = 8V; V_z = 30V, I_L = 50mA$$

$$\text{Assume } I_{z(\min)} = 5mA \text{ and } P_z = 1W.$$

(B) Draw and explain the block diagram of Series Regulator. [04]

(C) What is D.C. Load Line ? Give its significance and derive its equation for CE Amplifier. [04]

OR

Q.4) (A) Draw and explain the block schematic of a regulated power supply. What are the advantages of IC Regulators over discrete Component Regulator Circuit. [08]

(B) For an amplifier the midband frequency gain is 50 and the lower half power frequency is 80Hz. Find out the gain of the amplifier at the lower half power frequency. [04]

(C) Explain the effect of Coupling; bypass and junctions capacitors on the frequency response of an amplifier. [04]

Q.5) (A) Simplify the following expression and implement it by using NAND gates only.

$$\bar{W} \times Y\bar{Z} + XY\bar{Z} + X\bar{Y}\bar{Z} + X\bar{Y}Z \quad [06]$$

(B) Design Half Adder circuit using K-map. [06]

(C) Explain Positive and Negative Logic in Digital Systems. [04]

OR

- Q.6) (A)** Prove the following using Boolean Algebraic Theorem. [08]
- (1) $\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC = AB + BC + CA$
 - (2) $AB + \bar{A}C + BC = AB + \bar{A}C$
- (B)** Design one bit comparator using K-map and realize it using basic gates. [06]
- (C)** List Universal Gates and Realize AND Operation using NOR. [02]

SECTION - II

- Q.7) (A)** Draw the circuit diagram of Non-inverting Summing Amplifier with three inputs and derive the equation of output voltage. [07]
- (B)** State and explain Barkhausen Criteria. [04]
- (C)** Give Ideal Values of following OP-Amp Parameters : [05]
- (1) A_v
 - (2) R_i
 - (3) CMRR
 - (4) B.W.
 - (5) Slew Rate

OR

- Q.8) (A)** Draw neat circuit diagram of Wien Bridge Oscillator. Calculate Frequency of oscillations if $R = 50 \text{ k}\Omega$ and $C = 0.001 \text{ }\mu\text{F}$. [06]
- (B)** List the four Topologies of Negative Feedback and give the effect on Input and Output Resistance in each case. [06]
- (C)** Draw and explain Voltage Follower using OP-Amp. [04]
- Q.9) (A)** What is Transducer ? Compare Active and Passive Transducer. Give example of each. [04]
- (B)** With the help of neat circuit diagram explain construction and Working of LVDT. [08]
- (C)** Compare three types of Temperature Transducers. [04]

OR

Q.10)(A) Explain following Characteristics of Transducer : [04]

- (1) Accuracy
- (2) Ruggedness
- (3) Linearity
- (4) Repeatability

(B) Write short notes :

- (1) Strain Guage
- (2) Piezo-electric Transducer
- (3) RTD

[12]

Q.11)(A) Explain the following Front Panel Controls of CRO : [08]

- (1) Trigger
- (2) Chop
- (3) Alternate
- (4) X-Y Position

(B) Draw neat circuit diagram of Square Wave Oscillator using IC 555 and Calculate the component values to generate frequency of 1 kHz with duty cycle of 80% (Assume $C = 0.001 \mu F$) [10]

OR

Q.12)(A) Explain with block diagram : [08]

- (1) Electronic Counter
- (2) Burglar Alarm

(B) Draw neat circuit diagram of Monosable Multivibrator and explain its operation with the help of Waveforms at Trigger, Timing Capacitor, Output Voltage. Give applications of this circuits. [10]