

P1480

[3764] - 244

B.E. (Electronics)

VLSI DESIGN

(2003 Course)

Time : 3 Hours]

[Max. Marks : 100

Instructions to the candidates:

- 1) Answer any 3 questions from each section.
- 2) Answers to the two sections should be written in separate books.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Figures to the right indicate full marks.
- 5) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.
- 6) Assume suitable data, if necessary.

**SECTION - I**

Q1) Using structural modeling draw schematic and write VHDL code of 16:1 Mux by 4:1 Mux (as a component). [16]

OR

- Q2) a) List different synthesizable VHDL statements. [4]  
b) Explain function and procedure with VHDL examples. [12]

Q3) Draw state diagram and write VHDL code for Traffic light control. [16]

OR

- Q4) a) What is metastability and synchronization. [6]  
b) Write VHDL code for Lift control. [10]

Q5) Draw detail block diagram and explain different sub-blocks of CPLD. [18]

OR

- Q6) a) Draw only the block diagram FPGA and explain difference between CPLD and FPGA. [12]  
b) Write specification of CPLD and FPGA. [6]

## SECTION - II

- Q7)** a) What is clock skew and Jitter? Explain different techniques of clock distribution. [12]  
b) Define Global and switch Box routing. [4]  
OR
- Q8)** a) Explain the classification of memory. [12]  
b) Define off chip connection. [4]
- Q9)** a) What is technology scaling? Explain different scaling techniques. [12]  
b) Explain what is body effect in MOSFET. [4]  
OR
- Q10)** a) Explain different power dissipation in CMOS Inverter, also define power delay product. [12]  
b) Draw schematic and explain Transmission Gate. [4]
- Q11)** a) What is the need of DFT? With schematic explain different faults. [12]  
b) Define controllability and observability. [6]  
OR
- Q12)** Write short notes on: [18]  
a) TAP Controller.  
b) BIST.  
c) JTAG.

