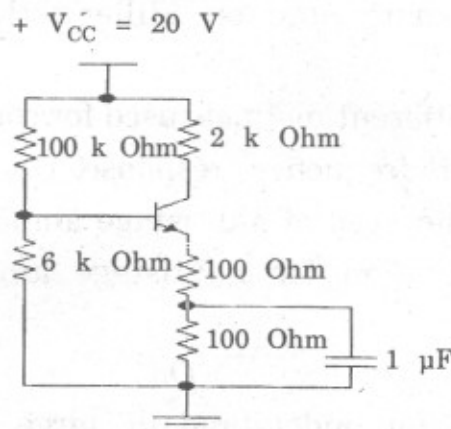


S.E. (Computer Engg.) (I Sem.) EXAMINATION, 2010**ELECTRONIC DEVICES AND CIRCUITS****(2003 COURSE)****Time : Three Hours****Maximum Marks : 100**

- N.B. :—** (i) Answer Question 1 or 2, 3 or 4 and 5 or 6 from Section I and Question 7 or 8, 9 or 10 and 11 or 12 from Section II.
- (ii) Answers to the two Sections should be written in separate answer-books.
- (iii) Neat diagrams must be drawn wherever necessary.
- (iv) Figures to the right indicate full marks.
- (v) Assume suitable data, if necessary.

SECTION I

1. (a) Define thermal resistance θ . State its unit. Derive equation of thermal stability in terms of thermal resistance. [8]
- (b) A voltage divider CE amplifier circuit as shown in Fig. 1, has $\beta = 50$, $V_{BE} = 0.7$ V. Find I_B , I_C , V_{CEQ} and S. [10]

**Fig. 1**

Or

2. (a) Compare fixed bias, collector to base bias and self bias circuits with respect to : [8]
- (i) Circuit diagram
 - (ii) Biasing resistances and its location
 - (iii) Negative feedback
 - (iv) Equation for stability factors.
- (b) Draw neat circuit diagram of a collector to base bias circuit and derive equations for I_C and V_{CE} . Explain with diagram, how temperature stability is insured in the above circuit. Also define s' and s'' . [10]
3. (a) Draw Approximate h -parameter model for common emitter transistor circuit with R_e . Also derive expression for R_i , R_o , A_v , A_{is} and A_i . [10]
- (b) Write a short note on Bootstrapped emitter follower circuit. [6]

Or

4. (a) Draw approximate h -parameter model for common emitter transistor circuit without R_e . Also derive expression for R_i , R_o , A_v , A_{vs} and A_i . [10]
- (b) Write a short note on Miller's theorem. [6]
5. (a) Explain different methods used for coupling multistage amplifiers with their frequency response. [8]
- (b) What is the need of multistage amplifier ? Explain the selection of configuration for multistage amplifier. [8]

Or

6. (a) What do you understand by large signal amplifier ? Classify them on the basis of Q point position and compare them. [8]

- (b) In three stage amplifier individual lower and upper cut-off frequency of an amplifier is 1 kHz to 100 kHz. Find bandwidth of cascaded amplifier. [8]

SECTION II

7. (a) What is meant by pinch-off voltage in FET ? Draw and explain drain and transfer characteristics for n -Channel FET. [8]
 (b) Why FET is called voltage operated device ? Also give comparison between FET and BJT. [4]
 (c) The p -channel FET has an $I_{DSS} = -10$ mA $V_P = 5$ V, V_{GS} is 5.32 V. Calculate drain current, transconductance. [4]

Or

8. (a) With the help of neat diagram, explain the operation of p -channel JFET. Also draw symbol of n -channel JFET, n -channel enhancement type MOSFET. [8]
 (b) For the circuit shown in Fig. 2, p -channel JFET has $V_P = 8$ V, $I_{DSS} = 5$ mA. Calculate : [8]
 (1) I_{DSQ}
 (2) V_{GSQ}
 (3) V_{DSQ}

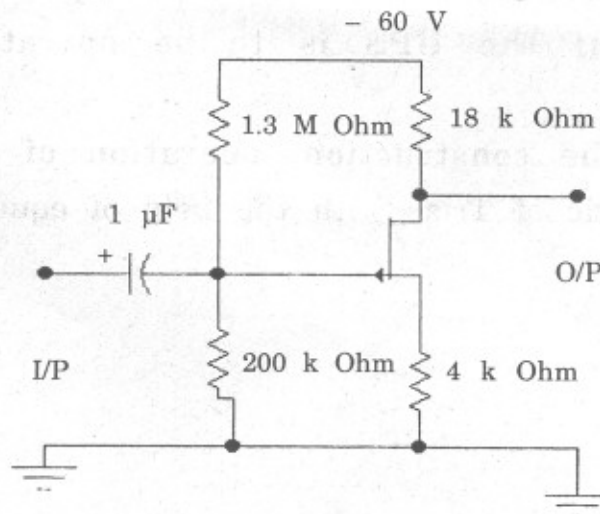


Fig. 2

9. (a) Draw the circuit diagram of emitter coupled differential amplifier and obtain its d.c. analysis. [8]
(b) What is Schmitt trigger ? What are threshold levels and hysteresis ? Explain with a neat circuit diagram. [8]

Or

10. (a) Draw and explain the circuit diagram of a zero crossing detector by using Op-Amp 741. Why Op-Amp can not be used in open configuration as an amplifier ? [8]
(b) Draw and explain integrator circuit using Op-Amp 741. Also draw input, output waveform. [8]
11. (a) Draw and explain two transistor model of SCR. Also explain regenerative action in SCR operation. [8]
(b) Compare SCR and TRIAC. Draw and explain step up (Boost) switching regulator with regulating action. [10]

Or

12. (a) Draw and explain on-line UPS. What operating changes are required if the UPS is to be operated as off-line UPS ? [8]
(b) Explain the construction, operation of Triac and V-I characteristic of Triac with the help of equivalent circuit of it. [10]