

Total No of Questions: [12]

SEAT NO. :

[Total No. of Pages : 3]

FE 2008 COURSE BASIC ELECTRICAL ENGINEERING

Time: 3 Hours

Max. Marks : 100

Instructions to the candidates:

- 1) *Answers to the two sections should be written in separate answer books.*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right side indicate full marks.*
- 4) *Use of Calculator is allowed.*
- 5) *Assume Suitable data if necessary*

SECTION I

- Q.1 (a) Define Resistance Temperature Coefficient (RTC). State its unit. With usual notations prove that 8M

$$\alpha_2 = \alpha_1 / [1 + \alpha_1 (t_2 - t_1)]$$

- (b) An electric pump lifts 12 m^3 of water per minute to a height of 15 meters. If its overall efficiency is 60 %, find the input power. If the pump is used for 4 hours a day find the cost of energy for the month of April. 8M

OR

- Q.2 (a) Define insulation resistance & Derive its expression for single core cable. 8M
- (b) With neat sketch explain construction & working of Lead Acid Battery. 8M
- Q.3 (a) State & Prove maximum power transfer theorem as applied to a d c resistive circuit. 8M
- (b) Obtain the equations to convert delta connected resistive network into equivalent star connected network. 8M

OR

- Q.4 (a) State & explain Kirchoff's laws as applied to a d c circuit. 8M
- (b) State & explain Superposition Theorem as applied to a d c circuit. 8M
- Q.5 (a) Compare Electric circuit with magnetic circuit stating clearly the similarities & dissimilarities. 8M
- (b) Define self inductance of a coil. & hence state the factors that affect its value. 4M
- (c) The length of an air cored solenoid is 1.7 m & area of cross section is 12 cm^2 . The number of turns of the coil is 1000. Calculate- 6M
- a) the self inductance b) the energy stored in the magnetic field when a current of 10 A flows through the coil.

OR

Total No of Questions: [12]

SEAT NO. :

[Total No. of Pages : 3]

FE 2008 COURSE BASIC ELECTRICAL ENGINEERING

Time: 3 Hours

Max. Marks : 100

Instructions to the candidates:

- 1) *Answers to the two sections should be written in separate answer books.*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right side indicate full marks.*
- 4) *Use of Calculator is allowed.*
- 5) *Assume Suitable data if necessary*

SECTION I

- Q.1 (a) Define Resistance Temperature Coefficient (RTC). State its unit. With usual notations prove that 8M

$$\alpha_2 = \alpha_1 / [1 + \alpha_1 (t_2 - t_1)]$$

- (b) An electric pump lifts 12 m^3 of water per minute to a height of 15 meters. If its overall efficiency is 60 %, find the input power. If the pump is used for 4 hours a day find the cost of energy for the month of April. 8M

OR

- Q.2 (a) Define insulation resistance & Derive its expression for single core cable. 8M
- (b) With neat sketch explain construction & working of Lead Acid Battery. 8M
- Q.3 (a) State & Prove maximum power transfer theorem as applied to a d c resistive circuit. 8M
- (b) Obtain the equations to convert delta connected resistive network into equivalent star connected network. 8M

OR

- Q.4 (a) State & explain Kirchoff's laws as applied to a d c circuit. 8M
- (b) State & explain Superposition Theorem as applied to a d c circuit. 8M
- Q.5 (a) Compare Electric circuit with magnetic circuit stating clearly the similarities & dissimilarities. 8M
- (b) Define self inductance of a coil. & hence state the factors that affect its value. 4M
- (c) The length of an air cored solenoid is 1.7 m & area of cross section is 12 cm^2 . The number of turns of the coil is 1000. Calculate- 6M
- a) the self inductance b) the energy stored in the magnetic field when a current of 10 A flows through the coil.

OR

- Q.6 (a) Define & state units of i) Reluctance ii) MMF 8M
 iii) Magnetic flux density iv) permeance
- (b) Compare statically induced emf & Dynamically induced emf 4M
- (c) Define coefficient of coupling & Derive expression for it. 6M

SECTION II

- Q.7 (a) Define Average value of sinusoidally varying quantity. Derive its expression in terms of its peak value. 8M
- (b) Two capacitors of $8\ \mu\text{f}$ & $2\ \mu\text{f}$ are connected in series across 400 V supply. Calculate i) resultant capacitance ii) charge on each capacitor iii) voltage across each capacitor. 6M
- (c) Define & state the units of - i) Electric flux density ii) Electric field intensity 4M

OR

- Q.8 (a) Define RMS value of sinusoidally varying quantity. Derive its expression in terms of its peak value. 8M
- (b) An alternating current is given by $i = 14.14 \sin 377t$. Find i) RMS value of current 6M
 ii) Frequency iii) instantaneous value of current at $t = 3\ \text{msec}$. Assume wave starts from origin & increasing positively.
- (c) Define - i) Form factor ii) Peak factor 4M
- Q.9 (a) A series R-L-C circuit has resistance of 50 ohms, inductance of 0.1 H & capacitance of $50\ \mu\text{f}$ connected in series across single phase 230 V, 50 Hz supply. Calculate - i) current drawn by circuit ii) power factor of circuit iii) active and reactive power consumed by the circuit. 8M
- (b) Define the terms - i) admittance ii) conductance iii) susceptance as related to a c circuit. State their units. Draw admittance triangle. 8M

OR

- Q.10 (a) Two impedances $(8+j6)\ \Omega$ & $(3-j4)\ \Omega$ are connected in parallel. If the total current drawn by combination is 25 A at unity power factor, find the current and power taken by each impedance. 8M
- (b) Sketch the waveform of voltage, current & power if $v = V_m \sin \omega t$ volts is applied across R-L series circuit. Derive the expression of current in this case. Also state the expression of power in this case. 8M
- Q.11 (a) Write short notes on - i) Losses in transformer ii) Dimmerstat 8M
- (b) Three identical coils each having resistance of $10\ \Omega$ & inductance of 0.03 H are connected in delta across a three phase 400 V, 50 Hz supply. Calculate - 8M
 i) Phase current ii) line current iii) total power consumed by load.

OR

- Q.12 (a) With the help of neat circuit diagram describe the method of performing direct load test on a single phase transformer. Explain how efficiency & regulation can be calculated in this case. 8M
- (b) Derive the emf equation of single phase transformer. 4M
- (c) State the relationship between line value & phase value of voltage and current for 3 phase star connected load. Also state the expression for active power and reactive power. 4M
