

266

Total No. of Questions : 8]

SEAT No. :

P2018

[Total No. of Pages : 2

F.E.

BASIC ELECTRONICS ENGINEERING

(2012 Pattern)

Time : 2 Hours]

[Max. Marks :50

Instructions to the candidates:

- 1) *All questions are compulsory.*
- 2) *Figures to the right indicate full marks.*

- Q1)** a) Explain Voltage tripler and quadrupler circuit. [6]
b) Explain input output characteristics of CE amplifier. [6]

OR

- Q2)** a) Explain working principle of photo diode with characteristics. Why photodiode is operated in reverse biased mode when used as a optical detector. [6]
b) Explain Drain Characteristics of an n-channel enhancement type MOSFET. [6]

- Q3)** a) Draw the circuit diagram and write the output equation for [6]
i) Inverting summer with three inputs
ii) Ideal differentiator
b) Explain the operation of Multiplexer and Demultiplexer [6]

OR

- Q4)** a) Draw three pin IC voltage regulator. Define load and Line regulation. [6]
b) Implement the following with minimum number of NAND gates. [6]
i) $y = AD + CB$
ii) $z = A(\bar{B} + CD)$

P.T.O.

Q5) a) Explain with block diagram Digital Thermometer. [7]

b) Explain construction of SCR. [6]

OR

Q6) a) Explain various criteria used to select a transducer. [7]

b) Explain Characteristics of DIAC. [6]

Q7) a) Give advantages, disadvantages and applications of Co-axial cable. [6]

b) Explain the block diagram of GSM system. [7]

OR

Q8) a) Define Modulation index with reference to AM and FM. Draw AM waveform for overmodulation case. [6]

b) Write a note on Optical Fiber and explain how light travels through a fiber. [7]

