



304205

Seat No.	
-------------	--

T.E. (Electronics) (Semester – I) Examination, 2014
POWER ELECTRONICS
(2008 Course)

Time : 3 Hours

Max. Marks : 100

- Instructions :**
- 1) Answers to the **two** Sections should be written in **separate** answer books.
 - 2) **Neat** diagrams and waveforms must be drawn **wherever** necessary.
 - 3) Figures to the **right** side indicate **full** marks.
 - 4) Use of nonprogrammable calculator is **allowed**.
 - 5) Assume suitable data if **necessary**.

SECTION – I

1. a) With the help of neat circuit diagram and relevant waveforms, explain operation of circulating current type single phase dual converter. Derive the expression for average o/p voltage. 10
b) A three phase full converter is operated from a three phase Y-connected 208 V, 60 Hz supply and the load resistance is 10Ω . If $\alpha = 60^\circ$ find average o/p d.c. voltage, r.m.s. o/p voltage, r.m.s. o/p current, average output current and rectification efficiency. 8
- OR
2. a) Explain effect of source impedance on the performance of single phase full converter, derive the expression for average o/p voltage. 10
b) What are the different types of triggering methods for Phase Controlled Rectifiers ? Explain any one in detail, 8
3. a) Explain with circuit diagram operation of step up chopper. Derive an expression for its o/p voltage. 8
b) A dc chopper has a resistive load of 10Ω and the input voltage is 220 V. When the chopper switch remains on, its voltage drop is 2 V and the chopping frequency is 1 kHz. If the duty cycle is 50%, determine
i) the average output voltage
ii) the rms output voltage
iii) the chopper efficiency
iv) the effective input resistance of the chopper. 8

OR

4. a) Explain the operation of four quadrant chopper with circuit diagram and waveforms. 8
b) Explain the operation of Buck-Boost converter. Derive the equation of average output voltage. 8

P.T.O.



5. a) Explain with circuit diagram and waveforms operation of SLR half bridge DC to DC converter in discontinuous mode. 10
 b) Compare ZVS and ZCS. 6
 OR
6. a) What is cyclo converter ? Explain single phase cyclo converter with various wave forms. 10
 b) Write note on Matrix converters. 6

SECTION – II

7. a) Explain the operation of three phase transistorized inverter for resistive star connected load. Draw relevant waveforms with 120° conduction mode. 10
 b) Write a note on voltage control and harmonic reduction in voltage source inverter. 8
 OR
8. a) Compare voltage source inverter and current source inverter. 6
 b) Explain with relevant waveforms sequential current source inverter in detail. 12
9. a) Draw a twelve pulse converter used in HVDC transmission. Write the advantages of HVDC transmission over HVAC transmission. 8
 b) What are different protection circuits for power devices ? Explain with circuit diagram how to protect a power device from dv/dt rating. 8

OR

10. Write a note on (any two) : 16
 a) Electronic ballast
 b) Electric welding
 c) HF induction heating.
11. a) What is importance of power factor ? Explain symmetric angle control method for the power factor improvement. 8
 b) Explain measurement of power line disturbances. 8

OR

12. a) Explain types of power line disturbances with sources and preventive techniques. 8
 b) Write a note on energy audit. 8