

Total No. of Questions : 12]

SEAT No. :

P3507

[4858]-156

[Total No. of Pages : 2

T.E. (Electronics) (Semester - II)
DRIVES AND CONTROL (DAC)
(2008 Pattern)

Time : 3 Hours]

[Max. Marks : 100

Instructions to the candidates:

- 1) *Answers to the two sections should be written in separate books.*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right indicate full marks.*
- 4) *Assume suitable data, if necessary.*

SECTION - I

- Q1)** a) Explain with a neat circuit diagram and relevant waveforms the working of 3 ϕ dual converter. **[8]**
b) Explain working of 1- Φ full converter for continuous and discontinuous current mode of series d.c. motor drive. **[10]**

OR

- Q2)** a) Explain the motor performance parameter. **[8]**
b) The speed of a separately excited motor is controlled by 1 ϕ Semi converter. The field current is also controlled a semiconverter is set to maximum possible value. The ac supply vtg. to the armature & field converter is 1 Φ 230 50 Hz, $R_a = 0.25\Omega$, $k_v = 0.7032$ v/a-rad/s, $T_L = 50$ N-m at 1000 rpm. The armature & field current are continuous & ripple free. Determine **[10]**
i) the field current I_F
ii) Delay angle α_a
iii) I/p PF of armature ckt. converter

- Q3)** a) Explain open loop control of dc drives with transfer function. **[8]**
b) Explain briefly the braking methods of d.c. motors. **[8]**

OR

- Q4)** a) What is PLL? Explain in Brief. **[8]**
b) Compare the PF improvement techniques SAC, EAC, PWM. **[8]**

- Q5)** a) Which are the speed control methods of induction motor? Explain briefly one of the methods. **[8]**
b) Explain briefly the braking methods of induction motor. **[8]**

P.T.O.

OR

- Q6)** a) Explain the various protections for induction motor. [8]
b) Explain the construction and operation of 3 ϕ induction motor. Derive the expression for slip. [8]

SECTION - II

- Q7)** a) Explain the Cylindrical rotor motor with vector diagram. [8]
b) Draw and explain the operation of 3 ϕ brushless d.c. motor drive. [10]

OR

- Q8)** a) Compare Variable reluctance motor and Salient pole Synchronous motor. [10]
b) Difference between half step and full step control of stepper motor. [8]

- Q9)** a) Explain the switched reluctance motor and close loop control of synchronous motor. [8]
b) Describe construction and principle of working : [8]
i) Variable reluctance and
ii) Permanent magnet type stepper motors.

OR

- Q10)** a) List the drive requirements for stepper motor drive. Draw the circuit diagram and explain the working of Chopper drive (unipolar) for stepper motor. [8]
b) With the help of a neat circuit diagram and relevant waveforms, explain the operation of bipolar voltage chopper drive for PM and hybrid stepper motors. [8]

- Q11)** a) Explain Neural network based PWM controller. [8]
b) Explain Fussy logic based wind generation system. [8]

OR

- Q12)** Write short note on : [16]
a) Traction motor driver
b) PI control tuning of a drive
c) Chopper fed DC drives.

