

Total No. of Questions : 12]

SEAT No. :

P1394

[Total No. of Pages : 3

[4858] - 155

T.E. (Electronics)

POWER ELECTRONICS

(2008 Pattern) (Semester - I)

Time : 3 Hours]

[Max. Marks : 100

Instructions to the candidates:

- 1) Answer any three questions from each section.*
- 2) Answers to the two sections should be written in separate answer books.*
- 3) Neat diagrams must be drawn wherever necessary.*
- 4) Figures to the right side indicate full marks.*
- 5) Use of calculator is allowed.*
- 6) Assume suitable data if necessary.*

SECTION - I

Q1) a) Explain the operation of 3Øfully controlled bridge converter with R-L load. Describe in detail the following modes of operation with associated waveforms. [12]

i) Rectifier mode

ii) Inverter mode

b) For 3Øfully controlled bridge converter with R-L load derive an equation for r.m.s output voltage. [6]

OR

Q2) a) What is dual converter? Explain in detail the operation of dual converter with Circulating current. List the advantage and disadvantage of the same. [12]

b) What is triggering? Give types of triggering? Explain microprocessor/microcontroller based triggering. [6]

P.T.O.

Q3) a) What is DC to DC converter? Explain with circuit diagram & waveforms working of chopper? Why it is preferred over phase controlled converters. [10]

b) A D.C. chopper circuit connected to a 100V D.C. source supplies an inductive load having 40mH in series with a resistance of 5Ω . A freewheeling diode is placed across the load. The load current varies between the limits of 10A and 12A. Determine [6]

- i) Average value of load current.
- ii) Maximum value of load current.
- iii) The time ratio of the chopper.

OR

Q4) a) Explain working of SLR half bridge DC to DC converter along with waveforms. [8]

b) What is SMPS? Explain in brief. [8]

Q5) a) What is resonant converter? Explain the need of resonant converter. Give its Classification. [8]

b) Define cycloconverter. Explain basic principle of operation of cycloconverter with neat equivalent circuit diagram. State its advantages & disadvantages. [8]

OR

Q6) Write short notes on any three : [16]

- a) 4 Quadrant chopper.
- b) 2-quadrant type C chopper.
- c) Inverse Cosine Method.
- d) Matrix converter

SECTION - II

Q7) a) What are inverters? Explain with circuit diagram & waveforms, working 3 Φ voltage source inverter operating in 120° mode with R-load. [10]

b) Explain the sinusoidal pulse width modulation tech used in inverter. [8]

OR

Q8) a) What is the need of cooling in industries? Suggest the remedies for reducing heating & power Dissipation in the Semi- conductor devices. [10]

b) What do you mean by Snubbers circuit? Give design of snubber circuit. [8]

Q9) a) Explain HF induction heating. [8]

b) What is the difference between soldering & welding? Explain at least one type of welding techniques. [8]

OR

Q10) a) What is HVDC? Explain advantage of HVDC over HVAC. [10]

b) What is CT/PT? Explain. [6]

Q11) a) What is importance of power factor? Explain the EAC method for PF improvement. [10]

b) Explain sequence control of series converters. [6]

OR

Q12) a) What is necessity of power quality? Explain with different types of power line disturbances. [8]

b) What is energy audit? Explain the required procedure for energy audit. [8]

