

Total No. of Questions : 12]

SEAT No. :

P2011

[4759] -114

[Total No. of Pages : 3

B.E. (Electronics)

ADVANCED POWER ELECTRONICS

(2008 Course) (Semester - I) (Elective - I)

Time : 3 Hours]

[Max. Marks : 100

Instructions to the candidates:

- 1) *Answer any three questions from each section.*
- 2) *Answers to the two sections should be written in separate answer books.*
- 3) *Neat diagrams must be drawn wherever necessary.*
- 4) *Figures to the right indicate full marks.*
- 5) *All questions carry equal marks.*
- 6) *Assume suitable data, if necessary.*
- 7) *Use of logarithmic tables slide rule, moillier charts, electronic pocket calculator and steam tables is allowed.*

SECTION - I

Q1) a) What are converters? Explain with circuit diagram working of single phase series full converter for level load. [10]

b) What is the need of cooling in industries? Explain. [6]

OR

Q2) a) Explain the need of 12-pulse converter in industries? Draw suitable circuit diagram & W/F s for the same- [10]

b) What is power factor conditioning of rectifier diode? Explain. [6]

Q3) a) What are DC-drives? Explain with diagram how will you control the speed of DC motor using Microcontroller. [12]

b) Why cyclo converters are not preferred for Large AC power control applications? Comment on P.F. [6]

OR

P.T.O.

Q4) a) Explain Double sided PWM converter with circuit diagram & comment on p.f. [8]

b) What are AC drives? Explain with neat block diagram, speed control technique of 3ϕ I.M by using $\frac{v}{f}$ Method. Comment on T_q Vs N characteristics. [10]

Q5) a) What is soft switching in resonant converter? Explain with diagram & waveforms, working of ZVS resonant converter with suitable load. State its limitations. [10]

b) What are different types of harmonic elimination technique. [6]

OR

Q6) a) What are multi level inverters? Explain with circuit diagram & comment on p.f. [8]

b) With the help of block diagram, explain PLL control of DC drives & state its advantages. [8]

SECTION - II

Q7) a) What are low drop out regulators? Explain. [6]

b) Compare linear, switched mode & Resonant converters. [6]

c) Advanced modulation technique. [6]

OR

Q8) a) What is the role of power electronics in renewable energy? Explain with diagram variable wind energy conservation system. [10]

b) Explain with circuit diagram & waveforms working of ZCS system. [8]

Q9) a) What is power quality? Explain different types of power line disturbances, preventing & nullifying measurement techniques & comment on power related quality issues. [10]

b) What are solar powered drives? Explain. [6]

OR

Q10)a) What is HVDC? Explain. [8]

b) What is the need of energy audit? Explain. [8]

Q11)a) What are synchronous rectifier? Explain. [8]

b) What is FACTS [Flexible AC X^{ssion} system]. Explain in detail. [8]

OR

Q12) Write short notes on any three. [16]

a) Photo voltaic energy

b) Traction drives

c) H.F. heating

d) Battery charger circuit

e) Matrix

f) Adaptive control technique.

