

Total No. of Questions : 12]

SEAT No. :

P2329

[4758] - 64

[Total No. of Pages :3

T.E. (Electronics)

DRIVES & CONTROLS

(2008 Course) (304207) (Semester - II)

Time : 3 Hours]

[Max. Marks : 100

Instructions to the candidates:

- 1) Answer 3 questions from Section I and 3 questions from Section II.*
- 2) Answers to the two sections should be written in separate books.*
- 3) Neat diagrams must be drawn whenever necessary.*
- 4) Figures to the right indicate full marks.*
- 5) Electronic pocket calculator is allowed.*
- 6) Assume suitable data, if necessary.*

SECTION - I

- Q1)** a) Draw the circuit diagram and explain the operation of 3-Phase full converter drive. Also sketch the output voltage and output current waveform at firing angle of 90 degree and 120 degree. **[10]**
- b) Explain with associated waveforms how factor can be improved with symmetrical angle control scheme. **[8]**

OR

- Q2)** a) What is braking? Explain Regenerative braking of DC machine. Mention its advantages & disadvantages. **[8]**
- b) Draw the circuit & waveforms of single-phase full converter drives for continuous & discontinuous motor current. **[10]**

- Q3)** a) Explain open loop & closed loop control of dc drives with transfer function. **[10]**
- b) Explain the principle of phase locked loop control of dc drives with block diagram. **[6]**

OR

- Q4)** a) Explain the basic principle of operation of an Induction Motor with references to its equivalent circuit diagram. **[8]**
- b) With the help of diagram explain use of CSI for speed control of Induction Motor. **[8]**

P.T.O.

- Q5) a)** With the help of block diagram explain close loop control of Induction Motor. [10]
- b) Explain the necessity of soft acceleration & soft deceleration in case of Induction Motor. [6]

OR

- Q6)** Write short notes on following: [16]
- a) 2-Quadrant dc drive using chopper.
- b) Microprocessor/microcontroller based dc drive.
- c) Induction motor performances characteristics.
- d) Braking of Induction motor.

SECTION - II

- Q7) a)** Draw & explain torque versus torque angle characteristics of Synchronous motor with cylindrical rotor. [8]
- b) With neat diagram explain Switched reluctance motor. [10]

OR

- Q8) a)** List the drive requirements for A C drive. [8]
- b) With neat block diagram explain microprocessor based Synchronous motor drive. [10]

- Q9) a)** Explain operation of a stepper motor driver circuit with diagram. Mention advantages. [8]
- b) With the help of diagrams & waveforms explain ac motor drive. [8]

OR

- Q10)a)** Explain operation of variable reluctance stepper motor with diagram.[8]
- b) Compare between ac & dc drive. [8]

- Q11)**a) Explain harmonic reduction techniques in inverters. [8]
b) Explain Tuning of a controller for a drive system. [8]

OR

- Q12)**a) Explain Torque-Speed characteristics with volts/hertz control in AC drives. [8]
b) With diagram explain static scherbius drive for Induction Motor control. [8]

