

Total No. of Questions : 12]

SEAT No. :

P2328

[4758] - 63

[Total No. of Pages :3

T.E. (Electronics)
POWER ELECTRONICS
(2008 Pattern) (Semester - I)

Time : 3 Hours]

[Max. Marks : 100

Instructions to the candidates:

- 1) Answer 3 questions from Section -I and 3 questions from Section -II.*
- 2) Answers to the two sections should be written in separate books.*
- 3) Neat diagrams must be drawn wherever necessary.*
- 4) Figures to the right indicate full marks.*
- 5) Use of logarithmic tables, electronic pocket calculator is allowed.*
- 6) Assume suitable data, if necessary.*

SECTION - I

Q1) a) Explain the operation of 3ϕ fully controlled bridge converter with resistive load. Describe in detail the following modes of operation with associated waveforms. **[12]**

- i) Discontinuous conduction mode
 - ii) Continuous conduction mode.
- b) For 3ϕ fully controlled bridge converter with resistive load derive an equation for rms output voltage. **[6]**

OR

Q2) a) What is dual converter? Explain in detail the operation of dual converter with Circulating current. List the advantage and disadvantage of the same. **[12]**

- b) What is triggering? Give types of triggering? Explain any one type of it. **[6]**

P.T.O.

Q3) a) What is DC to DC converter? Explain with circuit diagram & waveforms working of chopper? Why it is preferred over phase controlled converters. [10]

b) A step down chopper has resistive load of $R = 15\Omega$ and input voltage $E_{dc} = 200V$. When the chopper remains in ON, its voltage drop is 2.5V. The chopper frequency is 1kHz. If the duty cycle is 50%, determine [6]

i) average output voltage

ii) RMS output voltage

iii) chopper efficiency.

OR

Q4) a) What are Cycloconverter? Explain with diagram & waveforms, 3 pulse cycloconverter. State its advantages & disadvantages. [10]

b) What is SMPS? Explain in brief. [6]

Q5) a) What is resonant converter? Explain the need of resonant converter. [4]

b) Explain 3-pulse and 6-pulse cycloconverter. [6]

c) Write a short note on SLR half bridge DC to DC converter. [6]

OR

Q6) Write short notes on any three, [16]

a) 4 Quadrant chopper

b) μP based firing circuit for triggering.

c) Inverse Cosine Method

d) Matrix converter.

SECTION - II

Q7) a) What are inverters? Explain with circuit diagram & waveforms, working 3ϕ voltage source inverter operating in 180° mode with R-load. [10]

- b) Draw the schematic of a 3 ϕ CSI and describe its operation with current waveforms. [8]

OR

- Q8)** a) What is the need of cooling in industries? Suggest the remedies for reducing heating & power Dissipation in the Semi-conductor devices.[10]

- b) What is auto sequential current fed PWM inverter? Explain. [8]

- Q9)** a) What is electric ballast? Explain with diagram and characteristics. [8]

- b) What is the difference between soldering & welding? Explain at least one type of welding techniques. [8]

OR

- Q10)** a) What is HVDC? Explain with its application. [10]

- b) What is CTPT? Explain. [6]

- Q11)** a) What is power quality? Explain different types of power line disturbances, preventive & nullifying measurement techniques. [10]

- b) What is the need of 12 pulse inverter in industry? Explain. [6]

OR

- Q12)** a) What is necessity of power quality? Explain with different types of power line disturbances. [8]

- b) What is energy audit? Explain the required procedure for energy audit.[8]

