

Total No. of Questions : 8]

SEAT No. :

P2397

[4758] - 558

[Total No. of Pages :4

T.E. (Electronics)

NETWORK SYNTHESIS

(2012 Pattern) (Semester - I) (End - Semester)

Time : 3 Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Answer Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right side indicate full marks.
- 4) Use of electronic pocket calculator is allowed.
- 5) Assume Suitable data if necessary.

Q1) a) Determine the range of 'k' so that, polynomial $P(s) = s^3 + 14s^2 + 56s + k$ is Hurwitz. **[6]**

b) Synthesize the following function using Foster - II and Cauer - II form. **[6]**

$$Z(s) = \frac{s(s^2 + 9)}{(s^2 + 1)(s^2 + 16)}$$

c) Realize the transfer function as an open circuited LC ladder network. **[8]**

$$H(s) = \frac{s^4}{(s^2 + 1)(s^2 + 3)}$$

OR

Q2) a) Explain the following basic removal operations? **[6]**

- i) Removal of a pole at $s = \infty$ from the function.
- ii) Removal of a pole at $s = 0$ from the function.

b) An admittance function is given as: **[6]**

$$Y(s) = \frac{8s^2 + 10s}{s + 1}$$

Realize the network using Cauer - I and Cauer - II form.

P.T.O.

- c) What is constant Resistance Network? Also Synthesize the following transfer function for a constant resistance lattice with $1\ \Omega$ termination.[8]

$$\frac{V_2}{V_1} = \frac{s^2 - 3s + 2}{s^2 + 3s + 2}$$

- Q3)** a) State the properties of Butterworth Approximation? [4]
 b) Find the transfer function of third order normalized low pass Butterworth filter and realize as a LC transfer impedance function terminated by $1\ \Omega$? [8]
 c) Convert the low pass filter of Fig 1, into a band stop filter with $500\ \Omega$ impedance level, bandwidth (B.W) = 20 Krad/sec. and pass band center at $\omega_0 = 50$ Krad/sec. [4]

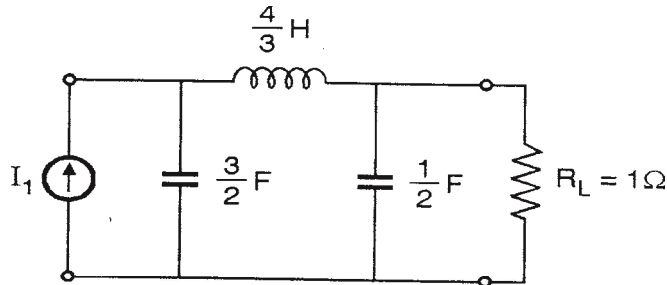


Figure 1

OR


- Q4)** a) Explain frequency and impedance normalization? [5]
 b) Obtain a system function $H(s)$ that exhibits the Chebyshev characteristics with not more than 1dB ripple in pass band and attenuation of 20dB at $\omega = 2$ rad/sec. [6]
 c) Explain in detail the properties of Chebyshev polynomials used in filter approximation? [5]

- Q5)** a) Synthesize second order low pass filter to have a pole frequency of 25 kHz and a pole Q is 10? Use Sallen and Key circuits based on positive feedback topology. [10]
 b) What is cascade approach in active filter synthesis? Explain in brief and list the advantages of the approach? [6]

OR

- Q6)** a) Design third order low pass Butterworth filter with cut-off frequency $f_c = 2\text{kHz}$ (use positive feedback topology)? [8]
- b) Design a second order Butterworth low pass filter having upper cut off frequency is 1.5kHz ? Then using RC-CR transformation realize high pass filter with same frequency? [8]

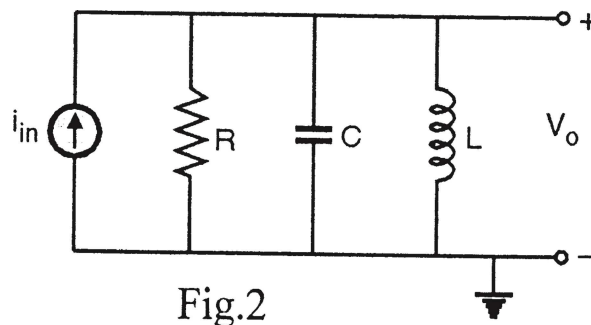- Q7)** a) Find the transfer impedance function $\frac{V_o}{I_{in}}$ for the passive RLC Circuit shown in fig. 2? Compute the sensitivities of ω_p , Q_p and K with respect to the passive elements R , L and C ? [6]



- b) Explain the concept of gain sensitivity? Also explain the various factors affecting the gain sensitivity? [6]
- c) Explain the effect of offset voltage on active filter performance. The input to the inverter shown in Fig. 3 is a sine wave of amplitude 5 volt. If the slew rate of the op amp is 1V/sec , find the frequency at which the slew rate limiting occurs. [6]

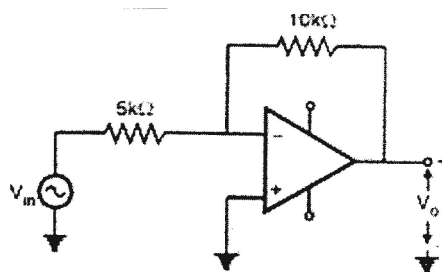


Figure 3

OR

Q8) a) Define sensitivity? Why it is needed? Find sensitivity of resonating frequency of series resonating circuit with respect to the components R, L and C? [6]

b) Prove the following sensitivity relationships? [4]

i) $S_{\sqrt{P}} = \frac{1}{2} S_X^P$

ii) $S_{\sqrt{X}}^P = 2 S_X^P$

c) Discuss how the following parameters of op amp affect the filter performance? [8]

i) Dynamic range

ii) Slew rate

iii) Input Offset voltage

iv) CMRR

