

Total No. of Questions : 12]

SEAT No. :

P4900

[Total No. of Pages : 3

[4959]-116

B.E. (Electronics)

ADVANCE POWER ELECTRONICS

(2008 Course)

Time : 3 Hours]

[Max. Marks : 100

Instructions to the candidates:-

- 1) Answers to the two sections should be written in separate books.*
- 2) Neat diagrams must be drawn wherever necessary.*
- 3) Figures to the right indicate full marks.*
- 4) Assume suitable data, if necessary.*

SECTION - I

Q1) a) Draw a neat circuit diagram and relevant waveforms of a single phase series full converter. **[10]**

b) Why power factor of a controlled converter is never unity even for a resistive load? **[8]**

OR

Q2) a) Explain how unwanted harmonics are eliminated in a 12 pulse converter? **[8]**

b) Draw a circuit diagram of 3 phase IGBT based PWM rectifier and explain the advantages. **[10]**

Q3) a) Draw equivalent circuit diagram of a separately excited DC motor. State the equations that govern the operation of the motor. Explain the field weakening operation. **[8]**

b) Draw a circuit diagram and waveforms of a Cyclo converter to reduce the incoming frequency by a factor of four. **[8]**

OR

Q4) a) Why V/f method of induction motor speed control is very popular? **[8]**

b) Draw circuit diagram and explain operation of ZCS converter. **[8]**

P.T.O.

- Q5) a)** Draw circuit diagram of a three level multilevel inverter and explain the device selection criteria. **[8]**
- b) Explain the third harmonic injection modulation method to improve THD of inverter output. **[8]**

OR

- Q6) a)** Why PLL drive improves the speed regulation of a drive? **[8]**
- b) Explain microcontroller based DC motor drive. **[8]**

SECTION - II

- Q7) a)** Compare linear power supply, SMPS and resonant converter power supply. **[6]**
- b) Explain an application where Low Drop out regulator is essential. **[6]**
- c) Explain the concept of soft switching. **[6]**

OR

- Q8) a)** With relevant diagram explain traction motor drive. **[8]**
- b) What are parallel redundant power supplies? How load is shared in these supplies? **[10]**

- Q9) a)** What is power quality? Explain the different line disturbances and their mitigation techniques. **[8]**
- b) Why Bi-Directional converter is essential for a wind energy system? **[8]**

OR

- Q10)a)** What are the advantages and applications of HVDC system? **[8]**
- b) Draw schematic circuit of solar PV operated battery assisted DC motor drive? **[8]**

Q11)a) What are synchronous rectifiers? Explain in detail. **[8]**

b) Explain Fuzzy logic based wind generation system. **[8]**

OR

Q12) Write short notes on : **[16]**

- a) Z source inverters
- b) Cascaded H bridge multilevel inverters
- c) Energy Audit
- d) Flexible AC transmission

