

Total No. of Questions—6]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

[4956]-11

F.E. (Common) (Second Semester) EXAMINATION, 2016

BASIC ELECTRONICS ENGINEERING

(2008 Pattern)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Answer Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6.

(ii) Answer *all* questions in same answer-book.

(iii) Neat diagrams must be drawn wherever necessary.

(iv) Figures to the right side indicate full marks.

(v) Use of calculator is allowed.

(vi) Assume suitable data if necessary.

1. (a) A bridge rectifier is applied with input from a step down transformer having turns ratio 8 : 1 and input 230V, 50Hz. If diode forward resistance is 1Ω , secondary resistance is 10Ω , load resistance is $2K\Omega$, [8]

find :

- (i) DC power output
- (ii) PIV across each diode
- (iii) Percentage efficiency
- (iv) Percentage regulation.

(b) Explain the operation of BJT as a switch with neat diagram. [4]

(c) With a neat construction diagram explain the working of TRIAC. Also draw its characteristic. [6]

P.T.O.

Or

2. (a) Explain the operation of a bridge rectifier. Also state its advantages. [8]
(b) Write a short note on : Seven segment display. [4]
(c) Compare SCR and TRIAC. [6]
3. (a) Draw a neat diagram of three input inverting summing amplifier using op-amp and obtain the expression of its output voltage. [8]
(b) What is full adder ? Explain the working of full adder with the help of truth table and give equation for sum and carry. [8]

Or

4. (a) Draw diagram of 8 : 1 MUX. What is the relation between number of select lines and inputs ? Give applications of multiplexers. [6]
(b) Draw a neat circuit diagram of Ideal integrator and explain its operation with input and output waveform. Also state drawbacks of this circuit. [6]
(c) State and prove the DeMorgan's theorems. [4]
5. (a) Differentiate AM and FM. [6]
(b) Write expression of AM. Also draw its frequency spectrum. [2]
(c) Draw constructional details of LVDT (displacement transducer). Explain its operation. State its advantages and disadvantages. [8]

Or

6. (a) What is the need of modulation ? Explain. [6]
(b) Explain wired communication and wireless communication. [4]
(c) Draw block diagram of electronic weighing machine and explain its operation. [6]