

Total No. of Questions :12]

SEAT No. :

**P2921**

[Total No. of Pages :3

**[4958] - 155**

**T.E. (Electronics)**

**POWER ELECTRONICS**

**(Semester - I) (2008 Course)**

*Time : 3 Hours]*

*[Max. Marks :100*

*Instructions to the candidates:*

- 1) Answer 3 questions from section - I and 3 questions from Section - II.*
- 2) Answer to the two Sections should be written in separate books.*
- 3) Neat diagrams must be drawn wherever necessary.*
- 4) Figures to the right indicate full marks.*
- 5) Use of logarithmic tables, electronic pocket calculator is allowed.*
- 6) Assume suitable data, if necessary.*

**SECTION - I**

- Q1)** a) For  $3\phi$  fully controlled bridge converter with R-L load derive an equation for r.m.s output voltage. **[6]**
- b) Explain the operation of  $3\phi$  fully controlled bridge converter with R-L load. Describe in detail the following modes of operation with associated waveforms. **[12]**
- i) Rectifier mode
  - ii) Inverter mode

OR

- Q2)** a) What is dual converter? Explain in detail the operation of dual converter with Circulating current. List the advantage and disadvantage of the same. **[12]**
- b) Define **[6]**
- i) Holding Current
  - ii) Latching Current
  - iii) Forward break over voltage

**P.T.O.**

**Q3) a)** What is DC to DC converter? Explain with circuit diagram & waveforms working of chopper? Why it is preferred over phase controlled converters. **[10]**

b) A d.c chopper circuit connected to a 100 V d.c source supplies an inductive load having 40mH in series with a resistance of  $5\Omega$ . A freewheeling diode is placed across the load. The load current varies between the limits of 10A and 12A. Determine **[6]**

- i) average value of load current
- ii) maximum value of load current.
- iii) the time ratio of the chopper.

OR

**Q4) a)** Explain working of SLR half bridge DC to DC converter along with waveforms. **[8]**

b) What is SMPS? Explain in brief. **[8]**

**Q5) a)** What is resonant converter? Explain the need of resonant converter. Give its classification. **[8]**

b) Define cycloconverter. Explain basic principle of operation of cycloconverter with neat equivalent circuit diagram. State its advantages & disadvantages. **[8]**

OR

**Q6)** Write short notes on any three, **[16]**

- a) 4 Quadrant chopper.
- b) 2 - quadrant type C chopper.
- c) Inverse Cosine Method
- d) Matrix converter

## **SECTION - II**

- Q7)** a) Classify Inverters. Explain with circuit diagram & waveforms, working  $3\phi$  voltage source inverter operating in  $120^\circ$  mode with R - load. [10]  
b) Explain the sinusoidal pulse width modulation tech used in inverter. [8]

OR

- Q8)** a) What is the need of cooling in industries? Suggest the remedies for reducing heating & power Dissipation in the Semi - conductor devices.[10]  
b) What do you mean by Snubberscircuit. Give design of snubber circuit.[8]

- Q9)** a) Explain HF induction heating. [8]  
b) What is the difference between soldering & welding? Explain at least onetype of welding techniques. [8]

OR

- Q10)**a) What is HVDC? Explain advantage of HVDC over HVAC. [10]  
b) What is CTPT? Explain. [6]

- Q11)**a) What is importance of power factor. Explain the EAC method for PF improvement. [10]  
b) Explain sequence control of series converters. [6]

OR

- Q12)**a) What is necessity of power quality? Explain with different types of power line disturbances. [8]  
b) What is energy audit? Explain the required procedure for energy audit.[8]

