

**T.E. (Electronics)**  
**DRIVES AND CONTROLS**  
**(2008 Course) (304207) (Semester - II)**

*Time : 3 Hours]*

*[Max. Marks : 100*

*Instructions to the candidates:*

- 1) *Answer Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8, Q9 or Q10, Q11 or Q12.*
- 2) *Answers to the TWO sections should be written in separate book.*
- 3) *Neat diagrams must be drawn wherever necessary.*
- 4) *Figures to the right side indicate full marks.*
- 5) *Assume Suitable data if necessary.*
- 6) *Use of nonprogrammable Electronic pocket calculator is allowed.*

**SECTION - I**

- Q1)** a) What are DC motor performance parameters? Explain in brief. [6]
- b) Compare chopper fed and Converter fed DC drives? Also explain how to select a power electronics converter for a DC motors drive. [6]
- c) Explain with circuit diagrams the operation of single phase dual converter fed drive for a separately excited DC motor. [6]

OR

- Q2)** a) Draw and explain the working of three phase full converter feeding a separately excited d.c. motor. Explain with typical waveforms, the operation in continuous and discontinuous armature current modes. [8]
- b) Explain any two power factor improvement techniques for single phase converters. [10]

- Q3)** a) What is PLL? Explain in brief with block diagram PLL based speed control of a DC motor. Explain the advantages of this control. [8]
- b) What are the advantages of Microprocessor based drives? With the help of a neat block diagram, explain the operation of Microcontroller based single phase dual converter fed DC drive. [8]

OR

- Q4)** a) What is the need of braking? Explain in detail dynamic and regenerative braking for DC machines. [8]
- b) Explain the operation of a closed loop DC motor drive. Also explain closed loop control of DC drives with Transfer function. [8]
- Q5)** a) With the help of neat diagram explain use of CSI for speed control of three phase induction motor. [8]
- b) Explain Direct and Indirect Vector control of three phase induction motors? [8]

OR

- Q6)** a) Enlist different methods for speed control of induction motor. Explain variable frequency control of 3 phase induction motor using Cycloconverter. [8]
- b) State and explain various schemes for induction motor speed control by voltage source inverters. [8]

### SECTION - II

- Q7)** a) Compare Salient pole motor and Permanent magnet motor. [4]
- b) Draw and explain block diagram of a self controlled synchronous motor fed from a three phase inverter. [8]
- c) Draw and explain briefly the torque speed characteristics of synchronous reluctance motor at constant voltage and frequency. [6]

OR

- Q8)** Write Short note on [18]
- a) Salient pole motor Drive.
- b) Cylindrical rotor motor Drive.
- c) Synchronous Reluctance motor drive.
- Q9)** a) With the help of a neat circuit diagram and waveforms explain the operation of 3 phase brushless dc motor drive. Also explain related waveforms. [8]
- b) Explain the operation of Switched Reluctance motor. Also list the advantages of SRM used as adjustable speed drive. [8]

OR

- Q10)** a) What is a stepper motor? Explain various operating modes of stepper motor. Mention various types of stepper motors. Explain any one in details. [8]
- b) Compare variable reluctance motor with permanent magnet stepper motor. [4]
- c) Explain the operation of any one stepper motor driver circuit. [4]

- Q11)** a) What is Neuro Fuzzy system? Explain Adaptive network based Fuzzy Interface System. [8]
- b) Explain the operation of Fuzzy logic based Induction motor drive. [8]

OR

**Q12)** Write Short notes on (any two) [16]

- a) Neural network based PWM controller.
- b) Application of neural network in drives and control.
- c) Traction drives.

x x x