

[5058]-75**T.E. (Electronics) (Semester - I)****POWER ELECTRONICS****(2008 Pattern)****Time : 3 Hours]****[Max. Marks : 100****Instructions to the candidates:**

- 1) *Answers to the two Sections should be written in separate books.*
- 2) *Figures to the right indicate full marks.*
- 3) *Use of logarithmic tables and electronic non-programmable pocket calculator is allowed.*
- 4) *Assume suitable data, if necessary*
- 5) *Solve Q. 1 or 2, Q. 3 or 4, Q. 5 or 6 from Section I and Q. 7 or 8, Q. 9 or 10, Q. 11 or 12 from Section II*

SECTION - I

- Q1)** a) Explain working of 3 phase semi controlled converter with circuit diagram and waveforms for RL load. Comment on power factor. Derive equation for DC load voltage and Load current. **[10]**
- b) Explain source and load inductance effect on the operation of single phase converter. Derive the equation of average output current ' I_{dc} ' and load voltage V_L . **[8]**

OR

- Q2)** a) Single phase dual converter is operated from a 120 V, 50Hz supply and $R_L = 20$ ohms. The circulating inductance is $L_c = 60$ mH. Delay angles are $\alpha_1 = 60$ and $\alpha_2 = 120$. Calculate the peak circulating current. **[8]**
- b) What is need of triggering? Explain UJT or MSI triggering for three phase controlled converter with suitable diagram. Discuss necessity of isolation in triggering and converter circuit? **[10]**
- Q3)** a) Explain working of Buck-Boost converter with circuit diagram. Which factors decide buck-boost action, How? **[8]**
- b) DC chopper is working at 40 KHz with battery voltage of 200 V. The minimum turn-on and turn-off time of the chopper are $2\mu\text{sec}$ and $4\mu\text{Sec}$ respectively. Determine the min. and max. dc voltage that the chopper can deliver. **[8]**

P.T.O.

OR

- Q4)** a) Explain fly-back converter topology for SMPS with circuit diagram, waveform and mathematical analysis. [8]
- b) Explain operation of four quadrant chopper with waveforms. How this is utilized in reversible drive? [8]

- Q5)** a) Explain operation of SLR half bridge DC/DC converter in low frequency (discontinuous conduction) mode [8]
- b) Why cycloconverters are required? Explain operation of 6 pulse cycloconverters with diagram and waveforms. [8]

OR

- Q6)** a) What are resonant converters? Why zero current switching is preferred at high voltages? [8]
- b) Compare Linear, Switched mode and resonant converter with merits and de-merits of each. [8]

SECTION - II

- Q7)** a) Explain working of 3 phase VSI with 180° conduction mode with purely resistive load. Draw circuit diagram and waveforms for load voltage and current [10]
- b) Explain different voltage control methods in inverters [8]

OR

- Q8)** a) Transistorised inverters are better in performance than thyristorised one. Justify. [8]
- b) Draw circuit diagram of a Three phase CSI and explain its operation with current waveforms. [10]

- Q9)** a) Compare and contrast different types of cooling techniques [8]
- b) Why di/dt and dv/dt protection is required? List considerations and steps in designing these protection circuits. [8]

OR

- Q10)** a) Explain Electric welding process with its block diagram and operation[8]
b) What is HVDC transmission? List its merits over HVAC transmission.[8]

- Q11)** a) Compare phase angle control (PAC) and symmetric angle control (SAC) methods of controlling load voltages. [8]
b) Why energy audit is necessary? Explain the process in steps / flowchart.[8]

OR

- Q12)** a) Compare different power factor improvement schemes [8]
b) What are different power line disturbances? How to minimize them? [8]

