

G.R. No.	
----------	--

DECEMBER 2017 / ENDSEM**F. Y. B. TECH. (COMMON) (SEMESTER - I)****COURSE NAME: Basic Electronics Engineering
(2017 PATTERN)**

Time: [2 Hours]

[Max. Marks: 50]

(* Instructions to candidates:

- 1) Answer Q.1 OR Q.2, Q.3 OR Q.4 and Q.5
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

- Q.1 a) State and prove Demorgan's theorems, Draw the logical diagrams. [6]
b) Design half adder with the help of suitable logic gates. [6]
c) Prove the following [4]
i) $(A+B)(A+C) = A+BC$
ii) $\overline{AB} + \overline{CD} + \overline{EF} = (\overline{A} + \overline{B})(\overline{C} + \overline{D})(\overline{E} + \overline{F})$

OR

- Q.2 a) Convert binary number 110110.1011 to decimal number and convert [6]
decimal number 82.625 to binary number.
b) Explain the working of 4:1 MUX and 1:4 De-MUX with block diagram [6]
and truth table.
c) Explain D flip flop with truth table. [4]
- Q.3 a) Draw and explain the block diagram of basic instrumentation system. [6]
b) Compare active and passive transducer. [4]
c) Explain any four characteristics of transducer. [4]

OR

- Q.4 a) What is RTD? Explain its construction and working principle. Draw the [6]
circuit diagram for measurement of temperature using RTD.
b) What is primary and secondary transducer? State two examples of each. [4]
c) Draw the construction diagram of thermistor and explain the working [4]
principle of it.

Q.5) Attempt following multiple choice questions: [1x20=20 marks]

1. Peak inverse voltage for a diode is the [1]
 - a) voltage corresponding to rated maximum voltage
 - b) maximum voltage that can be applied across the diode in the conducting direction
 - c) maximum voltage that can be applied across the diode in the non-conducting direction
 - d) none of the above.
2. The output frequency of a full-wave rectifier is _____ the input frequency. [1]
 - a) one-half
 - b) equal to
 - c) twice
 - d) one-quarter
3. In photodiode ----- current is proportional to light incident. [1]
 - a) forward current
 - b) reverse current
 - c) reverse leakage current
 - d) dark current.
4. Which diode(s) have a zero current and voltage drop in the ideal model? [1]
 - a) Si
 - b) Ge
 - c) Neither Si nor Ge
 - d) Both Si and Ge
5. In LED light is emitted because [1]
 - a) Diode gets heated up
 - b) Light falling on gets amplified
 - c) Light gets reflected due to lens action
 - d) Recombination of charge carriers take place
6. A transistor has a β_{dc} of 250 and a base current, I_B of 20 μA . The collector current, I_C equals: [1]
(a) 500 nA b) 5 A c) 50 mA d) 5 mA

7. The phase difference between the input and output ac voltage signals of a common-emitter amplifier is _____. [1]
a) 0°
b) 180°
c) 80°
d) 360°
8. V_{CE} approximately equals _____ when a transistor is in cut off state. [1]
a) V_B
b) V_{CC}
c) 0.2 V
d) 0.7 V
9. In which region are both the collector-base and base-emitter junctions Reverse-biased? [1]
a) Active
b) Cutoff
c) Saturation
d) All of the above
10. When transistors are used in digital circuits they usually operate in the: [1]
a) active region
b) breakdown region
c) saturation and cutoff regions
d) linear region
11. A BJT is a _____-controlled device. The MOSFET is a _____ - controlled device. [1]
a) voltage, voltage
b) voltage, current
c) current, voltage
d) current, current
12. Which of the following devices does not have a cathode terminal? [1]
a) SCR
b) PN Junction Diode
c) Triac
d) Zener diode

13. Which of the following transistors can an SCR be represented as? [1]
- a) npn, pnp
 - b) npn, npn
 - c) pnp, pnp
 - d) None of the above
14. In the forward-blocking region, the SCR is [1]
- a) in the *off* state
 - b) reverse-biased
 - c) in the *on* state
 - d) at the point of breakdown
15. In E-MOSFET, there is no drain current until V_{GS} [1]
- a) reaches $V_{GS(th)}$
 - b) is positive
 - c) is negative
 - d) equals 0 V
16. How many terminals do the 78XX series fixed positive voltage regulators have? [1]
- a) 2 b) 3 c) 4 d) 5
17. The 7912 regulator IC provides _____. [1]
- a) 5 V b) -12V c) 12V d) -5V
18. With zero volts on both inputs, an op-amp ideally should have an output equal to [1]
- a) the positive supply voltage
 - b) zero
 - c) the negative supply voltage
 - d) the CMRR
19. For an op-amp with negative feedback, the output is [1]
- a) equal to the input
 - b) increased
 - c) fed back to the non-inverting input
 - d) fed back to the inverting input
20. A voltage-follower [1]
- a) has a gain of 1
 - b) is non-inverting
 - c) has no feedback resistor
 - d) has all of these