

G.R. No.

SEPTEMBER 2017 / IN - SEM (T1)**F. Y. B.TECH. (COMMON) (SEMESTER - I)****COURSE NAME : BASIC ELECTRICAL ENGINEERING****(2017 PATTERN)****Solution and scheme of marking**

Time : [1 Hour]

[Max. Marks : 30]

(*) Instructions to candidates:

- 1) Answer Q.1 OR Q.2, Q.3 OR Q.4
- 2) Figures to the right indicate full marks.

Q 1) a) Circuit dig	01M
Derivation correct steps	02M
Final three correct formulas	03M
b) Statement	02M
To find V_{Th}	01M
To find R_{eq}	01M
Thevenin's Equivalent circuit	01M
To find I_L	01M
c) $5I_1 + 10 I_2 = 4$	01M
$4I_1 - 9 I_2 = -3$	01M
$I_{5\Omega} = 0.0706 \text{ A}$	02M

OR

Q2) a) KCL- statement 01M,	Explanation with simple circuit	02M
KVL- statement 01M,	Explanation with simple circuit	02M
b) For 40V, $I_{XY} = 5\text{A}$ (forward)		02M
For 20V, $I_{XY} = 2.5\text{A}$ (reverse)		02M
For 10V, $I_{XY} = 1.876\text{A}$ (forward)		01M
$I_{XY} = 5 - 2.5 + 1.876 = 4.376\text{A}$ forward		01M

c) $6 \parallel 6 = 3$ and $12 \parallel 12 = 6 \Omega$	02M
$3, 3, 6$ in series $= 12 \Omega$	01M
$12 \parallel 10 = 5.45 \Omega$	01M

Q3) a) $X_L = 31.41 \Omega$, $Z = 37.24 \Omega$	01M
$I = 5.37A$	02M
p.f. $= 0.5370$ lag	01M
$P = 576.74 W$	02M

b) Circuit diagram	01M
Derivation	02M
Phasor diagram	01M

c) Impedance triangle	01M
$Z = R - j X_C \Omega$	01M
$\phi = \tan^{-1}(-X_C / R)$ Negative	01M
p.f. - leading	01M

OR

Q4) a) $X_C = 31.83 \Omega$	01M
Impedance, $Z = 50 - j31.83 \Omega$	01M
Power factor $= 0.8435$ leading	01M
Current $= 3.88 \angle 32.48^\circ A$	02M
Phasor diagram	01M

b) Form factor	Definition and value for sinusoidal waveform	01+01	02M
Peak factor	Definition and value for sinusoidal waveform	01+01	02M

c) Circuit diagram	01M
Derivation	02M
Phasor diagram	01M