

G.R. No.

SEPTEMBER 2017 / IN - SEM (T1)

F. Y. B.TECH. (COMMON) (SEMESTER - I)

COURSE NAME : BASIC ELECTRICAL ENGINEERING

(2017 PATTERN)

Time : [1 Hour]

[Max. Marks : 30]


(*) Instructions to candidates:

- 1) Answer Q.1 OR Q.2, Q.3 OR Q.4
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

Q 1) a) Obtain the equations to convert three given delta connected resistances R_{12} , R_{23} and R_{31} into its equivalent star circuit with circuit diagram. [6]

b) State Thevenin's theorem and explain the steps to find V_{Th} , R_{eq} , and load current I_L . [6]

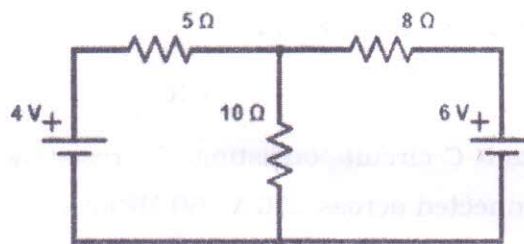
c) Using Kirchhoff's laws, calculate current flowing through 5Ω in given circuit. [4]




OR

Q2) a) State and explain Kirchhoff's laws. [6]

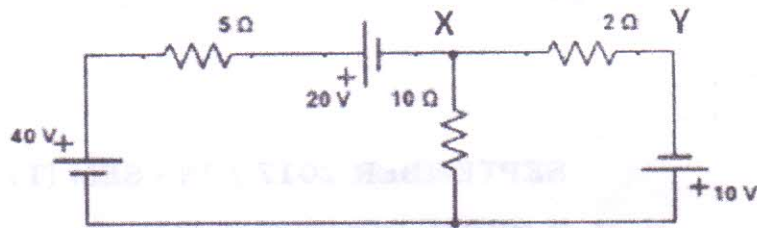b) Using superposition theorem, find current flowing through 2Ω resistance for the network shown. [6]



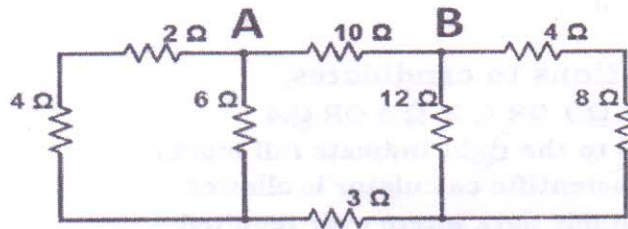- c) Find equivalent resistance between A and B for the network shown in the figure below. [4]



- Q3) a) A coil having resistance of $20\ \Omega$ and an inductance of $0.1\ \text{H}$ is connected to $200\ \text{V}$, $50\ \text{Hz}$ supply. Calculate:- (i) circuit current (ii) phase angle (iii) Power factor (iv) power consumed (v) voltage drop across resistance and inductance [6]
- b) Prove that current in purely inductive circuit lags applied voltage by 90° . [4]
- c) Draw impedance triangle, write formula for impedance and phase angle and nature of p.f. for series R-C circuit. [4]

OR

- Q4) a) A series R-C circuit consisting of a resistance of $50\ \Omega$ and a capacitor of $100\ \mu\text{F}$ is connected across $230\ \text{V}$, $50\ \text{Hz}$ ac supply, calculate: i) Impedance ii) Power factor iii) Current. Draw phasor diagram. [6]
- b) Define with reference to alternating quantities varying sinusoidally i) Form factor ii) Peak factor. Obtain their values for sinusoidal waveform. [4]
- c) Prove that current in purely capacitive circuit leads applied voltage by 90° . [4]