

Total No. of Questions – [4]

Total No. of Printed Pages 02

G.R. No. _____

Paper Code - U117-104A(T2)

October
SEPTEMBER 2017 / IN - SEM (T2)

F. Y. B.TECH. (COMMON) (SEMESTER - I)

**COURSE NAME: Basic Electronics Engineering
(2017 PATTERN)**

Time : [1 Hour]

[Max. Marks : 30]


(*) Instructions to candidates:

- 1) Answer Q.1 OR Q.2, Q.3 OR Q.4
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

- Q1 a) Draw and explain the operation of N channel Enhancement-MOSFET with its characteristics. [6]
- b) Draw and Explain working of SCR with V-I characteristics. [6]
- c) For N-channel Enhancement -MOSFET $I_{D(on)} = 500\text{mA}$ at $V_{GS} = 10\text{V}$ and $V_{th} = 1\text{V}$. Find I_D when $V_{GS} = 5\text{V}$. [4]

OR

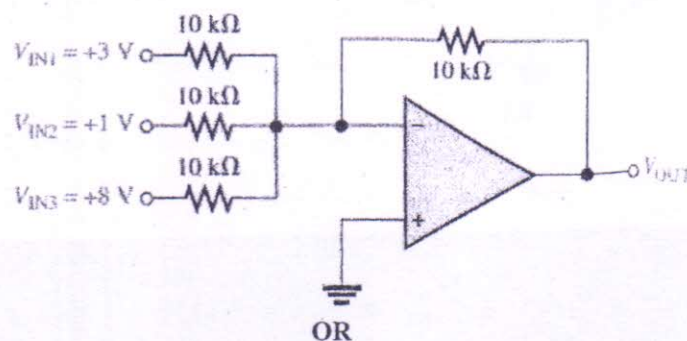- Q2 a) Draw and Explain working of TRIAC with V-I characteristics. [6]
- b) Explain controlled full wave rectifier using SCR with neat diagram and waveforms [6]
- c) Compare features of BJT and MOSFET. Draw symbols of P-Channel and N-Channel Enhancement type MOSFET. [4]
- Q3 a) Draw the circuit of close loop inverting amplifier. Derive the expression for gain of inverting amplifier. Draw input & output waveforms. [6]
- b) Draw the block diagram of Op-Amp. Label the blocks. State the function of each block. [4]
- c) Determine the output voltage in following Figure: [4]



- Q4 a) Draw the circuit of close loop non inverting amplifier. Derive the expression for gain of non inverting amplifier. Draw input & output waveforms. [6]
- b) Explain following parameters of op-amp [4]
- a) Slew rate
 - b) Input offset current & Input bias current.
- c) A certain op-amp has an differential voltage gain of 100,000 and a Common-mode gain of 0.2. Determine the CMRR and express it in decibels. [4]