

Total No. of Questions – [ 4 ]

Total No. of Printed Pages 2

G.R. No.

Paper Code :- U127-104B(T1)

**FEBRUARY 2018 / IN - SEM (T1)**

**F. Y. B.TECH. (COMMON) (SEMESTER - II)**

**COURSE NAME : BASIC ELECTRICAL ENGINEERING**

**(2017 PATTERN)**


Time : [1 Hour]

[Max. Marks : 30]

**(\*) Instructions to candidates:**

- 1) Answer Q.1 OR Q.2, Q.3 OR Q.4
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

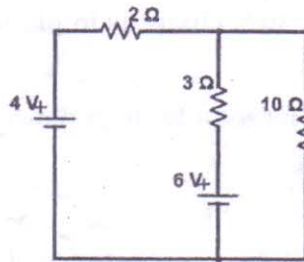Q 1) a) Calculate current flowing in  $10\ \Omega$  resistance using Thevenin's theorem for the circuit given below. [6]



b) Using the equations derived from three delta connected resistances into its equivalent star, derive the equations to convert these three star connected resistances into its equivalent delta circuit. [6]

c) Define following terms with suitable examples:

1. Linear network


2. Non-linear network

[4]

OR

Q2) a) State and explain Kirchhoff's laws. [6]

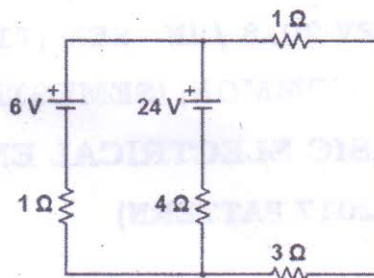- b) Using superposition theorem, find current flowing through  $4\ \Omega$  resistance for the network shown. [6]



- c) Define following terms with suitable examples:

1. Unilateral network
  2. Bilateral network
- [4]

- Q3) a) A coil having resistance of  $10\ \Omega$  and an inductance of  $0.2\ \text{H}$  is connected to  $220\ \text{V}$ ,  $50\ \text{Hz}$  supply. Calculate:- (i) Impedance (ii) Phase angle (iii) Power factor (iv) Current (v) Power consumed [6]

- b) Prove that current in purely resistive circuit is in phase with applied AC voltage. [4]

- c) Draw impedance triangle, write formula for impedance and phase angle and nature of p.f. for series R-L circuit. [4]

OR

- Q4) a) A series R-C circuit consisting of a resistance of  $8\ \Omega$  and a capacitor of  $50\ \mu\text{F}$  is connected across  $200\ \text{V}$ ,  $50\ \text{Hz}$  ac supply, calculate: i) Impedance ii) Voltage drop across resistance iii) Voltage drop across capacitance. [6]

- b) Define terms:

1. Active Power
2. Reactive Power

Also write formula along with their units. [4]

- c) Draw circuit diagram and phasor diagram for series R-C circuit connected to an alternating voltage source. [4]