

**FEBRUARY 2018 / IN - SEM (T1)**  
**F. Y. B.TECH. (COMMON) (SEMESTER - II)**  
**COURSE NAME: Basic Electronics Engineering**  
**(2017 PATTERN)**


Time :[1 Hour]

[Max. Marks : 30]


(\*) Instructions to candidates:

- 1) Answer Q.1 OR Q.2, Q.3 OR Q.4
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

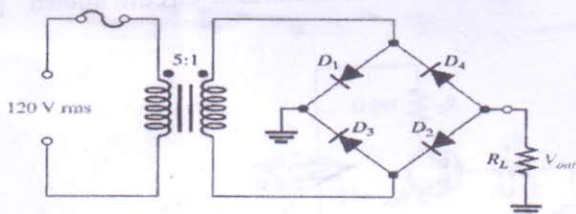- Q1 a)** Draw the output voltage waveform, calculate average output voltage and PIV of the rectifier shown in figure below. The Input voltage at primary of transformer is 120Vrms. [6]



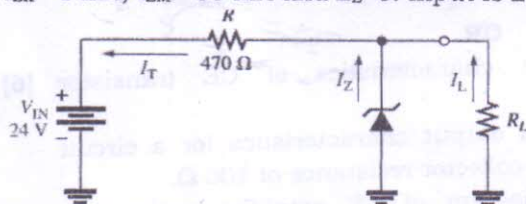- b)** Determine the minimum and maximum currents for which Zener diode shown in figure below that will maintain regulation. What is the minimum value of the  $R_L$  that can be used? Given  $V_Z=12V$ ,  $I_{ZK}=1\text{ mA}$ ,  $I_{ZM}=50\text{ mA}$  and  $Z_Z=0$ . Input is 24 V. [6]




- c)** Explain why Photo diode always operated in reverse bias mode? [4]  
What is dark current?

**OR**


- Q2 a)** Draw the neat circuit diagram and explain in detail working of full wave Bridge rectifier. Derive the expression for DC output voltage. [6]
- b)** A certain full-wave rectifier has a peak output voltage of 30 V. A 50  $\mu\text{F}$  capacitor filter is connected to the rectifier. Calculate the peak-to-peak ripple voltage, the dc output voltage and ripple factor developed across a load resistance of 600  $\Omega$ . Assume supply frequency to be 60 Hz. [6]
- c)** i) For a certain rectifier,  $V_{NL}=15.5\text{ V}$ ,  $V_{FL}=14.9\text{ V}$  Calculate Percentage Load regulation. [4]

ii) In certain Zener regulator, output voltage changes by 0.2V when input voltage goes from 5 V to 10 V. What is percentage line regulation?

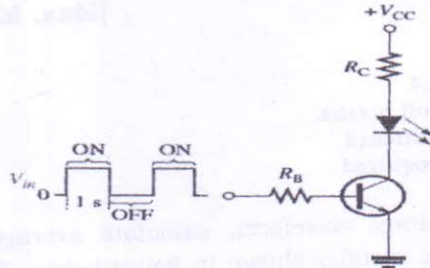- Q3 a)** For a transistorized flasher circuit shown below, calculate the magnitude of the square wave for proper operation of circuit. LED requires 30mA to emit sufficient light.  $V_{CC} = 9\text{ V}$ ,  $V_{CE(sat)} = 0.3\text{ V}$ ,  $R_C = 220\ \Omega$ ,  $R_B = 3.3\text{ K}\Omega$ ,  $\beta_{DC} = 50$ , and  $V_{LED} = 1.6\text{ V}$ . Use base current which is two times of minimum base current. [6]



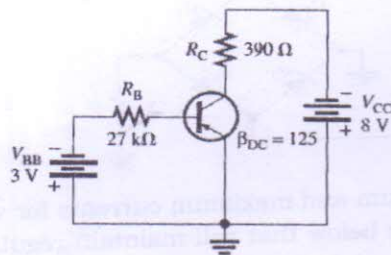- b)** Find all  $I_B$ ,  $I_C$ ,  $V_{CE}$  and  $V_{CB}$  in the transistorised circuit shown below. [4]



- c)** Draw the circuit diagram and explain in detail working of transistor as a switch. [4]

**OR**

- Q4 a)** Draw Input and output characteristics of CE transistor configuration. [6]

Draw the DC load line on output characteristics for a circuit supplied with  $V_{CC} = 10\text{ V}$  and collector resistance of  $100\ \Omega$ .

- b)** Draw the neat circuit diagram of CE amplifier using npn transistor. Derive the expression for voltage gain. [4]
- c)** Determine  $I_{C(sat)}$  for the transistor shown in figure below. What is the value of  $I_B$  necessary to produce saturation? What minimum value of  $V_{IN}$  is necessary for saturation? Assume  $V_{CE(sat)} = 0\text{ V}$ . [4]

