

Total No. of Questions - [4]

Total No. of Printed Pages 4

G.R. No.

Paper Code - U127-104B (T2)

MARCH 2018 / IN - SEM (T2)

F. Y. B.TECH. (COMMON) (SEMESTER - II)

COURSE NAME : BASIC ELECTRICAL ENGINEERING

(2017 PATTERN)

Model answer and scheme of marking

Time : [1 Hour]

[Max. Marks : 30]

(*) Instructions to candidates:

- 1) Answer Q.1 OR Q.2, Q.3 OR Q.4
- 2) Figures to the right indicate full marks.

Q 1) a) $(P_T)_{3-\phi} = 8 \text{ kW} = 8000 \text{ W}$, $\cos \phi = 0.8$,
 $V_L = 460 \text{ V}$ $\therefore \phi = 36.86^\circ \therefore \sin \phi = 0.6$
for Δ $V_{ph} = V_L / \sqrt{3} = 460 / \sqrt{3} = 265.58 \text{ V}$
 $Z_{ph} = V_{ph} / I_{ph}$
 $P_T = \sqrt{3} V_L I_L \cos \phi$ $8000 = (\sqrt{3})(460) I_L (0.8)$
 $\therefore I_L = 12.55 \text{ A} = I_{ph}$
 $\therefore Z_{ph} = V_{ph} / I_{ph} = 265.58 / 12.55 = 21.16 \Omega$
 $R_{ph} = Z_{ph} \cos \phi = 16.93 \Omega$ (3M) $X_{Lph} = I_{ph} \sin \phi = 12.69 \Omega$

b) Neat connection diagram for a three phase balanced delta connected

resistive load with correct marking of line currents, line voltages,
phase voltages and phase currents.

03M

Neat phasor diagram for a three phase balanced delta connected
resistive load with correct marking of line currents, line voltages,
phase voltages and phase currents.

03M

c) definition of Balanced load

02M

definition of unbalanced load

02M

OR

Q2) a) $W_1 = 10.4 \text{ kW}$, $W_2 = -3.4 \text{ kW}$, $V_L = 400 \text{ V}$

$$\text{P.f.} = \cos \phi = \cos \left\{ \tan^{-1} \left(\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right) \right\} = \cos \left\{ \tan^{-1} \left(\frac{\sqrt{3}(10.4 - (-3.4))}{10.4 + (-3.4)} \right) \right\}$$

$$\text{P.f.} = \cos \left\{ \tan^{-1} \left(\frac{23.90}{7} \right) \right\} = \cos \left\{ \tan^{-1} (3.41) \right\} = \cos (73.67^\circ)$$

$$\text{P.f.} = \cos (73.67^\circ) = 0.28 \quad \text{--- (02M)}$$

$$(P_T)_{3-\phi} = W_1 + W_2 = 10.4 - 3.4 = 7 \text{ kW} = 7000 \text{ W} \quad \text{--- (02M)}$$

$$(P_T)_{3-\phi} = \sqrt{3} V_L I_L \cos \phi \quad 7000 = (\sqrt{3})(400) I_L (0.28)$$

$$\therefore I_L = 7000 / 193.98 = 36.08 \text{ A} \quad \text{--- (02M)}$$

b) Phasor diagram (any one line voltage/ all three line voltages) 03M

Derivation steps for relation between line and phase voltages with correct relation 02M

$$V_L = \sqrt{3} V_{ph}$$


01M

c)
$$\left. \begin{aligned} (P_T)_{3-\phi} &= \sqrt{3} V_L I_L \cos \phi \\ &= 3 V_{ph} I_{ph} \cos \phi \end{aligned} \right\} \quad \text{--- (01M)}$$

$$(Q_T)_{3-\phi} = \sqrt{3} V_L I_L \sin \phi = 3 V_{ph} I_{ph} \sin \phi \quad \text{--- (01M)}$$

$$(S_T)_{3-\phi} = \sqrt{3} V_L I_L = 3 V_{ph} I_{ph} \quad \text{--- (01M)}$$

Power triangle for lagging p.f.

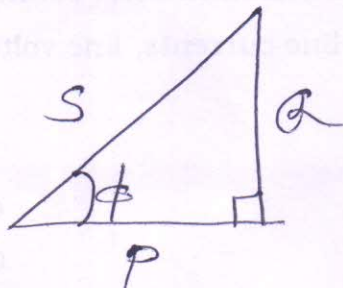

--- (01M)

Q3) a) $P_i = 1.5 \text{ kW}$ $(P_{Fe})_{cu} = 1 \text{ kW}$

① $n = \frac{A.L.}{F.L.} = \frac{F.L.}{F.L.} = 1$ $\cos \phi = 1$

$\% \eta = \frac{n (KVA_{Rating}) \times 10^3 \times 105 \phi \times 100}{F.L. n (KVA_{Rating}) \times 10^3 \cos \phi + P_i + n^2 (P_{cu})_{F.L.}} = \frac{(1)(100 \times 10^3)(1) \times 100}{(1^2) + 1.5 \times 10^3 + (1)^2(1000)} = 97.5\%$

② $n = \frac{A.L.}{F.L.} = \frac{H.L.}{F.L.} = \frac{1}{2}$ $\cos \phi = 0.8$

$\% \eta = \frac{(\frac{1}{2})(100 \times 10^3)(0.8) \times 100}{(\frac{1}{2})(100 \times 10^3)(0.8) + (1.5 \times 10^3) + (\frac{1}{2})^2(1000)} = 95.81\%$

b) 4 correct points 1 mark for each point

c) diagram of CT	01M
application of CT	01M
diagram of PT	01M
application of PT	01M

OR

Q4) a) $\frac{E_2}{E_1} = \frac{N_2}{N_1}$ $\frac{200}{3300} = \frac{80}{N_1} \therefore N_1 = 1320$ — (01M)

$(I_1)_{F.L.} = \frac{KVA_{Rating} \times 10^3}{V_1} = \frac{100 \times 10^3}{3300} = 30.30 \text{ A}$ — (02M)

$(I_2)_{F.L.} = \frac{KVA_{Rating} \times 10^3}{V_2} = \frac{100 \times 10^3}{200} = 500 \text{ A}$ — (02M)

$E_1 = 4.44 f \phi_m N_1$

$f_m = \frac{E_1}{4.44 f N_1} = \frac{3300}{(4.44)(50)(1320)}$ — (02M)

$\phi_m = 11.26 \text{ mwb}$ — (01M)

b) i) Definition of Voltage Regulation

1M

Formula

1M

$$\% \text{ reg.} = [E_2 - V_2 / E_2] * 100$$

ii) Definition of Efficiency

1M

Formula

1M

$$\% \eta = n[V_2 I_2 \cos \phi] / \{n[V_2 I_2 \cos \phi] + P_i + n^2 P_{cu}\} * 100$$

c) i) types of losses occurring in the transformer 1M

ii) their location - 1M

iii) whether constant or variable loss - 1M

iv) how to minimize it - 1M