

Total No. of Questions - [5]

Total No. of Printed Pages 02

G.R. No.

U118-104A (BE-FS)

DEC. 2018 / ENDSEM

F. Y. B. TECH. (COMMON) (SEMESTER - I/II)

COURSE NAME: Basic Electronics Engineering ET10174A
(2017 PATTERN)

Time: [2 Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) Answer Q.1 OR Q.2, Q.3 OR Q.4 and Q.5
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

- Q1 a) State and prove Demorgan's theorems, with the help of logical diagrams. [6]
b) Construct basic gates NOT, OR and AND gate using NAND gate only. [6]
c) Explain working of gated S-R flip flop with block diagram and truth table [4]

OR

- Q2 a) Define and draw NAND gate and NOR gate. For both gates develop the truth table for two inputs based on their logical expression [6]
b) Explain the working of 4:1 MUX and 1:4 De-MUX with block diagram and truth table. [6]
c) State and prove Commutative and Associative laws used in Boolean Algebra. [4]

- Q3 a) Draw and explain the block diagram of basic instrumentation system. [6]
b) Compare active and passive transducers. [4]
c) Define linearity, accuracy, sensitivity and repeatability of transducer used in an instrumentation system. [4]

OR

- Q4 a) What is RTD? Explain its construction and working principle. Draw the circuit diagram for measurement of temperature using RTD. [6]
b) What is primary and secondary transducer? State two examples of each. [4]
c) What is transducer? Give its classification based on its electrical parameters. [4]

Q.5) Attempt following multiple choice questions: [2x10=20 marks]

- a) If the ac supply is 60 Hz, what will be the ripple frequency out of the full-wave rectifier? [2]
a) 50 Hz b) 60 Hz c) 120 Hz d) 100 Hz
- b) The no load output voltage of half wave rectifier is [2]
a) $0.318 V_{peak}$ b) $2 V_{peak}$ c) $0.636 V_{peak}$ d) $0.5 V_{peak}$
- c) For what kind of amplifications, the active region of the common-emitter configuration is used? [2]
a) Voltage b) Current c) Power d) All of the above
- d) In the active region for a CE transistor configuration, the collector-base junction is _____-biased, the base-emitter is _____-biased. [2]
a) reverse, forward b) forward, reverse
c) forward, forward d) reverse, reverse
- e) Which of the following devices does not have a cathode terminal? [2]
a) SCR b) PN Junction Diode c) Triac d) Zener diode
- f) If $I_E = 5.34 \text{ mA}$, $I_B = 475 \mu\text{A}$, current gain beta of BJT will be [2]
a) 10.24 b) 9.24 c) 10.48 d) 11.24
- g) Which of the following applies to MOSFETs? [2]
a) Current controlled device
b) Device with low input impedance
c) Voltage controlled device
d) None of the above
- h) It is the insulating layer of _____ in the MOSFET construction that accounts for the very desirable high input impedance of the device. [2]
a) SiO b) GaAs c) SiO₂ d) HCl
- i) An non inverting operational amplifier with gain of 101 is applied with 1V input voltage, the output voltage will be [2]
a) +Vcc b) -Vcc c) 101 V d) -101 V
- j) The 7805 regulator IC provides _____ [2]
a) 5V b) -5V c) 12V d) -12V