

(11)

Total No. of Questions - [08]

Total No. of Printed Pages 03

G.R. No.	
----------	--

U218-135(ESE)

DECEMBER 2018/ENDSEM
S. Y. B. TECH. (E&TC) (SEMESTER - I)
COURSE NAME: DIGITAL ELECTRONINCS
COURSE CODE: ETUA21175
(PATTERN 2017)

Time: [2 Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

Q.1) a) Use a K-map to simplify each expression to minimum POS form: [6]
 i) $Y = (A + \bar{B} + C + \bar{D})(\bar{A} + B + \bar{C} + D)(\bar{A} + \bar{B} + \bar{C} + \bar{D})$
 ii) $Y = (X + \bar{Y})(W + \bar{Z})(\bar{X} + \bar{Y} + \bar{Z})(W + X + Y + Z)$

OR


b) Using a K-map, convert the following standard POS expression [6]
 into a minimum POS expression, a standard SOP expression,
 and a minimum SOP expression.
 $Y = (\bar{A} + \bar{B} + C + D)(A + \bar{B} + C + D)(A + B + C + \bar{D})(A + B + \bar{C} + D)$

Q.2) a) Design a logic circuit to produce a HIGH output only if the [6]
 input, represented by a 4-bit binary number, is greater than
 twelve or less than three. Write the truth table and then draw
 the logic diagram.

OR


b) Develop a combinational system which has three input and [6]
 produces output Y. Whenever even number of ones are detected
 by the system Output Y=1. Write the truth table and draw its
 logic diagram.

 Q.3) a) Draw the Q output relative to the clock for a D flip-flop with the [6]
 inputs as shown in fig. Assume positive edge triggering and Q
 initially LOW.



OR

 - b) The waveform in shown in fig. below is applied to the J, K, and clock inputs as indicated. Determine the Q output, assuming that the flip-flop is initially RESET. [6]



- Q.4) a) Design a shift register with suitable flip-flops that will follow the sequence 1000, 0100, 0010, 0001, 0000...write its truth table and draw its logic diagram. [4]

OR

- b) Design a synchronous circuit using suitable flip-flop which will follow the sequence 00, 01, 10, 11, 00... write its truth table and draw its logic diagram. [4]


- Q.5) a) A certain IC has two input CMOS NOR gates. Draw the internal diagram of CMOS NOR gate and explain its working for all the possible combination of inputs. [6]

- b) Draw the architecture of CPLD and write its parameters. [4]

- c) Three open-collector AND gate are connected in a wired AND configuration as shown in figure. Assume that the wired-AND circuit is driving four standard TTL inputs (-1.6 mA each). [4]

i) Write the logic expression for X.

 ii) Determine the minimum value of R_p if $I_{OL(max)}$ for each gate is 30 mA and $V_{OL(max)}$ is 0.4 V




OR

- Q.6) a) A certain IC has four two input TTL NAND gates. Draw the internal structure of TTL NAND gate and explain its working for all the possible combinations of inputs. [6]

- b) A certain IC is of CMOS NOT gates. Draw the internal structure of CMOS inverter gate and explain its working for all possible combinations on input. [4]

 - c) Determine the value of the limiting resistor, R_L , in the open-collector circuit of figure if the LED current is to be 20 mA. Assume a 1.5 V drop across the LED when it is forward-biased and a LOW-state output voltage of 0.1 V at the output of the gate. [4]



- Q.7) a) A long sequences of pulses enters a synchronous sequential circuit which is required to produce an output $z=1$, whenever the sequence 1111 occurs. Using suitable flip-flop design the non-overlapping system and draw its logic diagram. [6]
- b) With suitable example explain the following terms: [4]
1. State Table 2. State diagram
- c) Write truth table, excitation table for SR flip-flop and draw its state diagram [4]

OR

- Q.8) a) A long sequences of pulses enters a synchronous sequential circuit which is required to produce an output $z=1$, whenever the sequence 1010 occurs. [6]
- b) Write truth table, excitation table for JK flip-flop and draw its state diagram [4]
- c) Design a sequence detector which will produce output $z=1$, whenever the sequence 110 occurs. Using suitable flip-flop design the non-overlapping system and draw its logic diagram. [4]