

G.R. No.

U218-136 (ESE)

DECEMBER 2018/ENDSEM**S. Y. B. TECH. (E & TC) (SEMESTER - I)****COURSE NAME: NETWORK THEORY****COURSE CODE: ETUA21176****(PATTERN 2017)**

Time: [2 Hours]


[Max. Marks: 50]

(*) Instructions to candidates:

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

Q1 a) For the circuit of Fig. below, determine all four nodal voltages.

[6]

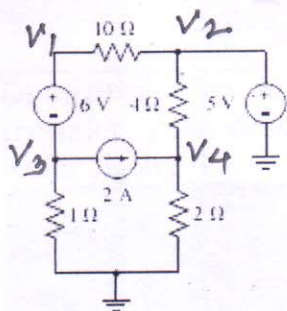**1.5 M for each node voltage**

We define v_1 at the top left node; v_2 at the top right node; v_3 the top of the $1\ \Omega$ resistor; and v_4 at the top of the $2\ \Omega$ resistor. The remaining node is the reference node.

We may now form a supernode from nodes 1 and 3. The nodal equations are:

$$-2 = \frac{v_3}{1} + \frac{v_1 - v_2}{10} \quad [1]$$

$$2 = \frac{v_4}{2} + \frac{v_4 - v_2}{4} \quad [2]$$


By inspection, $v_2 = 5\text{ V}$ and our necessary KVL equation for the supernode is $v_1 - v_3 = 6$. Solving,

$$\begin{aligned} v_1 &= 4.019\text{ V} \\ v_2 &= 5\text{ V} \\ v_3 &= -1.909\text{ V} \\ v_4 &= 4.333\text{ V} \end{aligned}$$

OR

- Q1 b) Determine the voltage V_x in the circuit of following Fig, and the power supplied by the 1 A source. [6]

$V_x = 3M$, Power = 3M

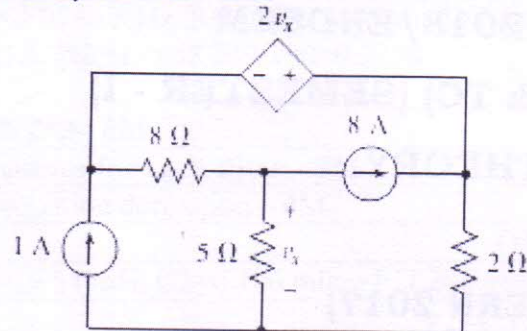

A strong choice for the reference node is the bottom node, as this makes one of the quantities of interest (v_x) a nodal voltage. Naming the far left node v_1 and the far right node v_3 , we are ready to write the nodal equations after making a supernode from nodes 1 and 3:

$$1 + 8 = \frac{v_1 - v_x}{8} + \frac{v_3}{2} \quad [1]$$

$$-8 - \frac{v_x - v_1}{8} + \frac{v_x}{5} \quad [2]$$

Finally, our supernode's KVL equation: $v_3 - v_1 = 2v_x$

Solving, $v_1 = 31.76$ V and $v_x = -12.4$ V

Finally, $P_{\text{supplied } 1A} = (v_1)(1) = 31.76$ W

- Q2 a) Find the current through branch ab of the network in figure 3 using thevenin's theorem. Let $V = 10$ V
 $R_{th} = 3M$ $V_{th} = 3M$ [6]

Obtain the voltage across open circuit called V_{TH} or V_{OC} .
Applying KVL to the loop we get,

$$-5I - 3I - j4I + 10 = 0$$

$$\therefore -I(8 + j4) = -10$$

$$\therefore I = \frac{10 \angle 0^\circ}{(8 + j4)} = \frac{10 \angle 0^\circ}{8.944 \angle 26.56^\circ} = 1.118 \angle -26.56^\circ \text{ A}$$

The open circuit voltage is the voltage across the impedance $3 + j4 \Omega$, hence

$$V_{TH} = I \times (3 + j4) = (1.118 \angle -26.56^\circ) \times (5 \angle 53.13^\circ) = 5.59 \angle +26.56^\circ \text{ V}$$

Step 3 :

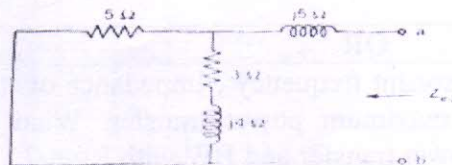


Fig. 2.29 (b)

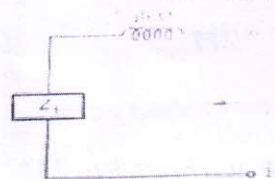


Fig. 2.29 (c)


Calculate the equivalent impedance across the terminals a-b, replacing the source by its internal impedance or short circuit.

Now the 5Ω resistance and the impedance $3 + j4$ are in parallel.

$$Z_{eq} = \frac{5 \times (3 + j4)}{5 + (3 + j4)} = \frac{5 \angle 0^\circ \times 5 \angle 53.13^\circ}{(8 + j4)} = \frac{25 \angle 53.13^\circ}{8.944 \angle 26.56^\circ} = 2.795 \angle 26.56^\circ = 2.5 + j1.25 \Omega$$

$$Z_{eq} = j5 + 2.5 + j1.25 = 2.5 + j6.25 \Omega$$

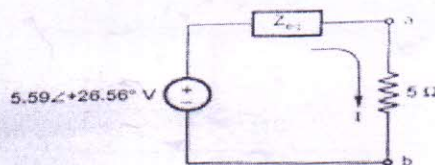Step 4 : Thevenin's equivalent circuit is,



Hence the current through the branch a-b is,

$$I = \frac{V_{TH}}{5 + [Z_{eq}]} = \frac{5.59 \angle 26.56^\circ}{5 + 2.5 + j6.25} = \frac{5.59 \angle 26.56^\circ}{7.5 + j6.25} = \frac{5.59 \angle 26.56^\circ}{9.7628 \angle 39.8^\circ} = 0.5725 \angle -13.24^\circ \text{ A}$$

This is the required current through branch a-b.

OR

- Q2 b) Determine the impedance to be connected at ab for maximum power transfer. Also determine power delivered to the load impedance at ab. Refer figure 4 [6]

Impedance=3M, Power=3M

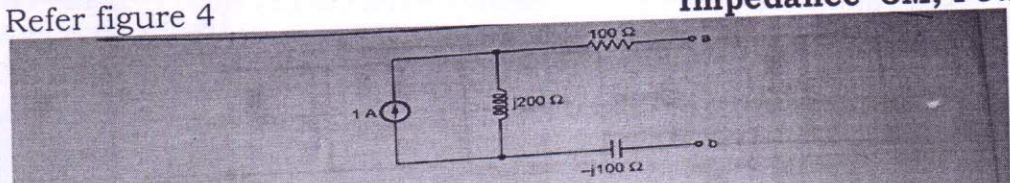


Fig. 2.70

Solution : To find load impedance for P_{max} , find Z_{eq} . So open the current source.

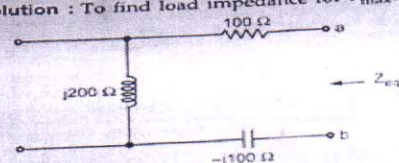


Fig. 2.70 (a)

$$\therefore Z_{eq} = 100 + j200 - j100 = 100 + j100 \Omega$$

Hence Z_L for P_{max} is conjugate of Z_{eq} so,

$$Z_L = Z_{eq}^* = 100 - j100 \Omega \text{ for } P_{max}$$

Connecting $Z_L = Z_{eq}^*$, the circuit reduces as shown in the Fig. 2.70 (b).

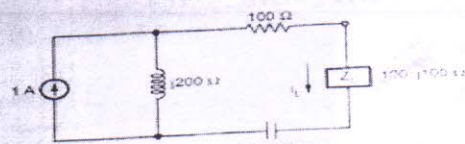


Fig. 2.70 (b)

The generator current is still 1 A at an angle 0° .

I_L can be calculated from the current division in parallel circuit,

$$I_L = 1 \times \frac{j200}{(j200 + 100 + 100 - j100 - j100)} = \frac{j200}{200} = 1 \angle 90^\circ \text{ A}$$

Power delivered to the load is,

$$P_{max} = I_L^2 R_L = (1)^2 \times (100) = 100 \text{ W}$$

Q3	a)	An inductor coil having resistance 20 ohm and an inductance 0.02 H is connected in series with a capacitor of 0.02 micro farad. Determine Quality factor of the coil, Resonant Frequency and two half power frequencies. $F_0 = \frac{1}{2\pi\sqrt{LC}} = 7.957 \text{ KHz} \quad \mathbf{2M}$ $Q_0 = \frac{\omega_0 L}{R} = 50 \quad BW = \frac{R}{2\pi L} = 79.57 \text{ Hz} \quad \mathbf{-2M}$ $F_1 = F_0 - \frac{BW}{2} = 7.87 \text{ KHz} \quad \mathbf{-1M}$ $F_2 = F_0 + \frac{BW}{2} = 8.03 \text{ KHz} \quad \mathbf{1M}$	[6]
OR			
Q3	b)	Refer following Fig 5. Determine resonant frequency, Impedance of the antiresonant circuit Z_{ar} and resistance R_g for maximum power transfer. What is the relation between BW of the circuit at Max. Power transfer and BW with $R_g=0$? $F_{ar} = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{1}{Q_0^2}} = 1.05 \text{ MHz} \quad \mathbf{2M}$ $Q_0 = 7$ $Z_{ar} = \frac{L}{CR} = 111.45 \text{ Kohm} = R_g \quad \mathbf{2M}$ <i>Bw with R_g matched with $Z_{ar} = 2$ BW without R_g</i> $\mathbf{2M}$	[6]
OR			
Q4	a)	$i_T(0^-) = \frac{36}{10 + (4 \parallel 4)}$ $= \frac{36}{10 + 2} = 3 \text{ A}$ $i(0^-) = 3 \times \frac{4}{4+4} = 1.5 \text{ A}$ Since current through the inductor cannot change instantaneously, $i(0^+) = 1.5 \text{ A}$ For $t > 0$, the transformed network is shown in Fig. 9.43 Applying KVL to the Mesh for $t > 0$, $-4I(s) - 4I(s) - 2sI(s) + 3 = 0$ $8I(s) + 2sI(s) = 3$ $I(s) = \frac{3}{2s + 8} = \frac{1.5}{s + 4}$ Taking the inverse Laplace transform, $i(t) = 1.5 e^{-4t} \quad \text{for } t > 0$	[4]
OR			

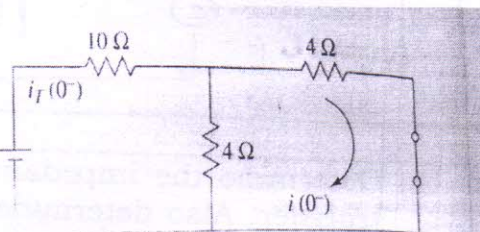


Fig. 9.42

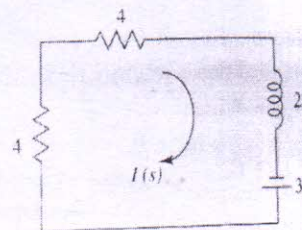


Fig. 9.43

b)

Solution At $t = 0^-$, steady-state condition is reached. Hence, the capacitor acts as an open circuit.

$$v(0^-) = 6 \times \frac{2}{4+2} = 2 \text{ V}$$

Since voltage across the capacitor cannot change instantaneously,

$$v(0^+) = 2 \text{ V}$$

For $t > 0$, the transformed network is shown in Fig. 9.37.

Applying KCL at Node for $t > 0$,

$$\frac{V(s)}{6} + \frac{V(s) - \frac{2}{s}}{\frac{1}{s}} + \frac{V(s)}{2} = 0$$

$$V(s) \left[\frac{2}{3} + s \right] = 2$$

$$V(s) = \frac{2}{s + \frac{2}{3}}$$

Taking the inverse Laplace transform,

$$v(t) = 2 e^{-(2/3)t}$$

for $t > 0$

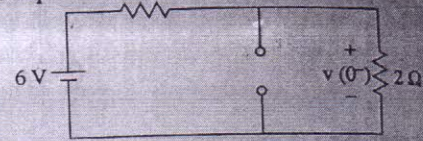


Fig. 9.36

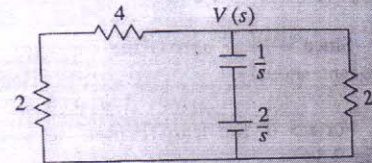



Fig. 9.37

[4]

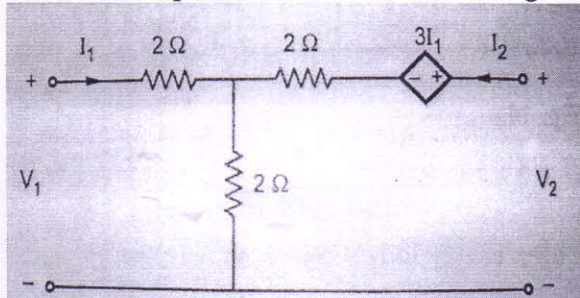Q5

a)

Determine Z parameters for the following network (Fig 8)



With port 2 open $I_2 = 0$ ----- 3M

$$-2I_1 - 2I_1 + V_1 = 0 \text{ and } V_2 = 3I_1 + 2I_1$$

$$Z_{11} = V_1/I_1 = 4 \text{ ohms, } Z_{21} = V_2/I_1 = 5 \text{ ohms}$$


With port 1 open $I_1 = 0$ ----- 3M

$$-2I_2 - 2I_2 + V_2 = 0 \text{ and } V_1 = 2I_2$$

$$Z_{22} = 4 \text{ ohms and } Z_{12} = 2 \text{ ohms}$$

[6]

b)

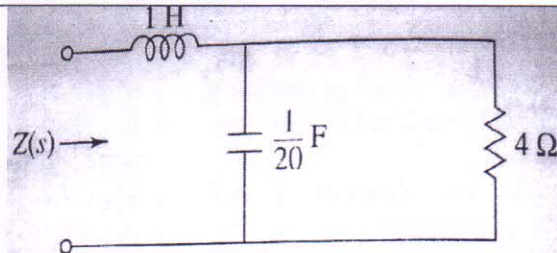


$$Z(s) = \frac{s^2 + 5s + 20}{(s+5)} \quad \text{Zeros at } s = -2.5 + j3.71 \text{ and } s = -2.5 - j3.71$$

$$\text{Pole at } s = -5 \text{ ----- 2M plot-2M}$$

[4]

c)

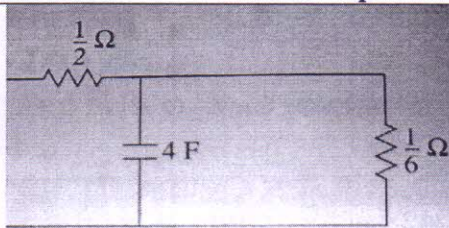

$$Y(s) = \frac{(2s+3)}{(s+2)} - 4M$$

[4]

OR

Q6

a)

$$V_1/I_1 = (2s^2 + s + 1)/s \text{ and } V_2/V_1 = 2s^2/(2s^2 + s + 1) - 3M \text{ each}$$

[6]

	b)	expressions for Z parameters in terms of Y parameters	[4]
	c)	transmission parameters for T network consisting of each series arm 100 ohm and shunt arm 200 ohm each parameter – 1M $V1/V2=3/2$, $I1/V2= 1/200$ etc.	[4]
Q7	a)	$f_c = 2.0546$ KHz, $R_0 = 774.596$ ohm, $Z_{oT} @ 1\text{KHz} = 676.596$ ohm $\beta @ 1\text{K} / \beta @ 5\text{k} = 58.249/180 = 0.3236$ each 2*3= 6M	[6]
	b)	all curves for each filter – 2M	[4]
	c)	Z_0 equation derivation – 4M	[4]
OR			
Q8	a)	$L1 = 26.54$ mH, $C2 = 0.106$ micro F, $L2 = 5.968$ mH, $C1 = 0.023$ micro F each 1.5M	[6]
	b)	$Z_0 = \sqrt{Z_{oc}Z_{sc}}$	[4]
	c)	$R1/2 = 490.90$ ohm ----2M and $R2 = 121.22$ ohm ---- 2 M	[4]