

Total No. of Questions – [8]

Total No. of Printed Pages-3

G.R. No.

U218-136(ESE)

DECEMBER 2018/ENDSEM

S. Y. B. TECH. (E & TC) (SEMESTER - I)

COURSE NAME: NETWORK THEORY

COURSE CODE: ETUA21176

(PATTERN 2017)

Time: [2 Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

Q1 a) For the circuit of Fig 1. below, determine all four nodal voltages. [6]

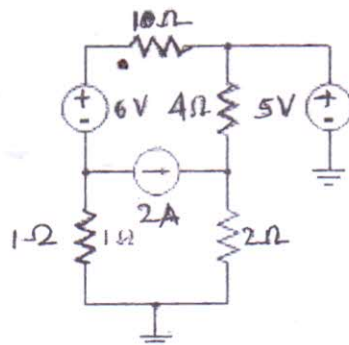


FIG. 1

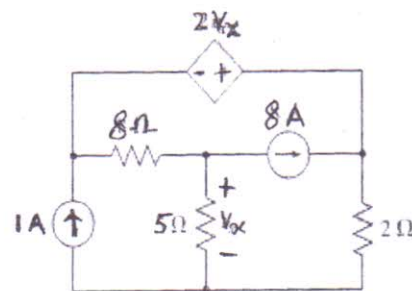


FIG. 2

OR

Q1 b) Determine the voltage V_x in the circuit of Fig 2, and the power supplied by the 1 A source. [6]

Q2 a) Find the current through branch ab of the network in figure 3 using thevenin's theorem. Let $V=10$ V [6]

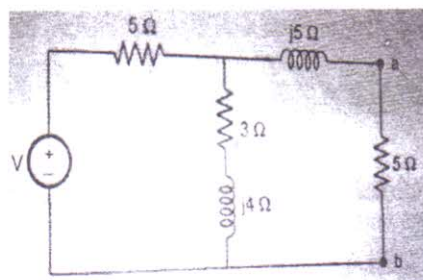


FIG. 3

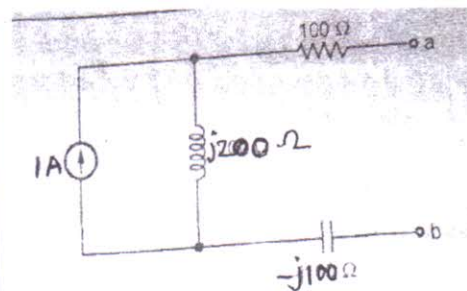


FIG. 4

OR

Q2 b) Determine the impedance to be connected at ab for maximum power transfer. Also determine power delivered to the load impedance at ab. Refer figure 4 [6]

- Q3 a) An inductor coil having resistance 20 ohm and an inductance 0.02 H is connected in series with a capacitor of 0.02 micro farad. Determine Quality factor of the coil, Resonant Frequency and two half power frequencies. [6]

OR

- Q3 b) Refer following Fig 5. Determine resonant frequency, Impedance of the antiresonant circuit Z_{ar} and resistance R_g for maximum power transfer. What is the relation between BW of the circuit at Max. Power transfer and BW with $R_g=0$? ($L=1.284$ mH, $R=2.23$ Kohms, $C=10$ pF) [6]

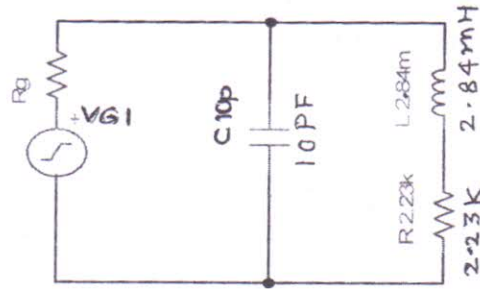


FIG. 5

- Q4 a) The network shown in fig. 6 has acquired the steady state with switch closed for $t < 0$. The switch is opened at $t=0$. Obtain the equation for $i(t)$ [4]

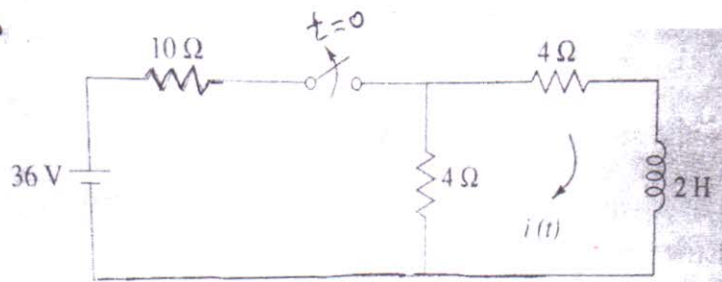


FIG. 6

OR

- Q4 b) In network the switch is moved from a to b at $t=0$ find $v(t)$. Refer fig 7 [4]

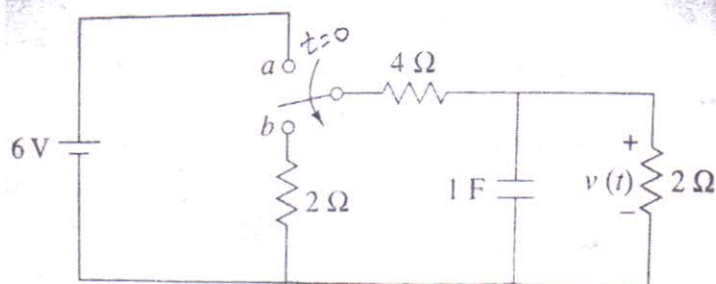


FIG 7

- Q5 a) Determine Z parameters for the following network (Fig 8) [6]

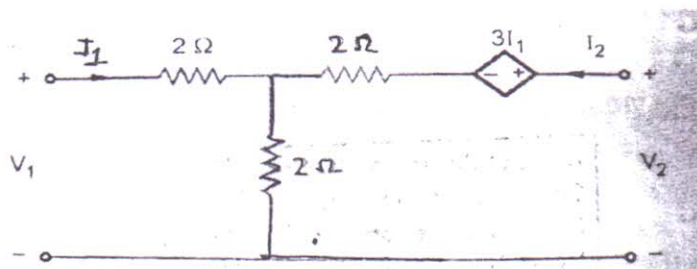


FIG 8

- b) Plot pole zero plot for driving point impedance for the network shown in fig 9 [4]

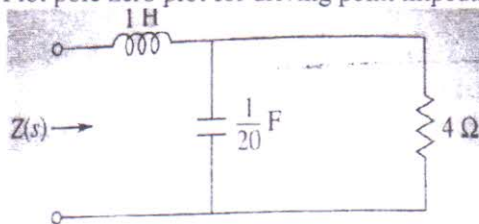


FIG 9


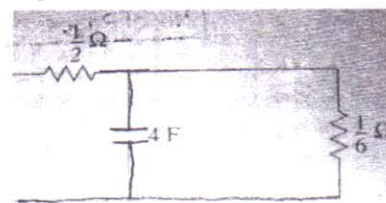


FIG 10

- c) Determine $Y(s)$ i.e. driving point admittance for the network shown in fig 10. [4]

OR

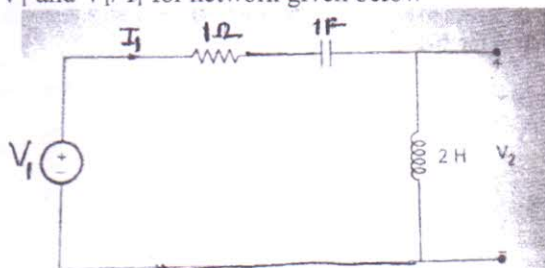- Q6 a) Determine V_2/V_1 and V_1/I_1 for network given below [6]



- b) Derive the expressions for Z parameters in terms of Y parameters [4]
 c) Determine transmission parameters for T network consisting of each series arm 100 ohm and shunt arm 200 ohm [4]

- Q7 a) In constant K LPF, Each series arm consists of inductor of 60mH and shunt arm consists of capacitor of 0.2 micro farad. Determine design impedance, cut off frequency, Characteristics impedance Z_{0T} at 1 KHz and ratio of phase constant at 1KHz and phase constant at 5KHz [6]

- b) Draw the characteristics curves for attenuation constant, phase constant and characteristics impedance Z_{0T} for LPF and BPF [4]
 c) Derive the expression for Characteristics impedance of Symmetrical T network [4]

OR

- Q8 a) Design a constant K Band pass filter with cutoff frequencies 4KHz and 10 KHz with design impedance , 500 ohms. [6]

- b) For prototype T network with each series arm $Z_1/2$ and shunt arm Z_2 Prove that $Z_0 = \sqrt{Z_{0C}Z_{0S}}$ [4]
 c) Design T attenuator for 20dB attenuation and design impedance 600 ohms [4]