

1

Total No. of Questions – [08]

Total No. of Printed Pages [02]

G.R. No.

U218-145 (ESE)

DECEMBER 2018/ENDSEM

S. Y. B. TECH. (INFORMATION TECHNOLOGY) (SEMESTER - I)

COURSE NAME: DIGITAL ELECTRONICS AND LOGIC DESIGN

COURSE CODE: ITUA21175

(PATTERN 2017)

Time: [2 Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

Q.1) a) Do the following conversions:

[6 marks]

- i) $(CD6)_{16} = (-----)_{10}$
- ii) $(1234)_{10} = (-----)_8$
- iii) $(25.675)_8 = ()_{16}$

OR

b) Perform following arithmetic using 2's Complement :

[6 marks]

- i) $(6)_{10} - (10)_{10}$
- ii) $(-6)_{10} - (10)_{10}$
- iii) $(-6)_{10} + (10)_{10}$

Q.2) a) List rules of BCD addition with example. Design (Truth Table, K-map, Logic Function, Circuit Diagram) BCD Adder using IC 7483.

[6 marks]

OR

b) Explain 3:8 Decoder IC 74138. Design (Truth Table, Logic Function, Circuit Diagram) Full Adder using IC 74138.

[6 marks]

Q.3) a) Draw pin diagram of IC 74191 & state function table. Design & draw Mod-11 (5 to 15) truncated UP counter using IC 74191.

[6 marks]

OR

b) Draw & Explain 4 bit ring counter with state diagram.

[6 marks]

Q.4) a) Implement the following functions using PLA [4 marks]

$$A(P, Q, R) = \sum m(0, 1, 6, 7)$$

$$B(P, Q, R) = \sum m(1, 2, 4, 6)$$

OR

b) List, draw and explain ASM chart notations. [4 marks]

Q.5) a) What is VHDL? Write features of VHDL. Explain the structure of VHDL module. [6 marks]

b) What is the difference between Sequential and Concurrent execution of VHDL statements? [4 marks]

c) Declare entity and architecture for 4:1 MUX VHDL module. [4 marks]

OR

Q.6) a) List and explain the different VHDL program modeling styles. [6 marks]

b) List any 4 operators used in VHDL code and explain each with example. [4 marks]

c) Declare entity and architecture for 3:8 Decoder VHDL module. [4 marks]

Q.7) a) Draw 8086 architecture and explain each functional block. [6 marks]

b) Compare Microprocessor and Microcontroller with their applications. [4 marks]

c) Draw and explain the Von Neumann architecture. [4 marks]

OR

Q.8) a) Explain 8086 programmer model with neat diagram. [6 marks]

b) Draw and explain the Harvard architecture. [4 marks]

c) List main features of 8051 Microcontroller. [4 marks]