

G.R. No.

OCTOBER 2018/IN-SEM (T1)

S. Y. B. TECH. (E &amp; TC) (SEMESTER - I)

COURSE NAME: NETWORK THEORY

COURSE CODE: ETUA21176

(PATTERN 2017)

Time: [1Hour]


[Max. Marks: 30]

(\*) Instructions to candidates:

- 1) Answer Q.1 OR Q.2 and Q.3 OR Q.4.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

Q1 a) Determine all mesh currents.

[6]

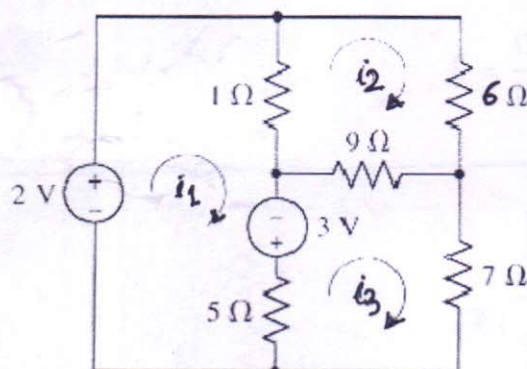**Solution****Three loop equations - 3M****Three currents- 3M**

We need to construct three mesh equations:


$$-2 + (1)(i_1 - i_2) - 3 + 5(i_1 - i_3) = 0 \quad [1]$$

$$(1)(i_2 - i_1) + 6i_2 + 9(i_2 - i_3) = 0 \quad [2]$$

$$5(i_3 - i_1) + 3 + 9(i_3 - i_2) + 7i_3 = 0 \quad [3]$$

Solving,  $i_1 = 989.2 \text{ mA}$ ,  $i_2 = 150.1 \text{ mA}$  and  $i_3 = 157.0 \text{ mA}$ b) Determine  $V_x$  using KCL and KVL equations.


[6]

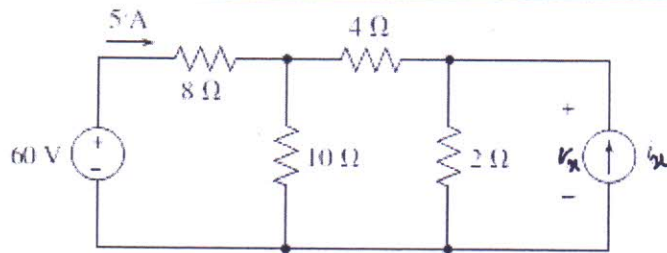

solution-

KVL and KCL equations -4M

$V_x$ - 2M

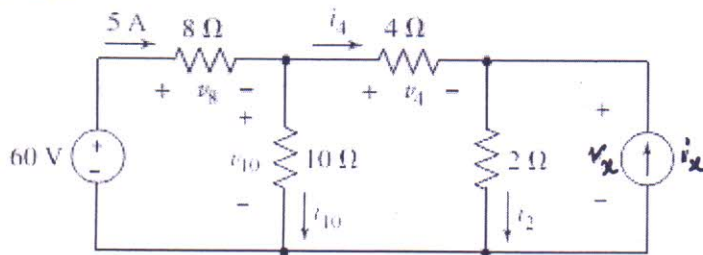

$$i_2 = i_4 + i_x$$

$$-60 + v_8 + v_{10} = 0$$


$$-v_{10} + v_4 + v_x = 0$$

$$v_x = 20 - v_4$$

$$i_4 = 5 - i_{10} = 5 - \frac{v_{10}}{10} = 5 - \frac{20}{10} = 3$$

$$v_x = 20 - 12 = 8 \text{ V.}$$

c)

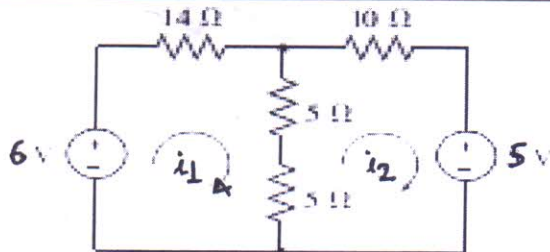

two loop equations - 2M

Answers- 2M

$i_1 = 184.2 \text{ mA}$

$i_2 = -157.9 \text{ mA}$

[4]


OR

Q2

a)

**Determine power dissipated in 4 ohm resistor using mesh analysis**

[6]

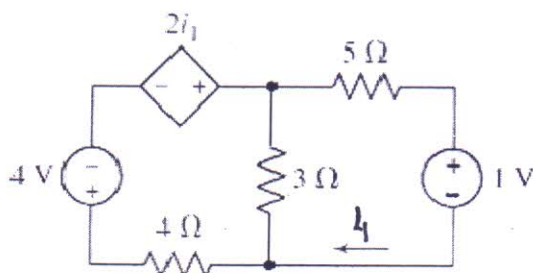

Loop equations - 3 M

Power calculations -3 M

In the lefthand mesh, we define a clockwise mesh current and name it  $i_2$ . Then, our mesh equations may be written as:

$$4 - 2i_1 + (3 + 4)i_2 - 3i_1 = 0 \quad [1]$$


$$-3i_2 + (3 + 5)i_1 + 1 = 0 \quad [2]$$

(note that since the dependent source is controlled by one of our mesh currents/variables/unknowns, these two equations suffice.)

Solving,  $i_2 = -902.4 \text{ mA}$  so  $P_{4\Omega} = (i_2)^2(4) = \boxed{3.257 \text{ W}}$

b) Determine the voltage  $v$  across 2 ohm resistor using nodal analysis

[6]

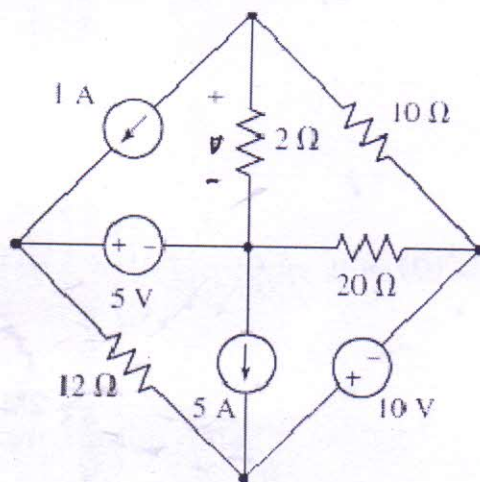

Nodal equations - 4M

Determination of  $v$  - 2M

We select the central node as the reference node. We name the left-most node  $v_1$ ; the node  $v_2$ , the far-right node  $v_3$  and the bottom node  $v_4$ .

By inspection,  $v_1 = 5 \text{ V}$

We form a supernode from nodes 3 and 4 then proceed to write appropriate KCL equations:

$$-1 = \frac{v_2}{2} + \frac{v_2 - v_3}{10} \quad [1]$$


$$5 = \frac{v_3 - v_2}{10} + \frac{v_3}{20} + \frac{v_4 - v_1}{12} \quad [2]$$

Also, we need the KVL equation relating nodes 3 and 4,  $v_4 - v_3 = 10$

Solving,  $v_2 = v = \boxed{1.731 \text{ V}}$



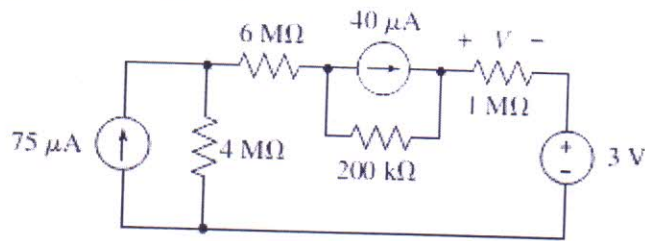
- c) compute the voltage  $V$  across the  $1\text{ M}\Omega$  resistor using repeated source transformations. [4]



Solution-

Conversion of current sources to voltage sources- 2M  
 $V = 27.2\text{ V} \quad - 2\text{M}$

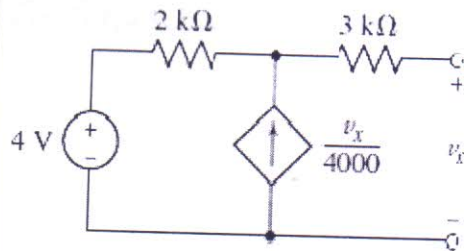- Q3 a) Obtain Thevenin's equivalent for the following network [6]



Solution-

$$-4 + 2 \times 10^3 \left( -\frac{v_x}{4000} \right) + 3 \times 10^3 (0) + v_x = 0$$

$$v_x = 8\text{ V} = V_{oc}$$

Determination of  $I_{sc}$  ----- 2M

$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{8}{0.8 \times 10^{-3}} = 10\text{ k}\Omega$$

----- 2M


----- 2M

- b) State and prove maximum power transfer theorem for network with reactive components. [4]

Statement - 1M

Proof- 3M

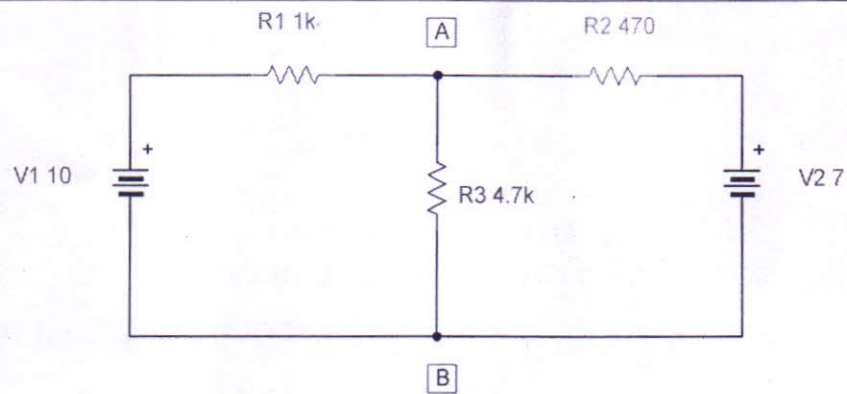- c) Apply superposition theorem to the following network and find the current through  $4.7\text{ K}$  resistor that is  $I_{AB}$  [4]




$I_{AB}$  with only 10 V = 0.64mA

$I_{AB}$  with only 7 V = 0.94mA ----- 3M

Total  $I_{AB}$  with both sources = 0.64 + 0.94 = 1.54 mA ---- 1M


**OR**

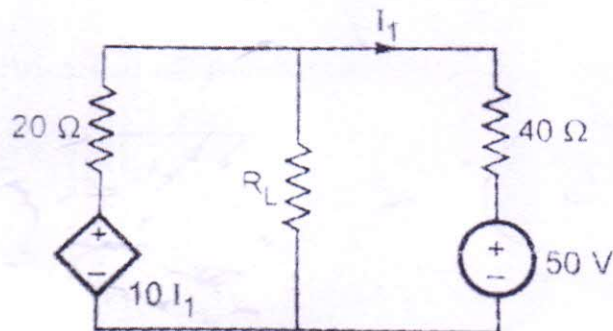Q4 a) Determine the value  $R_L$  to happen maximum power transfer [6]



Solution-

b) [4]

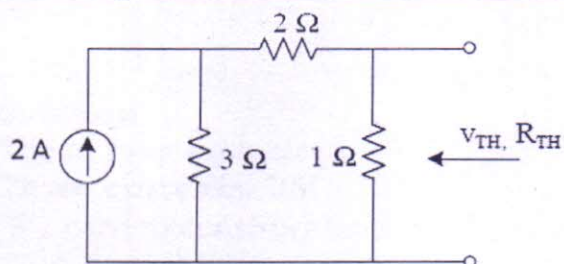

Solution -

Current through 1Ω resistor (using current division) =  $\frac{2 \times 3}{3+3} = 1 \text{ amp}$

$V_{th} = 1 \text{ volt}$

----- 2M

$R_{th} = 1 \parallel 5 = \frac{1 \times 5}{6} = \frac{5}{6} \Omega$  ----- 2M

c) Statement- 2M  
Explanation- 2M

[4]