

G.R. No.

U218-136(T1)

OCTOBER 2018/IN-SEM (T1)  
S. Y. B. TECH. (E & TC) (SEMESTER - I)

COURSE NAME: NETWORK THEORY

COURSE CODE: ETUA21176

(PATTERN 2017)

Time: [1Hour]


[Max. Marks: 30]

(\*) Instructions to candidates:


- 1) Answer Q.1 OR Q.2 and Q.3 OR Q.4.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required


Q1 a) Determine all mesh currents.

[6]

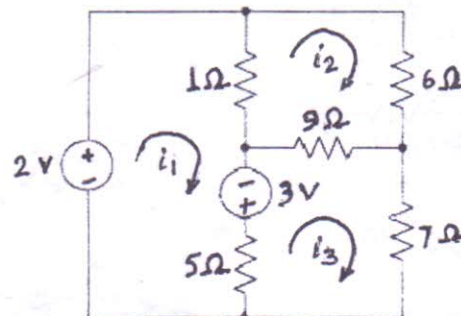b) Determine  $V_x$  using KCL and KVL equations.


[6]

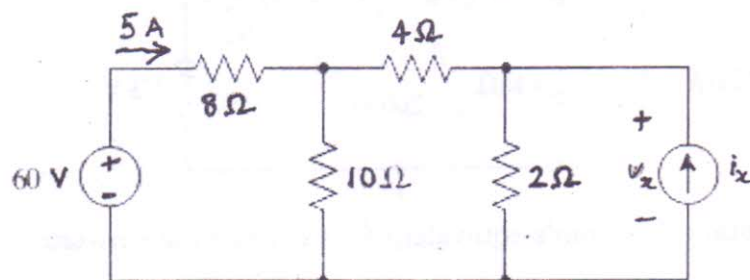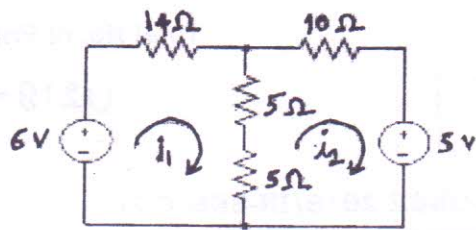c) Apply loop analysis to determine loop currents in the following network [4]  
network




OR

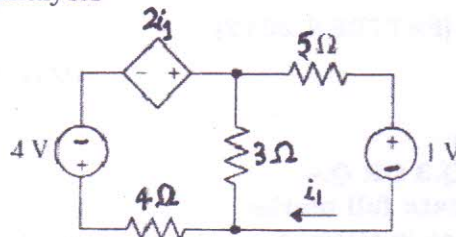
- Q2 a) Determine power dissipated in 4 ohm resistor using mesh [6]  
analysis



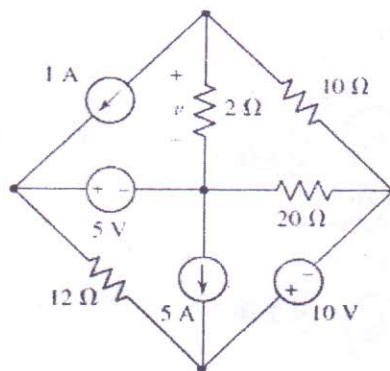- b) Determine the voltage  $v$  across 2 ohm resistor using nodal [6]  
analysis




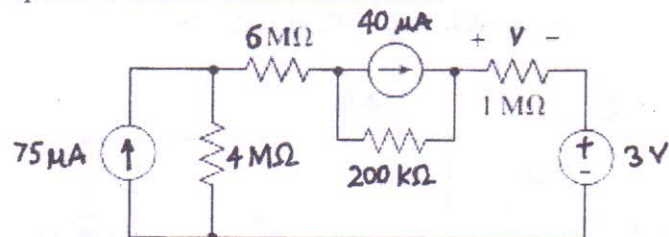- c) compute the voltage  $V$  across the 1 M ohm resistor using [4]  
repeated source transformations.




- Q3 a) Obtain Thevenin's equivalent for the following network

[6]

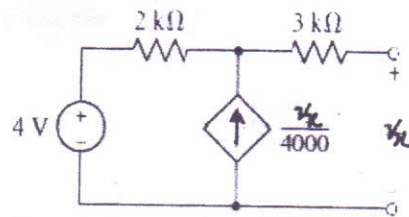


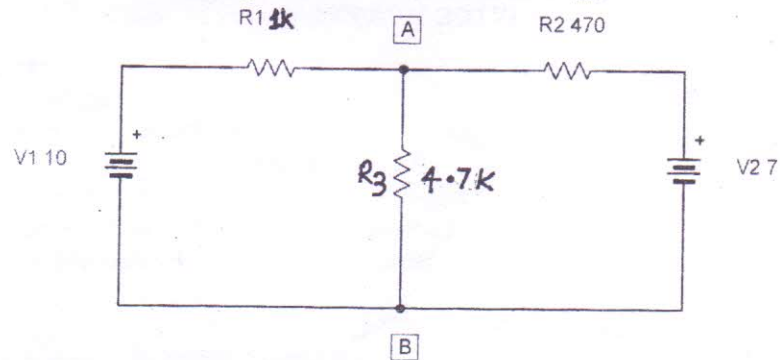- b) State and prove maximum power transfer theorem for network [4]  
with reactive components.
- c) Apply superposition theorem to the following network and find [4]  
the current through 4.7 K resistor that is  $I_{AB}$




OR

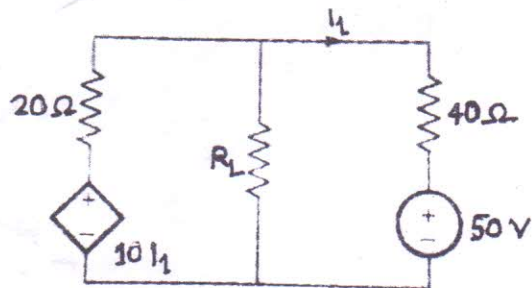- Q4 a) Determine the value  $R_L$  to happen maximum power transfer [6]



- b) [4]

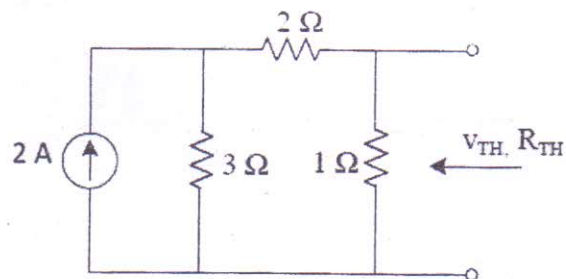

- c) State and explain Superposition theorem (Linearity Principle) [4]  
with suitable example