

OCTOBER 2018/IN-SEM (T1)**S. Y. B. TECH. (E&TC) (SEMESTER - I)****COURSE NAME: SEMICONDUCTOR DEVICES & CIRCUITS****COURSE CODE: ETUA21174****(PATTERN 2017)****Time: [1 Hour]****[Max. Marks: 30]****(*) Instructions to candidates:**

- 1) Answer Q.1 OR Q.2, Q.3 OR Q.4
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

- Q1** a) For voltage divider biasing circuit using silicon BJT with $V_{CC}=12$ V, $R_1=40K\Omega$, $R_2=5K\Omega$, $R_C=5K\Omega$ and $R_E=1K\Omega$ and $\beta=60$. Calculate I_B , I_C and V_{CE} . [6]
- b) Explain the need of bias stabilization in BJT amplifier circuit. Derive the expression for stability factor S for voltage divider biasing circuit for CE amplifier. [6]
- c) Draw h parameter model of CE amplifier and state the significance of each parameter. [4]

OR

- Q2** a) Compare CE, CB and CC amplifier with respect to performance parameters. [6]
- b) Determine the operating point parameters such as I_{BQ} , I_{CQ} and V_{CEQ} , if $V_{CC}=12$ V, $R_1=8K\Omega$, $R_2=4K\Omega$, $R_C=1K\Omega$, $R_E=1K\Omega$, $R_C=1K\Omega$ and $\beta=50$. Assume $V_{BE}=0.7$ V. Also draw DC load line. [6]
- c) What is meant by thermal runaway? Explain in detail. [4]
- Q3** a) Self-biased n-channel JFET CS amplifier with bypass capacitor shown in figure 3a has following specifications: $V_{DD}=20$ V, $R_D=3.3K\Omega$, $R_G=1M\Omega$, $R_S=500\Omega$, $I_{DSS}=16$ mA, $V_p=-8$ V, $V_{GS}=-4$ V and $r_d=50K\Omega$. Calculate A_v , R_i and R_o . [6]

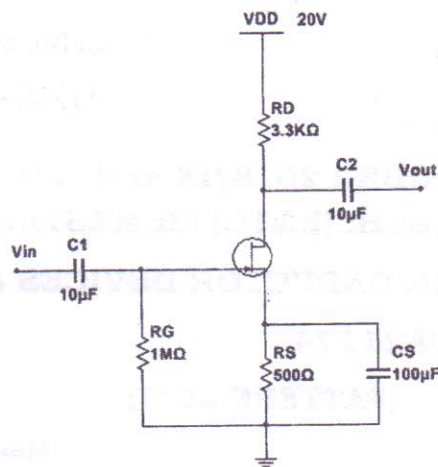


Fig. 3a

- b) For a n-channel JFET the data is as follows: [4]
 $I_{DSS} = 12 \text{ mA}$, $V_p = -6 \text{ V}$, Calculate the value of transconductance (g_m) and drain current I_D for $V_{GS} = -2 \text{ V}$.

- c) Draw neat drain characteristic and transfer characteristic for n-channel JFET. [4]

OR

- Q4 a) Self-bias circuit using n channel JFET has following parameters: [6]
 $V_{DD} = 18 \text{ V}$, $R_D = 4.7 \text{ K}\Omega$, $R_S = 1.5 \text{ K}\Omega$, $R_G = 1 \text{ M}\Omega$, $V_p = -4 \text{ V}$, $I_{DSS} = 8 \text{ mA}$.
 Determine operating point parameters such as V_{DSQ} , V_{GSQ} and I_{DQ} .

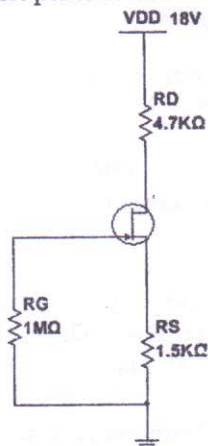


Fig. 4a

- b) With the help of ac equivalent circuit, derive the expressions for [4]
 input impedance, output impedance and voltage gain for CS amplifier with bypassed R_S .
- c) Justify the following statements: [4]
 i) JFET is a voltage controlled device.
 ii) The input resistance of JFET is higher than BJT.