

G.R. No.

U218-145 (T1)

**OCTOBER 2018/ IN-SEM (T1)****S. Y. B. TECH. (INFORMATION TECHNOLOGY) (SEMESTER - I)****COURSE NAME: DIGITAL ELECTRONICS AND LOGIC DESIGN****COURSE CODE: ITUA21175****(PATTERN 2017)**

Time: [1 Hour]

[Max. Marks: 30]

**(\*) Instructions to candidates:**

- 1) Answer Q.1 OR Q.2 and Q.3 OR Q.4.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

Q.1) a) Convert the following numbers:

- i.  $(2598.675)_{10} = ( )_{16}$
- ii.  $(110101.101010)_2 = ( )_8$
- iii.  $(A72E)_{16} = ( )_8$

[6 marks]

b) Construct Hamming Code for the following 8-bits word. Use Even Parity.

- i. 10101010
- ii. 00000000
- iii. 11111111

[6 marks]

c) Define Boolean algebra &amp; Boolean Expression. Explain any 4 basic properties of Boolean algebra? [4 marks]

**OR**

Q.2) a) Explain in short with respect to radix, symbols used, weight assigned to position, example, and applications of the following:

- i) Binary Number System
- ii) Hexadecimal Number System
- iii) Octal Number System

[6 marks]

b) Perform following arithmetic using 2's Complement:

- i)  $(7)_{10} - (11)_{10}$
- ii)  $(-7)_{10} - (11)_{10}$
- iii)  $(-7)_{10} + (11)_{10}$

[6 marks]

c) Minimize the 4-variable logic function using K-map technique.

$$f(A,B,C,D) = ABC'D + A'BCD + A'B'C' + A'B'D' + AC' + B'$$

[4 marks]

- Q.3) a) Explain Adder with Look-Ahead carry. Consider 4-bit adder and formulate Boolean expressions for the carry ( $C_0$ ,  $C_1$ ,  $C_2$ ,  $C_3$ ). [6 marks]
- b) Design (Truth Table, Logic Function, Circuit Diagram) Full Adder using MUX IC 74153. [4 marks]
- c) Define Digital Comparators. Draw and discuss n-bit comparator. [4 marks]

**OR**

- Q.4) a) Design (Truth Table, K-map, Boolean expressions, Circuit Diagram) and draw the 4-bit Code Converter circuit for converting Excess-3 Code to BCD Code. [6 marks]
- b) Design a Full Adder circuit using logic gates. Show Truth Table, K-map simplification and Circuit diagram. [4 marks]
- c) Discuss the 8-bit Parity generator/checker circuit IC 74180. [4 marks]