

G.R. No.	
-------------	--

Paper Code - U218-136 (T2)

OCTOBER 2018/IN-SEM (T2)

S. Y. B. TECH. (E & TC) (SEMESTER - I)

COURSE NAME: Network Theory

COURSE CODE: ETUA21176

(PATTERN 2017)

Time: [1Hour]

[Max. Marks: 30]

(*) Instructions to candidates:

- 1) Answer Q.1 OR Q.2 and Q.3 OR Q.4.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

Q.1) a) A parallel resonant circuit has an inductor 0.1 H with quality factor 5. Determine the capacitance and the coil resistance at resonant frequency 100 Hz. Also find the impedance at resonance.

[6 marks]

$$Q_{ar} = \frac{\omega_{ar} L}{R_{coil}} \quad R_{coil} = 12.56 \Omega \quad -2M$$

$$f_{ar} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R_{coil}^2}{L^2}}$$

$$C = 24.35 \mu F \quad -2M$$

$$Z_{ar} = \frac{L}{CR_{coil}} = 1.65 M\Omega \quad -2M$$

b) A circuit consisting of a coil of inductance 0.4H with internal resistance 10 Ω , is connected in series with a capacitor. The circuit is driven by 230V, 50Hz AC source. Determine the capacitance, voltage across inductor and current in the circuit at resonance.

[6 marks]

$$f_0 = 50 \text{ Hz Hence } C_0 = 25.33 \mu F \quad -2 M$$

$$Q_0 = 12.56$$


$$V_L = jQ_0 V = j2.89 KV = 2.89 \angle 90 \text{ KV} \quad -2M$$

$$I_0 = V/R = 23A \quad -2M$$

c) An inductor of 0.05H and internal resistance 50 Ω is connected in series with 0.02 μ F capacitor. Determine Quality factor and bandwidth

[4 marks]

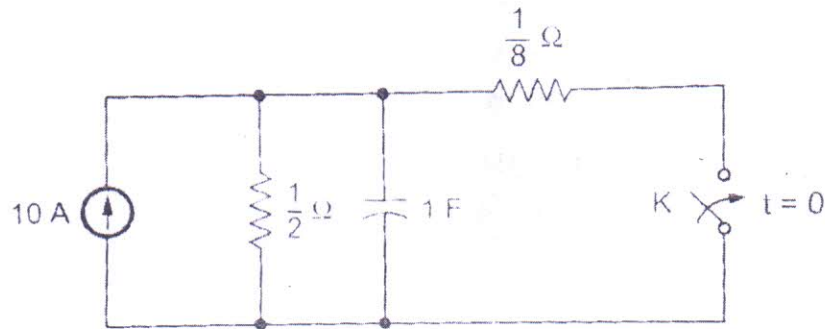Q.3) a) In the network shown below the switch is open for long time. At $t=0$ the switch is closed. Determine the voltage across capacitor. [6 marks]




$V_c(0^-) = 5 \text{ V}$ - 2M

$V_c(t) = 1 + 4e^{-10t} \text{ V}$ - 4M

b) Explain the concept and physical significance of complex frequency [4 marks]

Concept and significance of complex frequency S for all three cases - 4 M

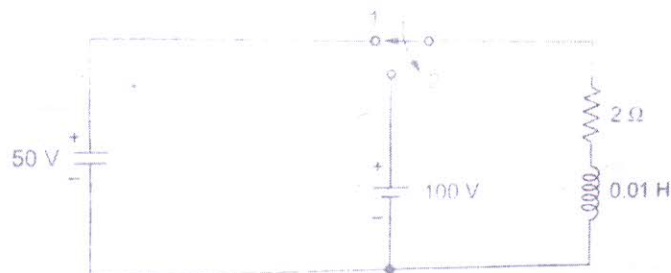c) In the following circuit the switch is moved from position 1 to 2 at $t=0$. Prior to this the steady state was reached. Determine $i(t)$ after switching. [4 marks]




$i_L(0^-) = 25 \text{ A}$ - 1M

$i_L(t) = 50 - 25e^{-200t} \text{ A}$ - 3M


OR

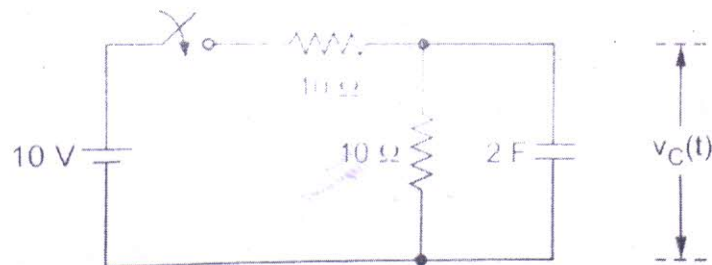Q.4) The switch is closed at $t=0$. Find the voltage across capacitor. Draw its graph. [6 marks]



$V_c(t) = 5 - 5e^{-0.1t} \text{ V}$ - 4M graph 2M

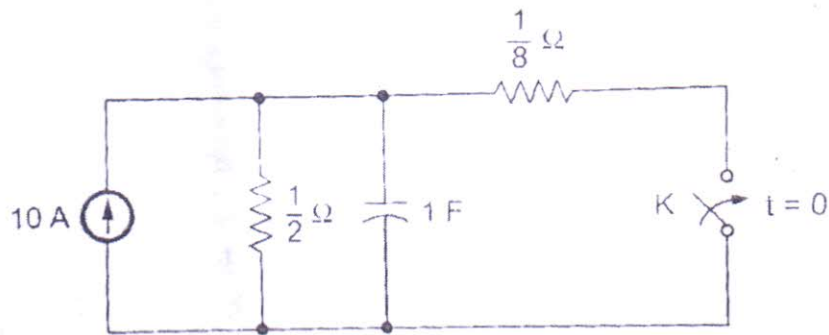Q.3) a) In the network shown below the switch is open for long time. At $t=0$ the switch is closed. Determine the voltage across capacitor. [6 marks]




$V_c(0^-) = 5 \text{ V} \quad -2\text{M}$

$V_c(t) = 1 + 4e^{-10t} \text{ V} \quad -4\text{M}$

b) Explain the concept and physical significance of complex frequency [4 marks]

Concept and significance of complex frequency S for all three cases – 4 M

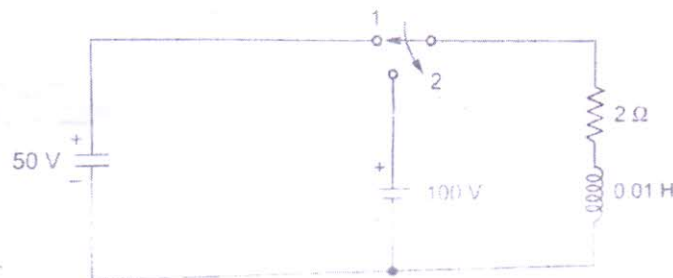c) In the following circuit the switch is moved from position 1 to 2 at $t=0$. Prior to this the steady state was reached. Determine $i(t)$ after switching. [4 marks]




$i_L(0^-) = 25 \text{ A} \quad -1\text{M}$

$i_L(t) = 50 - 25e^{-200t} \text{ A} \quad -3\text{M}$

OR

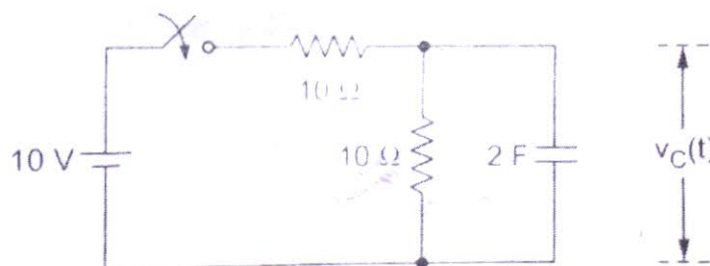Q.4) The switch is closed at $t=0$. Find the voltage across capacitor. Draw its graph. [6 marks]



$V_c(t) = 5 - 5e^{-0.1t} \text{ V} \quad -4\text{M} \quad \text{graph } 2\text{M}$


b) Determine Laplace transform for the following functions 1) $\cos(\omega t)$ 2) e^{-at}

[4 marks]

$$L\{\cos(\omega t)\} = \frac{s}{s^2 + \omega^2} \quad -2M$$

$$L\{e^{-at}\} = \frac{1}{s+a} \quad -2M$$

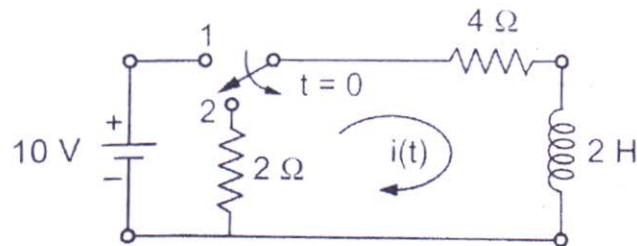c) In the following circuit the switch is moved from position 1 to 2 at $t=0$. Prior to this the steady state was reached. Determine $i(t)$ after switching. [4 marks]



$$i_L(0^-) = 2.5A \quad -1M$$

$$i_L(t) = 2.5e^{-3t} A \quad -3M$$