

G.R. No.	
-------------	--

Paper Code - 0218-136(T2)

OCTOBER 2018/IN-SEM (T2)
S. Y. B. TECH. (E & TC) (SEMESTER - I)

COURSE NAME: Network Theory**COURSE CODE: ETUA21176****(PATTERN 2017)**

Time: [1Hour]

[Max. Marks: 30]

(*) Instructions to candidates:

- 1) Answer Q.1 OR Q.2 and Q.3 OR Q.4.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

Q.1) a) A parallel resonant circuit has an inductor 0.1 H with quality factor 5. Determine the capacitance and the coil resistance at resonant frequency 100 Hz . Also find the impedance at resonance. [6 marks]

b) A circuit consisting of a coil of inductance 0.4 H with internal resistance $10\ \Omega$, is connected in series with a capacitor. The circuit is driven by 230 V , 50 Hz AC source. Determine the capacitance, voltage across inductor and current in the circuit at resonance. [6 marks]

c) An inductor of 0.05 H and internal resistance $50\ \Omega$ is connected in series with $0.02\ \mu\text{F}$ capacitor. Determine Quality factor and bandwidth [4 marks]


OR

Q.2) a) A circuit consisting of a coil of inductance 0.02 H , resistance $100\ \Omega$, is connected in series with a capacitor $0.02\ \mu\text{F}$. The circuit is driven by 50 V AC source. Determine the resonant frequency, frequency at which voltage across inductor is maximum, and frequency at which voltage across capacitor is maximum. What is the value of Z_0 (impedance) when the circuit is resonating. [6 marks]

b) A parallel resonant circuit has an inductor with quality factor 5. Determine the inductance and capacitance if the circuit impedance is $100+j0$ at resonant frequency 1.5 MHz . Also find its bandwidth. [6 marks]


c) Define Quality factor. Prove that under resonance, the anti-resonant circuit amplifies the current. [4 marks]

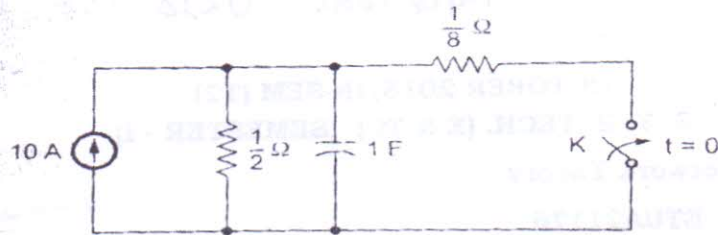Q.3) a) In the network shown below the switch is open for long time. At $t=0$ the switch is closed. Determine the voltage across capacitor. [6 marks]




b) Explain the concept and physical significance of complex frequency [4 marks]

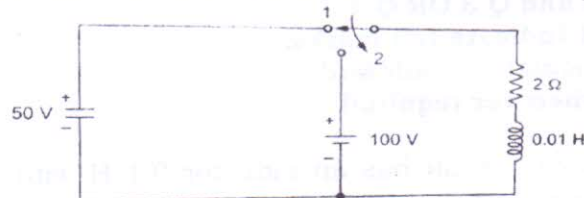c) In the following circuit the switch is moved from position 1 to 2 at $t=0$. Prior to this the steady state was reached. Determine $i(t)$ after switching. [4 marks]



OR

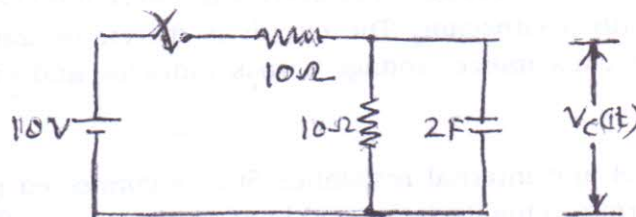Q.4) The switch is closed at $t=0$. Find the voltage across capacitor. Draw its graph. [6 marks]



b) Determine Laplace transform for the following functions 1) $\cos(\omega t)$ 2) e^{-at} [4 marks]

c) In the following circuit the switch is moved from position 1 to 2 at $t=0$. Prior to this the steady state was reached. Determine $i(t)$ after switching. [4 marks]

