

OCTOBER 2018/IN-SEM (T2)

S. Y. B. TECH. (E&TC) (SEMESTER - I)

COURSE NAME: Semiconductor Devices and Circuits

COURSE CODE: ETUA21174

(PATTERN 2017)

Q.NO	Sub Q.NO	Marking Scheme	Marks	Diffi culty Leve l	Cognitive level	CO Mapp ed
Q1	a)	$K_n = 1.40 \text{ mA/V}^2$ [2] (a) $i_D = 0.224 \text{ mA}$ [2] (b) $i_D = 2.02 \text{ mA}$ [2] Example 3.1 P. No. 134	[6]	M	Analysis	CO3
	b)	$I_D = 0.1 \text{ mA}$ [2] $V_{DS} = 3 \text{ V}$ [2] $P_T = 0.3 \text{ mW}$ [2] Example 3.3 P. No. 147	[6]	M	Analysis	CO3
	c)	Diagram [2] Working [2]	[4]	L	Knowledge	CO3
OR						
Q2	a)	(a) $I_D = 0.625 \text{ uA}$ [2] (b) $I_D = 0.6475 \text{ uA}$ [2] (c) for (a) $r_o = \infty$ [1] (c) for (b) $r_o = 53.3 \text{ M}\Omega$ [1] TYU 3.5 P. No. 146	[6]	M	Analysis	CO3
	b)	$R_1 = 885 \text{ K}\Omega$ [2] $R_2 = 454 \text{ K}\Omega$ [2] $R_D = 2.6 \text{ K}\Omega$ [2] Exercise 3.4 P. No. 150	[6]	H	Design	CO3
	c)	Body effect definition [2] Diagram [1] Equation [1]	[4]	L	Knowledge	CO3
Q3	a)	$G_m = 1.79 \text{ mA/V}$ [2] $R_o = 50 \text{ K}\Omega$ [2] $A_v = -4.26$ [2] Example 4.2 P. No. 211	[6]	M	Analysis	CO4
	b)	Definition of transconductance [2] Derivation of transconductance [2]	[4]	L	Knowledge	CO4
	c)	$K_n = 1.25 \text{ mA/V}^2$ [2] $g_m = 1.41 \text{ mA/V}$ [2]	[4]	L	Knowledge	CO4

OCTOBER 2018/IN-SEM (T2)
S. Y. B. TECH. (E&TC) (SEMESTER - I)
COURSE NAME: Semiconductor Devices and Circuits
COURSE CODE: ETUA21174
(PATTERN 2017)

		Example 4.1 P. No. 209				
OR						
Q4	a)	$A_v = -5.21$ [2] $R_i = 42 \text{ K}\Omega$ [2] $R_o = 9.66 \text{ K}\Omega$ [2] Example 4.3 P. No. 218	[6]	M	Analysis	CO4
	b)	AC equivalent circuit diagram [2] Explanation [2]	[4]	L	Knowledge	CO4
	c)	$g_m = 0.975 \text{ mA/V}$ [2] $A_v = -2.48$ [2] Example 4.5 P. No. 223	[4]	L	Knowledge	CO4