

G.R. No.

OCTOBER 2018/ IN-SEM (T2)

U218-145 (T2)

S. Y. B. TECH. (INFORMATION TECHNOLOGY) (SEMESTER - I)

COURSE NAME: DIGITAL ELECTRONICS AND LOGIC DESIGN

COURSE CODE: ITUA21175

(PATTERN 2017)

Time: [1 Hour]

[Max. Marks: 30]

## (\*) Instructions to candidates:

- 1) Answer Q.1 OR Q.2 and Q.3 OR Q.4.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

- Q.1) a) Explain the operation of a twisted-ring counter and give its state diagram. [6 marks]

**Marking scheme:** Block diagram with explanation and state diagram. [2-marks each]

- b) Design a Sequence Generator using Shift Register IC 74194 to generate the sequence 10110. [6 marks]

**Marking scheme:** Show number of FFs required, draw state table, k-map, logic expression, and circuit diagram. [2-marks each]

- c) Design a divide-by-96 (MOD-96) counter using IC 7490. [4 marks]

OR

- Q.2) a) Design the circuit for 3-bit Synchronous Up-Counter. [6 marks]

**Marking scheme:** Draw state table, k-map, logic expression, and circuit diagram.

- b) Convert JK flip-flop to D flip-flop. Show the design. [6 marks]

**Marking scheme:** Excitation table, k-map, logic expression, and circuit diagram.

- c) Design the circuit for 3-bit Asynchronous Down-Counter. [4 marks]  
Show output waveforms of counter.

[2-marks  
each]

**Marking scheme:** Circuit diagram and waveforms.


- Q.3) a) Explain the basic architecture of FPGA with suitable diagram. [6 marks]

**Marking scheme:** Architecture and explanation.

- b) Design 4:1 MUX using suitable PAL. [4 marks]

**Marking scheme:** Truth table, PAL program table, circuit

 - c) Draw an equivalent ASM chart for the state diagram shown below. It has 3 states, inputs x, and outputs z. [4 marks]



**Marking scheme:** ASM chart with proper notations.

OR

- Q.4) a) Design 3-bit Binary to Gray code converter using suitable PLA. [6 marks]

**Marking scheme:** Truth table, k-map, logic expression, design

- b) Draw ASM chart for a 2 bit up counter with output 'Q1Q0' and Enable signal X is to be designed. If X=0, counter changes the state as '00-01-10-11'. If X=1, counter should remain in present state. [4 marks]

**Marking scheme:** State diagram, ASM chart, state table, logic expression/function, circuit diagram.

- c) Explain the basic architecture of CPLD with suitable diagram. [4 marks]

**Marking scheme:** Architecture and explanation.