

Total No. of Questions – [08]

Total No. of Printed Pages: [02]

G.R. No.

paper code: U 229-134 (BE-F&FS)  
DECEMBER 2019/ENDSEM Backlog Exam

**S. Y. B. TECH. (E & TC) (SEMESTER - II)**

**COURSE NAME: Integrated Circuits (IC)**

**COURSE CODE: ETUA22174**

**(PATTERN 2017)**

Time: [2 Hours]

[Max. Marks: 50]

**(\*) Instructions to candidates:**

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

**Q1 a)** Describe with neat block diagram, how operational amplifier works [6]

**OR**

- b)** Define following parameters of operational amplifier along with their expressions. Also mention their ideal values. [6]
- a) Input bias current
  - b) Differential Voltage gain
  - c) Bandwidth

**Q2 a)** What is Instrumentation amplifier? Describe with reference to 3 opamp circuit. What are the requirements of good instrumentation amplifier( any three). [6]

**OR**

- b)** Which circuit will you use for converting square wave to triangular wave? Describe how the circuit works. [6]

**Q3 a)** With neat circuit diagram and waveforms, describe how Half wave Precision rectifier works. [6]

**OR**

- b)** In inverting comparator, sine wave input of 4Vpp is given to the inverting terminal and noninverting terminal is grounded. Draw and justify the input-output waveforms. [6]

**Q4 a)** What is Butterworth filter? Draw circuit diagram of second order Butterworth Low pass filter. [4]

**OR**

- b) Determine the cut off frequency of first order Butterworth high pass filter if  $R = 1 \text{ k ohm}$  and  $C = 0.1 \text{ micro farad}$ . What will be the roll off rate after cutoff frequency? [4]

- Q5** a) Draw the circuit diagram of any voltage to frequency convertor. Describe how the circuit works. [6]  
b) Draw the transfer characteristics of 4-bit ADC. Give its resolution. [4]  
c) What is sensitivity of V to I convertor. How much is the sensitivity of V to I convertor with 1mA current and 2V input. [4]

**OR**

- Q6** a) Draw the circuit of 3 bit Flash ADC and describe its operation. [6]  
b) Draw the circuit diagram of floating load V to I converter and describe its operation. [4]  
c) Define resolution of D to A converter? Determine the resolution for 3 bit DAC which has reference voltage 5V. [4]

- Q7** a) Justify that, the X-OR gate can be used as phase comparator. [6]  
b) Define free running frequency and capture range in PLL. [4]  
c) Describe how PLL is used as AM detector/demodulator. [4]

**OR**

- Q8** a) Draw the transfer characteristics of PLL and describe its working with its different modes of operation. [6]  
b) Describe how PLL is used as FM demodulator? [4]  
c) An output square wave having frequency 10 times the input square wave is to be obtained using PLL. Draw the block diagram and justify. [4]