

S.Y. B. Tech - Sem. - I
2017 course - 2014 - 20/12/19

Total No. of Questions - [8]

Total No. of Printed Pages 2

G.R. No.

Paper code - U 219-136 (BE-F&FS)

DECEMBER 2019/ENDSEM
S. Y. B. TECH. (E&TC) (SEMESTER - I)

Backlog Exam

COURSE NAME: NETWORK THEORY

COURSE CODE: ETUA21176

(PATTERN 2017)

Time: [2 Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

Q.1 a) State and Describe Superposition theorem with help of suitable example. [6]


OR

b) State and prove Norton's theorem with the help of suitable example. [6]

Q.2 a) State and prove Thevenin's theorem with the help of suitable example. [6]

OR

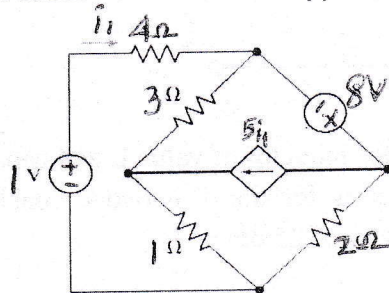b) Determine the current supplied by 1V source [6]




Q.3 a) In a series resonant circuit, with inductor of 1H and coil resistance 10 ohms and capacitor of 1nF, determine the resonant frequency. Also find the quality factor [6]

OR

b) Compare series and parallel resonance (any three points) [6]

Q.4 a) In the following circuit the switch is moved from position 1 to 2 at $t=0$. Prior to this the steady state was reached. Determine $i(t)$ after switching. [4]

Y2

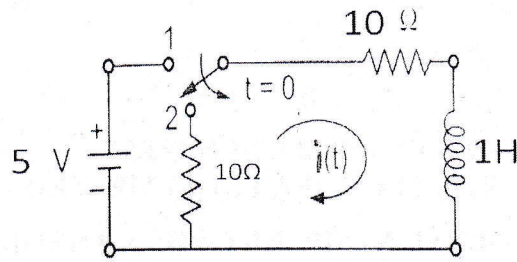


OR

- b) Determine Laplace transform for the following functions 1) $\cos(\omega t)$ 2) 10 [4]

- Q.5 a) Describe the stepwise procedure to determine Z parameters and Y parameters of the network. [6]
 b) Describe in details a) Input impedance b) transfer impedance [4]
 c) Determine Y_{11} and Y_{22} parameters for the T network consisting of each series arm of 100 ohms and shunt arm of 100 ohm. [4]

OR

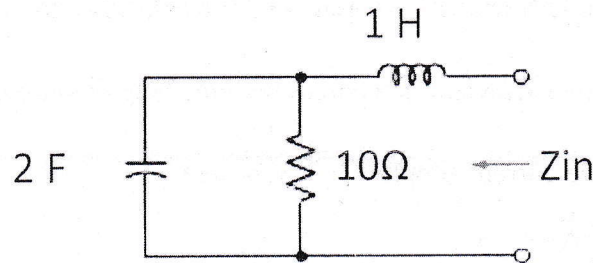- Q.6 a) Determine driving point impedance Z_{in} for the following network [6]



- b) Give the 'S' domain equivalents for inductor of value L and capacitor C [4]
 c) Determine Z_{11} and Z_{22} parameters for the T network consisting of each series arm of 25 ohms and shunt arm of 25 ohm. [4]
- Q.7 a) Draw the circuit diagram of constant K HPF. Draw its frequency response/ characteristics. [6]
 b) What is attenuation constant and phase constant. [4]
 c) Draw the characteristics curves for attenuation constant, phase constant and characteristics impedance Z_{0T} for LPF. [4]

OR

- Q.8 a) What are constant K filters? Draw the curve for attenuation and phase constant of constant k LPF. [6]
 b) Draw the characteristics curves for attenuation constant, phase constant and characteristics impedance Z_{0T} for HPF. [4]
 c) Define quality factor of the filter. How it affects the bandwidth of the filter? [4]