

Total No. of Questions – [08]

Total No. of Printed Pages: 04

G.R. No.

Paper code - (U 219 - 134 (BE - E&FS

DECEMBER 2019/ENDSEM - Backlog Exam

S. Y. B. TECH. (E&TC) (SEMESTER - I)

COURSE NAME: Semiconductor Devices & Circuits

COURSE CODE: ETUA21174

(PATTERN 2017)

Time: [2Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

Q.1) a) Draw voltage divider biasing circuit and Derive the expression for stability factor for voltage divider biasing circuit.

[6 marks]

OR

b) Calculate the Q point values of I_B , I_C and V_{CE} for the voltage divider bias circuit, if $V_{CC}=12\text{ V}$, $R_1=8\text{K}\Omega$, $R_2=4\text{ K}\Omega$, $R_C=1\text{K}\Omega$ and $R_E=1\text{ K}\Omega$. Assume silicon transistor with $\beta=50$.

[6 marks]

Q. 2)a) Draw the construction of n-channel JFET and explain its working in detail along with its characteristics.

[6 marks]

OR

b) N-channel JFET common source amplifier with bypass capacitor has $R_G=1\text{M}\Omega$, $R_D=5\text{K}\Omega$, $R_S=1\text{K}\Omega$, $g_m=2\text{mA/V}$, $r_d=10\text{K}\Omega$, Determine A_v , R_i and R_o .

[6 marks]

Q. 3) a) Draw and explain the output characteristic and transfer characteristic of N channel E-MOSFET.

[6 marks]

OR

b) Explain following non-ideal effects for MOSFET.

- i) Body effect
- ii) Break down effect

[6 marks]

Q. 4) a) For CS amplifier with voltage divider biasing circuit using n-channel MOSFET has $V_{DD}=10\text{V}$, $R_1=70\text{ K}\Omega$, $R_2=27\text{ K}\Omega$, $R_D=5\text{K}\Omega$. Calculate the values of g_m , and r_o . Assume following data for MOSFET: $V_T=1.2\text{V}$, $K_n=0.48\text{mA/V}^2$ and $\lambda=0.012\text{A/V}$.

[4 marks]


OR

- b) For CS amplifier using MOSFET determine g_m , I_D and r_o if $V_T = 1$ V, $K_n = 0.8$ mA/V², $\lambda = 0.01$ /V, $V_{GSQ} = 3$ V. [4 marks]

- Q. 5) a) Explain how n-channel MOSFET and p-channel MOSFET can be used as current sink and source respectively with the help of output I-V characteristics of both? [6 marks]


- b) Draw MOSFET as a practical switch model. Explain the significance of each component. [4 marks]

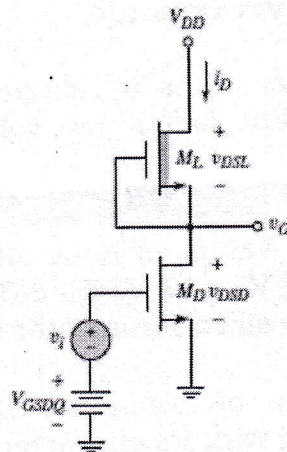- c) Determine the small-signal voltage gain of the NMOS amplifier with depletion load. For the circuit shown in figure, assume transistor parameters of $V_{TND} = +0.4$ V, $V_{TNL} = -0.8$ V, $K_{nD} = 2$ mA/V², $K_{nL} = 0.4$ mA/V², $\lambda_D = 0.01$ V⁻¹, and $\lambda_L = 0.02$ V⁻¹. Assume the transistors are biased at $I_{DQ} = 0.2$ mA. [4 marks]



OR

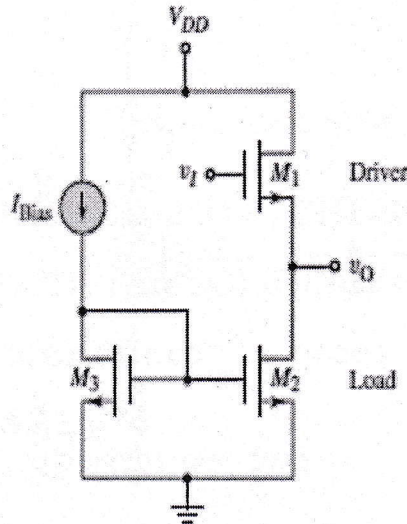
- Q. 6)a) The transconductance g_{m1} of the transistor M_1 in the circuit of figure is to be changed by changing the bias current such that the output resistance of the circuit is $R_o = 2$ k Ω . Assume the bias voltage is $V_{DD} = 3.3$ V. Assume that all transistors are matched with parameters $V_{TN} = 0.4$ V, $K_n = 0.20$ mA/V², and $\lambda = 0.01$ V⁻¹. The drain current in M_1 is $I_{D1} = I_{Bias} = 0.2$ mA. (a) What are the required value of g_{m1} and new value of I_{Bias} ? (b) Using the results of part (a), what is the small-signal voltage gain? [6 marks]



- b) Sketch CMOS common-gate amplifier circuit and its small-signal equivalent circuit. Write expression for small-signal voltage gain and output resistance. [4 marks]
- c) Sketch NMOS source follower amplifier circuit and its small-signal equivalent circuit. Write expression for small-signal voltage gain and output resistance [4 marks]
- Q. 7) a) Draw block schematic of following feedback topologies:
 i) Voltage series feedback topology
 ii) Voltage shunt feedback topology
 iii) Current series feedback topology [6 marks]
- b) A Colpitt Oscillator circuit having two capacitors of 24nF and 240nF respectively are connected in parallel with an inductor of 10mH. Determine the frequency of oscillations of the circuit. [4 marks]
- c) Explain Hartley oscillator with neat circuit diagram. Also write its cut off frequency expression. [4 marks]

OR

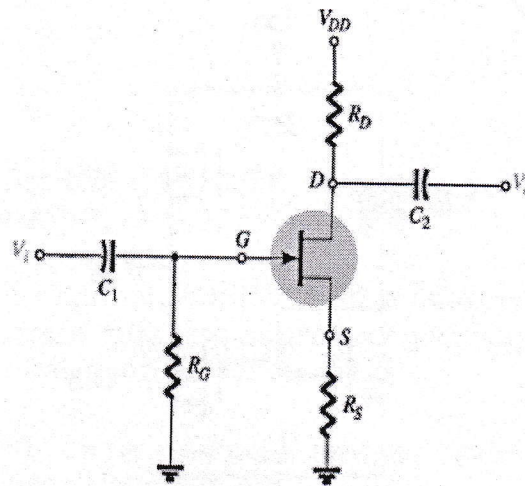- Q. 8) a) For a given current series feedback amplifier, determine G_{mf} , A_{vf} , R_{if} , R'_{of} if $R_s=1K\Omega$, $R_D=3.9K\Omega$, $R_G=1M\Omega$, $g_m=2mA/V$ and $r_o=25K\Omega$. [6 marks]



- b) Draw neat circuit diagram of Colpitt oscillator and explain it's working in detail.

[4 marks]

- c) Draw circuit diagram and AC equivalent of voltage series feedback amplifier and write it's final expression for ac parameters.

[4 marks]