

G.R. No.

Paper code - U239-135 (ESE)

DECEMBER 2019 ENDSEM**S. Y. B.TECH. (Electronics & Telecommunication) (SEMESTER - III)****COURSE NAME: Digital System Design****COURSE CODE: ETUA21185****(PATTERN 2018)**

Time: [2 Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) All questions are compulsory.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed.
- 4) Assume suitable data where ever required.

Q.1) Attempt any **one**

- a) Using K-map, simplify and obtain minimized SOP expression and draw its logic diagram

[4]

$$Y = \sum m(0,1,2,14,15) + d(3,5,7)$$

$$Y = \sum m(0,1,2,3,8,9,10,11) + d(6,14)$$

- b) Using K-map, simplify and obtain minimized POS expression and draw its logic diagram

[4]

$$Y = (\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + C + \bar{D})(A + B + \bar{C} + \bar{D})(\bar{A} + B + C + \bar{D})(A + \bar{B} + \bar{C} + \bar{D})$$

Q.2) Attempt any **one**

- a) Design a logic circuit which will subtract three numbers of one bit each and gives output as difference and borrow, draw its logic diagram.
- b) Design 3-bit gray to binary code converter and draw its logic diagram.


[4]

[4]


Q.3) Attempt any **one**

- a) Determine the Q output waveforms of the flip-flop JK and CLK inputs shown in Figure. Assume the negative edge triggered flip-flop is initially reset.

[6]

 

 - b) Determine the Q and \bar{Q} output waveforms of the flip-flop D and CLK inputs shown in Figure. Assume the positive edge triggered flip-flop is initially reset. [6]



Q.4) Attempt any **one**

- a) Using D flip-flop design a Asynchronous three bit down counter. Write truth table and draw its logic diagram. [10]
Design MOD-6 synchronous up counter using D flip flop. Write its truth table and draw its logic diagram.
- b) Using D flip-flop design a Synchronous four bit up-counter, Draw its logic diagram. [10]
Design MOD-6 synchronous down counter using D flip flop. Write its truth table and draw its logic diagram.

Q.5) Attempt any **one**

- a) A certain TTL IC has six one input NOT gates. Draw the internal structure of single NOT gate and explain its working for all the possible input combinations. [13]
Draw the block diagram of generic CPLD architecture, and write its parameters.
- b) A certain CMOS IC has four two input NOR gates. Draw the internal structure of single NOR gate and explain its working for all the possible input combinations. [13]
Draw the generic architecture of FPGA and write its parameters.

Q.6) Attempt any **one**

- a) List the modeling style of VHDL? Explain data flow modeling with suitable example? Write Syntax for When-Else? [13]
Write VHDL code for JK flip-flop?
- b) List the modeling style of VHDL? Explain Behavioral modeling in VHDL with suitable example? Write syntax for if-then-else in VHDL? [13]
Write VHDL code for half adder?