

G.R. No.

Paper Code – U 239-134 (ESE)

DECEMBER 2019 ENDSEM
S. Y. B.TECH. (E & TC) (SEMESTER –III)

COURSE NAME: Electronics Devices & Circuits
COURSE CODE: ETUA21184

(PATTERN 2018)

Time: [2 Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) All questions are compulsory.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed.
- 4) Assume suitable data where ever required.

Q.1) Attempt any one

- a) Compare Full wave and half wave rectifier with neat diagrams of both and other parameters. [4]
- b) Explain working principle of LED and state its applications. [4]

Q.2) Attempt any one

- a) Voltage divider biasing circuit uses silicon BJT has $\beta = 150$, $V_{CC} = 5$ V, $R_1 = 9$ K Ω , $R_2 = 2.25$ K Ω , $R_E = 200$ Ω and $R_C = 1$ K Ω . Find I_{BQ} and I_{CQ} . [4]
- b) Draw and explain hybrid model of BJT for common emitter configuration. [4]

Q.3) Attempt any one

- a) The self-bias circuit using n-channel JFET has $V_{DD} = 18$ V, $R_D = 4.7$ K Ω , $R_S = 1.5$ K Ω and $R_G = 1$ M Ω . Determine the co-ordinates of Q point such as I_{DQ} , V_{GSQ} and V_{DSQ} . Assume JFET has $V_P = -4$ V, $I_{DSS} = 8$ mA and $g_m = 5$ mS. [6]
- b) CS amplifier using n-channel JFET with self-bias and unbypassed source resistor has $R_G = 1.5$ M Ω , $R_D = 3$ K Ω , $R_S = 1.2$ K Ω , and $V_{DD} = 20$ V. The JFET parameters are $I_{DSS} = 8$ mA, $V_P = -8$ V and $Y_{OS} = 20$ μ S, $V_{GSQ} = -2$ V, $I_{DQ} = 2$ mA. Calculate g_m , r_o and A_v . [6]

Q.4) Attempt any one

- a) Voltage divider biasing circuit using n-channel E-MOSFET has $V_{DD} = 5$ V, $R_1 = 30$ K Ω , $R_2 = 20$ K Ω , $R_D = 20$ K Ω , $V_T = 1$ V, $K_n = 0.1$ mA/V². Determine the co-ordinates of Q point such as V_{DSQ} , V_{GSQ} and I_{DQ} . [6+4]

Explain following non-ideal effects for MOSFET.

- i) Break down effect
- ii) Channel length modulation.

- b) Draw the constructional (structure) diagram of n-channel E-MOSFET and explain its working with the help of both [6+4] characteristics.

An NMOS transistor is fabricated in a $0.4\text{-}\mu\text{m}$ process having $\mu_n C_{ox} = 200\text{ }\mu\text{A/V}^2$ and $V_A = 40\text{ V}$. If $L = 0.8\text{ }\mu\text{m}$ and $W = 16\text{ }\mu\text{m}$. Find λ and I_D that results when the device is operated with an overdrive voltage $(V_{GS} - V_T) = 0.5\text{ V}$ and $V_{DS} = 1\text{ V}$.

Q.5) Attempt any one

- a) Common source amplifier using n-channel E-MOSFET has $R_1 = 40\text{ M}\Omega$, $R_2 = 10\text{ M}\Omega$, $R_D = 4.7\text{ K}\Omega$, R_{sig} or $R_{Source} = 2.2\text{ K}\Omega$ and $V_{DD} = 25\text{ V}$. If MOSFET parameters are $V_T = 3\text{ V}$, $K_n = 0.4\text{ mA/V}^2$ and $r_o = 40\text{ K}\Omega$. Calculate A_v , R_i and R_o . [7+6]

Draw voltage divider biasing common source amplifier circuit using n-channel E-MOSFET and write the expressions for A_v , R_i and R_o .

- b) Determine I_{DQ} , g_m and r_o for a MOSFET CS amplifier if $V_{DD} = 5\text{ V}$, $V_{GSQ} = 2.12\text{ V}$, $R_D = 2.5\text{ K}\Omega$. Assume transistor parameters as $V_T = 1\text{ V}$, $K_n = 0.8\text{ mA/V}^2$ and $\lambda = 0.02/\text{V}$. [7+6]

Draw and explain the high frequency AC equivalent circuit for n channel E-MOSFET and explain the effect of source terminal resistances, R_s on the gain of the CS amplifier.


Q.6) Attempt any one

- a) Explain working of Hartley oscillator with neat circuit diagram. [7] A Hartley Oscillator circuit has two inductances of $L_1 = L_2 = 100\text{ }\mu\text{H}$ and $C = 0.05\text{ }\mu\text{F}$. Determine the frequency of oscillations of the circuit.

Draw block schematic of following feedback topologies:

- i) Voltage shunt feedback topology
- ii) Current shunt feedback topology
- iii) Current series feedback topology

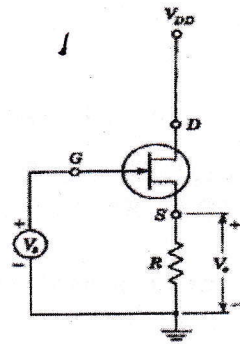- b) For the FET source follower circuit, calculate values of A_{vf} , R_{if} , R_{of} and R'_{of} . Assume $g_m = 2\text{ mA/V}$ and $r_d = 40\text{ K}\Omega$ and $R = 3\text{ K}\Omega$. [7+6]



Draw the block diagram of voltage series negative feedback amplifier and derive the expression for A_{vf} .