

G.R. No.

Paper code - U239-133 (ESE)

DECEMBER 2019 ENDSEM

S. Y. B.TECH. (E & TC) (SEMESTER -III)

COURSE NAME: ENGINEERING CIRCUIT ANALYSIS

COURSE CODE: ETUA21183

(PATTERN 2018)

Time: [2 Hours]



[Max. Marks: 50]

(*) Instructions to candidates:


- 1) All questions are compulsory.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed.
- 4) Assume suitable data where ever required.

Q.1) Attempt any **one (a or b)**a) Use KCL and KVL to find the voltage V_x .

[4]

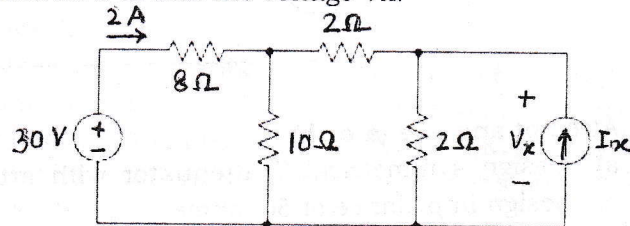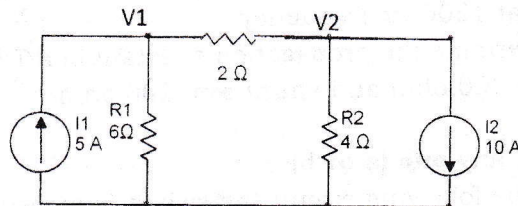
b) Use nodal analysis to find the voltages at the nodes V_1 and V_2 in the circuit of fig. [4]Q.2) Attempt any **one (a or b)**

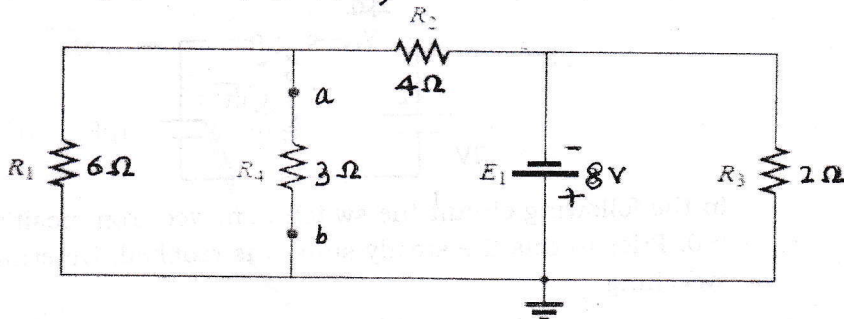a) Obtain the Thevenin's equivalent network for the network shown below (between a and b) [4]



1/2

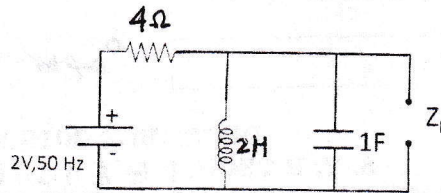
- b) What should be the value of impedance Z_L for maximum power transfer? [4]



Q.3) Attempt any **one (a or b)**

- a) A parallel circuit has a fixed capacitor and variable inductor having constant quality factor of 4. Find value of inductance and capacitance for circuit impedance of $1K\Omega$ at resonating frequency of 2.4 MHz. What is bandwidth of circuit? [6]

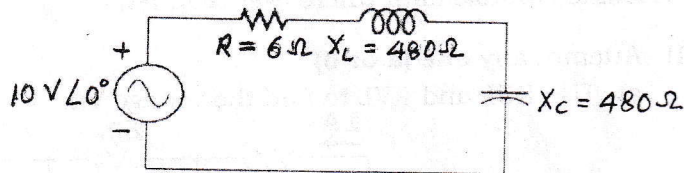- b) Determine the Quality factor, Voltage across inductor at resonance and current through the circuit at resonance. [6]



Q.4) Attempt any **one (a or b)**

- a) Design symmetrical T attenuator with attenuation of 40 dB and design impedance of 500ohms. [10]


Determine the open circuit and short circuit impedance of a T network with each series arm 100 ohm and shunt arm 200 ohm.

- b) Design a LPF T network with design impedance 660 ohm and cut off frequency 1000 Hz. Compute phase angle β at 500 Hz and α in dB at 1500 Hz frequency. [10]


Determine the propagation constant of a T network with each series arm 200 ohm and shunt arm 100 ohm.

Q.5) Attempt any **one (a or b)**

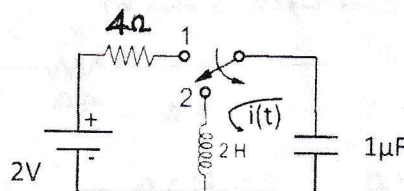- a) In the following circuit the switch is moved from position 1 to 2 at $t=0$. Prior to this the steady state was reached. Determine $i(t)$ after switching. [13]



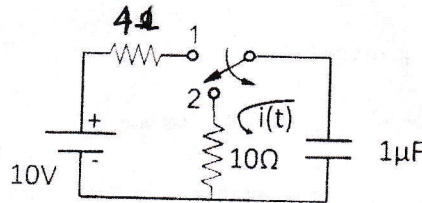
In the following circuit the switch is moved from position 1 to 2 at $t=0$. Prior to this the steady state was reached. Determine $i(t)$ after switching.



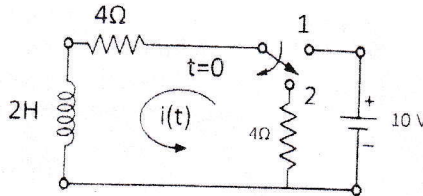- b) Give the significance of the complex frequency 's' and how damping parameter affects the nature of the output signal. [13]

Derive the S domain model for the inductor.

In the following circuit the switch is moved from position 1 to 2 at $t=0$. Prior to this the steady state was reached. Determine $i(t)$ after switching.



Q.6) Attempt any **one (a or b)**

- a) In transmission line describe its primary and secondary constants. [13]
Find the characteristics impedance, attenuation in db suffered by a telephone line of 100km length at frequency 1KHz. At this freq. Also find velocity of propagation and phase constant. The primary constants for line are-

$$R = 6\Omega / Km, L = 2.2mH / Km, G = 0.25mho / Km, C = .005\mu F / Km$$

- b) Using transmission line equations prove that, if the finite length line is terminated in characteristics impedance Z_0 , its input impedance is also Z_0 . [13]

A telephone line has characteristics impedance, 100Ω and attenuation 0.1 neper/km. The phase constant for the line is 0.2 rads/km. When $1V$ signal is applied at the sending end current of $100mA$ flows. What will be the current at the point on the line $30km$ away from sending end. The length of a line is $100km$.
