

Total No. of Questions – [ 3 ]

Total No. of Printed Pages: 2

G.R. No.	
----------	--

Paper Code - U128-107 (T1)

**MARCH 2019 / IN-SEM (T1)**

**F. Y. B.TECH. (COMMON) (SEMESTER -II)**

**COURSE NAME: BASIC ELECTRICAL ENGINEERING**

**COURSE CODE: ET 10182A**

**(PATTERN 2018)**

Time: [1 Hour]

[Max. Marks: 20]

**(\*) Instructions to candidates:**

- 1) All questions are compulsory.
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed.
- 4) Use suitable data where ever required.
- 5) Assume suitable data, if required.

Q 1) Attempt any **two**.

- a) Using Superposition theorem, find the current flowing through  $3\Omega$  resistance for the network shown in fig.1. [4]

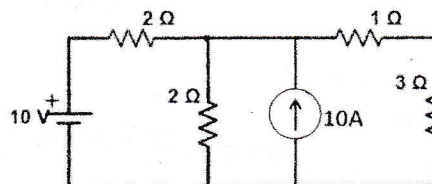


Fig.1

- b) Using Thevenin's theorem, find the current flowing through  $3\Omega$  resistance for the network shown in fig.1. [4]
- c) State and explain in brief Kirchhoff's laws. [4]

Q 2) Attempt any **two**.

- a) A circuit consists of a resistance of  $4\Omega$ , inductance of  $0.5H$  and a variable capacitance in series across  $100V$ ,  $50Hz$  ac supply. Calculate: i) the value of capacitance required to produce series resonance ii) current flowing at resonance iii) Voltage across resistance and capacitance at resonance. [4]
- b) Prove that current in purely inductive circuit lags behind the applied voltage by  $90^\circ$  if it is connected across an ac voltage source of  $v = V_m \sin \omega t$  Volts. [4]

- c) Derive with the help of a neat phasor diagram, an expression showing the relationship between line current and phase current in case of a three phase balanced delta connected load which has a lagging power factor and connected across a symmetrical three phase ac supply. [4]

Q 3) Attempt any **one**.

- a) 80 KVA, 3200/400 V, 50 Hz, single phase transformer has 111 turns on its secondary. Calculate: - i) number of turns on primary winding  
ii) primary and secondary full load current  
iii) cross sectional area of the core if the maximum flux density is 1.2 Wb/mm<sup>2</sup>. [4]
- b) State any two significant advantages and applications of a single phase autotransformer. [4]