

Total No. of Questions – [08]

Total No. of Printed Pages: 043

G.R. No.

Paper Code - U218-134 (BE-FF)

MAY 2019/ENDSEM

S. Y. B. TECH. (E&TC) (SEMESTER - I)

COURSE NAME: Semiconductor Devices & Circuits

COURSE CODE: ETUA21174

(PATTERN 2017)

Time: [2Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

Q.1)a) Explain voltage divider biasing circuit with neat circuit diagram and write its equations. [6 marks]

OR

b) Calculate the Q point values of I_B , I_C and V_{CE} for the voltage divider bias circuit, if $V_{CC}=12\text{ V}$, $R_1=8\text{K}\Omega$, $R_2=4\text{ K}\Omega$, $R_C=1\text{K}\Omega$ and $R_E=1\text{ K}\Omega$. Assume silicon transistor with $\beta=50$. [6 marks]

Q. 2) a) N-channel JFET common source amplifier without bypass capacitor has $R_G=1\text{M}\Omega$, $R_D=50\text{K}\Omega$, $R_S=1\text{ K}\Omega$, $g_m=2\text{mA/V}$, $r_d=10\text{K}\Omega$, Determine A_v , R_i and R_o . [6 marks]

OR

b) Draw and explain transfer characteristics and output characteristics of n-channel JFET. [6 marks]

Q. 3)a) Voltage divider biasing circuit using n-channel E-MOSFET has $V_{DD}=5\text{V}$, $R_1=30\text{ K}\Omega$, $R_2=20\text{ K}\Omega$, $R_D=20\text{K}\Omega$, $V_T=1\text{V}$, $K_n=0.1\text{ mA/V}^2$. Determine the co-ordinates of Q point such as V_{DSQ} , V_{GSQ} and I_{DQ} . [6 marks]

OR

b) Explain following non-ideal effects for MOSFET.
i) finite output resistance
ii) Temperature effect

[6 marks]


- Q. 4) a)** For CS amplifier using MOSFET determine g_m , I_D and r_o if $V_T = 1$ V, $K_n = 0.8$ mA/V², $\lambda = 0.01$ /V, $V_{GSQ} = 3$ V. [4 marks]

OR


- b)** Draw complete AC equivalent model for n-channel MOSFET CS amplifier with bypass capacitor. Write small-signal voltage gain expression for CS amplifiers. [4 marks]
- Q. 5) a)** Draw and explain current sink and current source circuit using n-channel MOSFET. [6 marks]
- b)** Draw MOSFET as a practical switch model. Explain the significance of each component. [4 marks]
- c)** Explain in detail MOS act as a active diode and resistor with neat circuit diagram. [4 marks]

OR

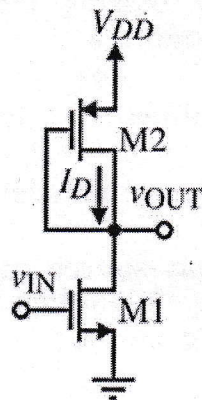- Q.6) a)** For the CMOS amplifier shown in figure, the parameters are: $V_{TN} = 1$ V, $V_{TP} = -0.8$ V, $k'_n = 80$ μ A/V², $k'_p = 40$ μ A/V², $(W/L)_1 = 80$, $(W/L)_2 = 1$, and $V_{DD} = 3.3$ V. $\lambda_n = 0.02$ V⁻¹ and $\lambda_p = 0.01$ V⁻¹. Drain current, $I_D = 0.1$ mA. Determine the small-signal voltage gain and output resistance. [6 marks]



- b)** Sketch NMOS source follower amplifier circuit and its small-signal equivalent circuit. Write expression for small-signal voltage gain and output resistance. [4 marks]
- c)** Explain CMOS inverter as a amplifier with neat circuit diagram [4 marks]
- Q. 7) a)** For the FET source follower circuit, calculate values of A_{vf} , R_{if} , R_{of} and R'_{of} . Assume $g_m = 2$ mA/V and $r_d = 40$ K Ω and $R = 4.7$ K Ω . [6 marks]

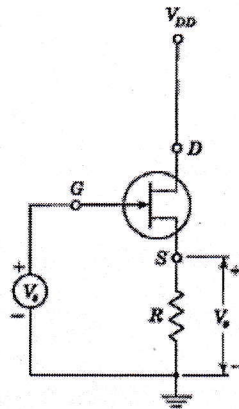

- b) A Colpitts Oscillator circuit having two capacitors of 24nF and 240nF respectively are connected in parallel with an inductor of 10mH . Determine the frequency of oscillations of the circuit.

[4 marks]

- c) An amplifier has open loop gain of 100 and its lower and upper cut off frequency of 100 Hz and 100 KHz respectively. A feedback network with feedback factor of 0.99 is connected to the amplifier. Calculate the new lower and upper cut off frequencies.

[4 marks]

OR

- Q. 8) a) Draw block diagram of voltage series and current series feedback topology.

[6 marks]

- b) Draw neat circuit diagram of Colpitts oscillator and explain in detail.

[4 marks]

- c) Draw circuit diagram and AC equivalent of voltage series feedback amplifier and write its final expression for ac parameters.

[4 marks]