

Total No. of Questions - [ 08 ]

Total No. of Printed Pages 03

|          |  |
|----------|--|
| G.R. No. |  |
|----------|--|

Paper code - U218-135 (BE-FF)

**MAY 2019/ENDSEM**

**S. Y. B. TECH. (E&TC) (SEMESTER - I)**

**COURSE NAME: DIGITAL ELECTRONICS**

**COURSE CODE: ETUA21175**

**(PATTERN 2017)**

Time: [2 Hours]

[Max. Marks: 50]

**(\*) Instructions to candidates:**

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data where ever required

Q 1) a) A four variable function is given by, [6]  
 $F(A,B,C,D) = \sum m(2,9,10,12,13) + D(15,14)$ . Use k-map to minimize the function in SOP.

OR


b) A four variable function is given as [6]  
 $f(A,B,C,D) = \sum m(0,2,3,4,5,7,9,13,15)$ . Use a K-map to minimize the function in SOP.

Q 2) a) A certain telephone exchange uses multiplexers for routing calls [6]  
from its exchange to another. Design a multiplexer having capacity of eight inputs and single output which routes only odd number of inputs.

OR


b) Develop a combinational system which has three input and [6]  
produces output Y. Whenever even number of ones are detected by the system Output  $Y=1$ . Write the truth table and draw its logic diagram.

 Q 3) a) Determine the Q and  $\bar{Q}$  output waveforms of the flip-flop D and [6]  
CLK inputs shown in Figure. Assume the positive edge triggered flip-flop is initially reset.



OR

 - b) Draw the Q output relative to the clock for a D flip-flop with the inputs as shown in fig. Assume positive edge triggering and Q initially LOW. [6]



- Q 4) a) Design a sequential circuit which will follow the sequence 000, 001, 010, 011, 100, 101, 000... using suitable flip-flop and draw its logic diagram. [4]

OR

- b) Design a synchronous circuit using suitable flip-flop which will follow the sequence 00, 01, 10, 11, 00... write its truth table and draw its logic diagram. [4]

- Q 5) a) A certain CMOS IC has four two input NAND gates. Draw the internal structure of single NAND gate and explain its working for all the possible input combinations. [6]

- b) Draw the block diagram of generic FPGA architecture, and write its parameters. [4]

- c) Determine the High-level and Low-level noise margins for CMOS and for TTL. [4]

For 5V CMOS,  $V_{IH(min)} = 3.5\text{ V}$ ,  $V_{IL(max)} = 1.5\text{ V}$ ,

$V_{OH(min)} = 4.4\text{ V}$ ,  $V_{OL(max)} = 0.33\text{ V}$ .

For 5V TTL,  $V_{IH(min)} = 2\text{ V}$ ,  $V_{IL(max)} = 0.8\text{ V}$ ,

$V_{OH(min)} = 2.4\text{ V}$ ,  $V_{OL(max)} = 0.4\text{ V}$

OR

- Q 6) a) A certain TTL IC has four two input NAND gates. Draw the internal structure of single NAND gate and explain its working for all the possible input combinations. [6]


- b) A certain CMOS IC is of NOT gate. Draw the internal structure of CMOS NOT gate and explain the working for all the possible input combination. [4]

- c) Three open-collector AND gate are connected in a wired AND configuration as shown in figure. Assume that the wired-AND circuit is driving four standard TTL inputs (-1.6 mA each). [4]

i) Write the logic expression for X.

 ii) Determine the minimum value of  $R_p$  if  $I_{OL(max)}$  for each gate is 30 mA and  $V_{OL(max)}$  is 0.4 V





- Q 7) a) A long sequences of pulses enters a synchronous sequential circuit which is required to produce an output  $z=1$ , whenever the sequence 1111 occurs. Design the non-overlapping system and draw its logic diagram. [6]
- b) Design a sequence detector which will produce output  $z=1$ , whenever the sequence 101 occurs. [4]
- c) Write truth table, excitation table for SR flip-flop and draw its state diagram. [4]

OR

- Q 8) a) A long sequences of pulses enters a synchronous sequential circuit which is required to produce an output  $z=1$ , whenever the sequence 1111 occurs. Design the non-overlapping system and draw its logic diagram. [6]
- b) Write truth table, excitation table for JK flip-flop and draw its state diagram. [4]
- c) With suitable example explain the following terms: [4]  
1. State Table 2. State diagram