

G.R. No.	
----------	--

Paper Code - U218-136 (BE-FS)

MAY 2019/ENDSEM

S. Y. B. TECH. (E & TC) (SEMESTER - I)

COURSE NAME: NETWORK THEORY

COURSE CODE: ETUA21176

(PATTERN 2017)

Time: [2 Hours]

[Max. Marks: 50]

(*) Instructions to candidates:

- 1) Answer Q.1, Q.2, Q.3, Q.4, Q.5 OR Q.6, Q.7 OR Q.8
- 2) Figures to the right indicate full marks.
- 3) Use of scientific calculator is allowed
- 4) Use suitable data wherever required

Q1 a) For the circuit of Fig 1. below, determine all four nodal voltages.

[6]

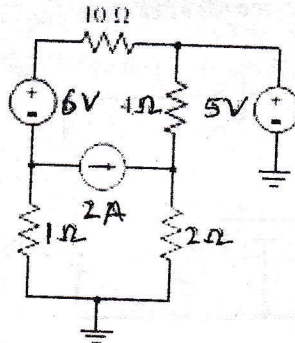


FIG. 1

OR

b) Determine all mesh currents. (Refer figure 2)

[6]

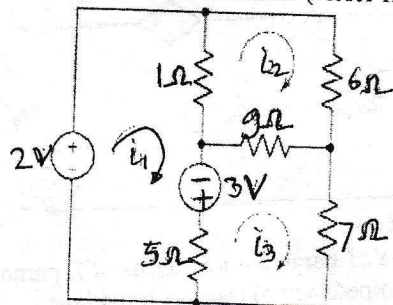


FIG. 2

Q2 a) Obtain thevenin's equivalent network for the following network (FIG. 3)

[6]

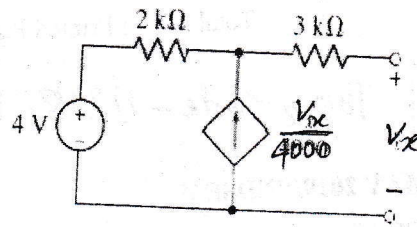


FIG. 3
OR

- b) State and prove maximum power transfer theorem for reactive load. State its applications (any two). [6]

- Q3 a) A parallel resonant circuit has an inductor 0.1 H with quality factor 5. Determine the capacitance and the coil resistance at resonant frequency 100 Hz. Also find the impedance at resonance. [6]

OR

- b) Define Quality factor. Draw the frequency response for series resonant circuit and Prove that under resonance, the series-resonant circuit amplifies the voltage. [6]

- Q4 a) Describe the concept and physical significance of complex frequency. [4]

OR

- b) In the following circuit the switch is moved from position 1 to 2 at $t=0$. Prior to this the steady state was reached. Determine $i(t)$ after switching. (FIG. 4) [4]

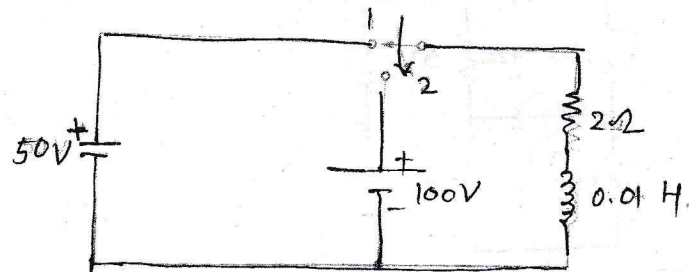


FIG. 4

- Q5 a) Determine Z parameters Z_{11} and Z_{22} for the following network (Fig5) [6]


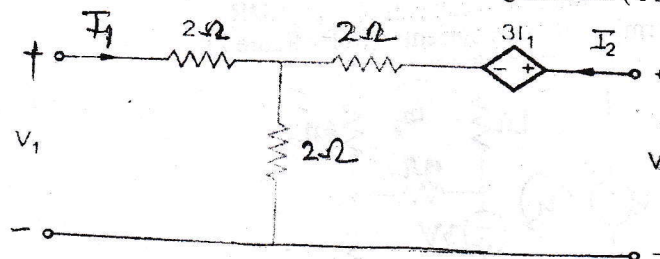


FIG 5

- b) Derive the expressions for Y_{11} and Y_{21} parameters in terms of Z parameters [4]
c) Describe in details a) driving point impedance b) transfer impedance [4]

OR

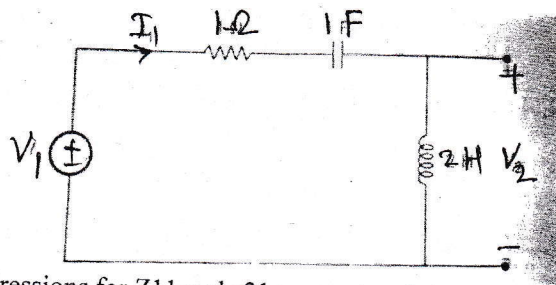- Q6 a) Determine V_2/V_1 and V_1/I_1 for network given below [6]



- b) Derive the expressions for Z_{11} and z_{21} parameters in terms of Y parameters [4]
 c) Determine transmission parameters for T network consisting of each series arm 100 ohm and shunt arm 200 ohm [4]
- Q7 a) Design a constant K Band pass filter with cutoff frequencies 4000 Hz and 10,000 Hz with design impedance, 0.5 k ohms [6]
 b) For prototype T network with each series arm $Z_1/2$ and shunt arm Z_2 Prove that $Z_0 = \sqrt{Z_{OC}Z_{SC}}$ [4]
 c) Derive the expression for Characteristics impedance of Symmetrical T network [4]
- OR**
- Q8 a) In constant K LPF, Each series arm consists of inductor of 0.06 H and shunt arm consists of capacitor of 200 nano farad. Determine design impedance, cut off frequency, Characteristics impedance Z_{OT} at 1 KHz. [6]
 b) What are constant K filters? Draw the curve for attenuation and phase constant of constant k LPF. [4]
 c) Design T attenuator for 20 dB attenuation and design impedance 600 ohms [4]